


UNIT - IDigital system and binary numbers

Introduction: In a real time basic signal is analog signal
analog signal is converted into digital signal

Analog signal:


- * It is a continuous time signal with respect to the amplitude

Ex: Sinusoidal signal

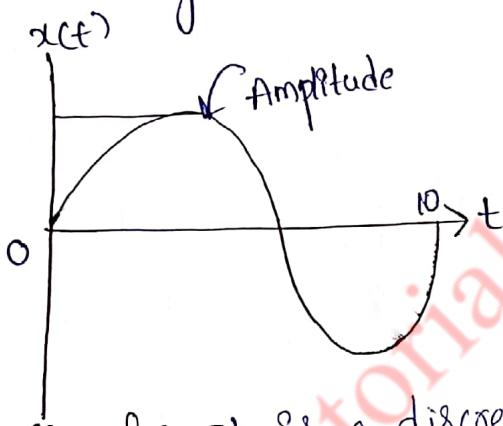

Digital signal: It is a discrete time signal. It's binary digits.

Ex: pulse signal

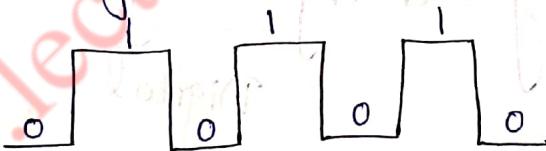


Convert analog to digital signal:

Basically analog to digital signal is conversion in a three steps.

1. Sampling

2. quantisation

3. coding

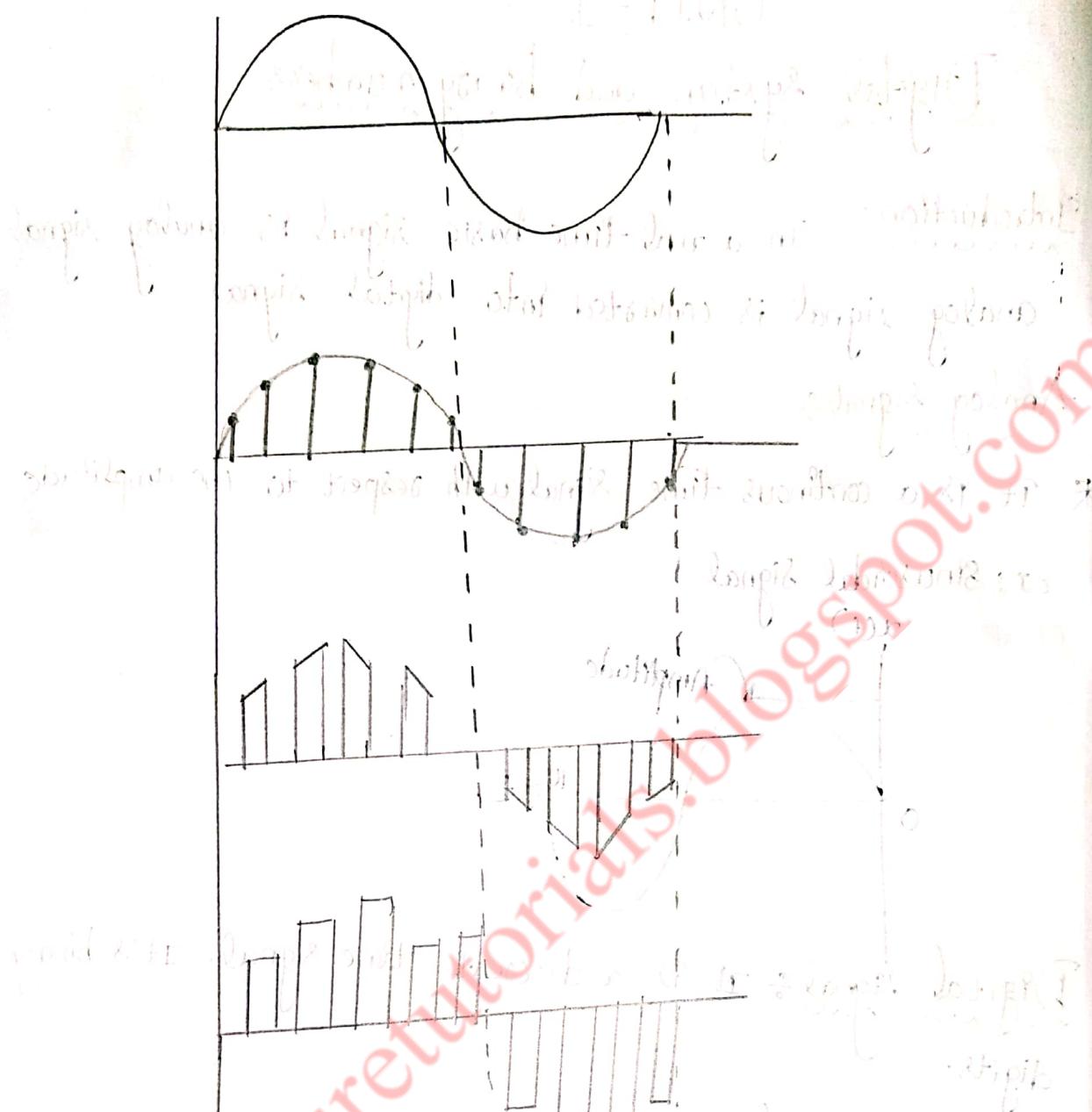

* Difference between analog and digital signal

| Analog | Digital |
|----------------------------|---------------------------|
| * low accuracy | * more accuracy |
| * procedure is slow | * procedure is large |
| * size is large | * size is small |
| * Expensive (or) high cost | * low cost |
| * It is not upgraded | * It is easily upgradable |
| * more noise occurs | * low noise occurs |

logic gates:

Basically logic gates are three types. They are

t.me/jntukonlinebits


1) AND gate

2) OR gate

3) NOT gate

AND gate:

The AND gate symbol is given below,

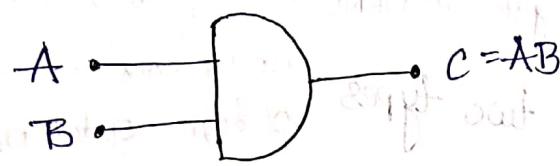


Truth table:

| A | B | C = AB |
|---|---|--------|
| 0 | 0 | 0 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | 1 |


OR gate:

The OR gate symbol is given below

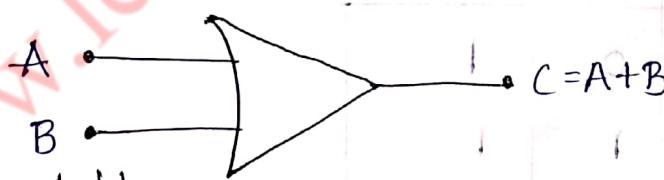

Truth table:

| A | B | C = A + B |
|---|---|-----------|
| 0 | 0 | 0 |
| 1 | 0 | 1 |
| 0 | 1 | 1 |
| 1 | 1 | 1 |

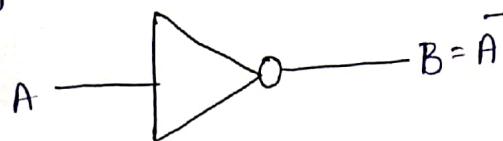NOT gate:NOT gate symbol is given belowtruth table:

| A | B = \bar{A} |
|---|-------------|
| 0 | 1 |
| 1 | 0 |

Universal gates: Universal gates are NAND, NOR. By using NAND and NOR we can construct any type of logic gate.


The universal gates are two types

NAND and NOR easily constructed Transistor Circuits.

1. NAND
2. NOR

1. NAND gate:The NAND gate symbol is given belowTruth table:

| A | B | C = \bar{AB} |
|---|---|--------------|
| 0 | 0 | 1 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 0 |

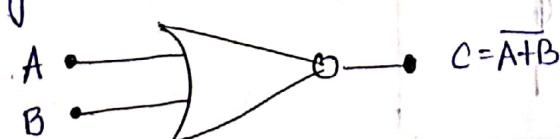NOR gate:NOR gate symbol is given below

truth table :-

t.me/jntukonlinebits

| A | B | C = A + B |
|---|---|-----------|
| 0 | 0 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 1 |

| A | B | C = A + B |
|---|---|-----------|
| 0 | 0 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 1 |

Design :- Design means to reduce the logic gates to generate logic gates


different components are connected to the sequential manner (or) sequence manner

Exclusive gates :-

X-OR gate :-

X-OR gate symbol is given below

Symbol :-

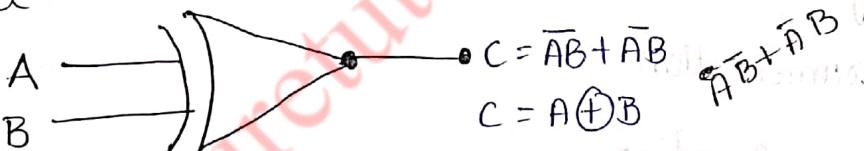


Truth table :-

| A | B | C = $\bar{A}B + \bar{A}B$ |
|---|---|---------------------------|
| 0 | 0 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 0 |

X-NOR gate :-

X-NOR gate symbol is given below

Symbol :-

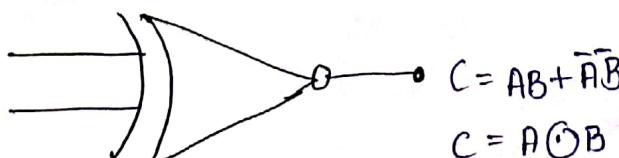

truth table :-

t.me/jntukonlinebits

| A | B | C = A ⊕ B |
|---|---|-----------|
| 0 | 0 | 1 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | 1 |

Feature & scope of digital logic design :-

The digital logic design mainly use is for real time applications.

- Tele communication
- Internet of thing (IOT)
- Cloud computing
- body area networking
- Information technology
- micro web point
- satelight & optical fibre technology
- Instrumentation
- Remote searching
- Signal processing
- Image processing

Digital system and Binary Numbers

Digital system or number system :-

- The basic digital decimal number system with qts 10 digits they are 0, 1, 2, 3, 4, 5, 6, 7, 8, 9.
- In digital communication operate with binary numbers which qts use only the digits 0s and 1s.
- The number systems are basically four types they are:
 - i) Binary number system (2)
 - ii) Octal number system (8)
 - iii) Decimal number system (10)
 - iv) Hexadecimal number system (16)

(i) Binary number system (2) :-

- The binary number system are used qts 0s and 1s
- The binary Position Values as a power of '2' qts represented by

| | | | | | | | | |
|-------|-------|-------|-------|---|----------|----------|----------|-------|
| 2^3 | 2^2 | 2^1 | 2^0 | . | 2^{-1} | 2^{-2} | 2^{-3} | |
|-------|-------|-------|-------|---|----------|----------|----------|-------|

MSB - Most significance Bit

LSB -

Least significance Bit

Ex:- Represent binary number 1101.101 in power of

2. find qts decimal Equivalent

| | | | | | | | | |
|---|---|---|---|---|---|---|---|---|
| 8 | 8 | 8 | 8 | 8 | 8 | 8 | 8 | 8 |
|---|---|---|---|---|---|---|---|---|

| 2^3 | 2^2 | 2^1 | 2^0 | 2^{-1} | 2^{-2} | 2^{-3} |
|-------|-------|-------|-------|----------|----------|----------|
| 1 | 1 | 0 | 1 | . | 1 | 0 |

$$N = 1 \times 2^3 + 1 \times 2^2 + 0 \times 2^1 + 1 \times 2^0 + 1 \times 2^{-1} + 0 \times 2^{-2} + 1 \times 2^{-3}$$

$$N = 8 + 4 + 0 + 1 + \frac{1}{8} + 0 + 1/8$$

$$N = (13.625)_{10}$$

Ex-2 $(1001101.10111)_2$

$$2^6 \quad 2^5 \quad 2^4 \quad 2^3 \quad 2^2 \quad 2^1 \quad 2^0 \quad 2^{-1} \quad 2^{-2} \quad 2^{-3} \quad 2^{-4} \quad 2^{-5}$$

| | | | | | | | | | | | | |
|---|---|---|---|---|---|---|---|---|---|---|---|---|
| 1 | 0 | 0 | 1 | 1 | 0 | 1 | . | 1 | 0 | 1 | 1 | 1 |
|---|---|---|---|---|---|---|---|---|---|---|---|---|

$$N = 1 \times 2^6 + 0 \times 2^5 + 0 \times 2^4 + 1 \times 2^3 + 1 \times 2^2 + 0 \times 2^1 + 1 \times 2^0 + 1 \times 2^{-1} + 0 \times 2^{-2} + 1 \times 2^{-3} + 1 \times 2^{-4} \times 1 \times 2^{-5}$$

$$N = 64 + 8 + 4 + 2 + 0.5 + 0.125 + 0.0625 + 0.03125$$

$$N = (78.71875)_{10}$$

* The octal number system uses first eight values are

decimal number system. they are 0, 1, 2, 3, 4, 5, 6, 7.

It's base is 8, octal position value as a power of 8.

represented is given by

| 8^3 | 8^2 | 8^1 | 8^0 | . | 8^{-1} | 8^{-2} | 8^{-3} |
|-------|-------|-------|-------|---|----------|----------|----------|
| MSB | | | | | | | LSB |

* Represent octal number 567 in power of 8 and find its decimal equivalent.

$$[8^0 = 1]$$

decimal Equivalent:

| 8^2 | 8^1 | 8^0 |
|-------|-------|-------|
| 5 | 6 | 7 |

$$N = 5 \times 8^2 + 6 \times 8^1 + 7 \times 8^0$$

$$= 5 \times 64 + 6 \times 8 + 7 \times 1$$

$$N = (375)_{10}$$

* $(4271.635)_8$

| 8^3 | 8^2 | 8^1 | 8^0 | . | 8^{-1} | 8^{-2} | 8^{-3} |
|-------|-------|-------|-------|---|----------|----------|----------|
| 4 | 2 | 7 | 1 | . | 6 | 3 | 5 |

$$N = 1 \times 8^0 + 7 \times 8^1 + 2 \times 8^2 + 4 \times 8^3 + 6 \times 8^{-1} + 3 \times 8^{-2} + 5 \times 8^{-3}$$

$$= 1 + 56 + 128 + 2048 + 6.125 + 0.1875 + 0.00976$$

$$= 1 + 56 + 128 + 2048 + 6.125 + 0.1875 + 0.00976$$

$$= (2239.80)_{10}$$

* $(64562.1057)_8$

| 8^4 | 8^3 | 8^2 | 8^1 | 8^0 | . | 8^{-1} | 8^{-2} | 8^{-3} | 8^{-4} |
|-------|-------|-------|-------|-------|---|----------|----------|----------|----------|
| 6 | 4 | 5 | 6 | 2 | . | 1 | 0 | 5 | 7 |

$$N = 6 \times 8^4 + 4 \times 8^3 + 5 \times 8^2 + 6 \times 8^1 + 2 \times 8^0 + 1 \times 8^{-1} + 0 \times 8^{-2} + 5 \times 8^{-3} + 7 \times 8^{-4}$$

$$= 24576 + 2048 + 320 + 48 + 2 + 0.125 + 0.00625 + 0.00968 + 0.0017089$$

$$N = (26994.13639)_{10}$$

∴ To convert an octal number to decimal multiply each digit by 8^n and add the results.

Decimal number system :-

→ In Decimal number system we can express any decimal number in units, tens, hundreds and thousands.

→ In Decimal number system the numbers are 0, 1, 2, 3, 4, 5, 6, 7, 8, 9

→ The Decimal position values as a power of 10 is represented by

| | | | | | | | |
|-----|--------|--------|--------|-----------|-----------|-----------|-----|
| ... | 10^2 | 10^1 | 10^0 | 10^{-1} | 10^{-2} | 10^{-3} | ... |
|-----|--------|--------|--------|-----------|-----------|-----------|-----|

MSB

LSB

Ex :- 6587.6

$10^3 \quad 10^2 \quad 10^1 \quad 10^0$

| | | | | | | |
|---|---|---|---|---|---|---|
| 6 | 5 | 8 | 7 | . | 6 | 0 |
|---|---|---|---|---|---|---|

$$\begin{aligned}
 N &= 6 \times 10^3 + 5 \times 10^2 + 8 \times 10^1 + 7 \times 10^0 + 6 \times 10^{-1} \\
 &= 6000 + 500 + 80 + 7 + 0.6 \\
 &= 6587.6
 \end{aligned}$$

Hexa Decimal number system :-

→ The Hexa Decimal number system as a base of 16.

→ The having 16 digits they are 0, 1, 2, 3, 4, 5, 6, 7, 8, 9, A, B, C, D, E, F

→ The hexa decimal position values as a power of 16 is represented by

| | | | | | | |
|--------|--------|--------|--------|-----------|-----------|-----------|
| 16^3 | 16^2 | 16^1 | 16^0 | 16^{-1} | 16^{-2} | 16^{-3} |
| MSB | | | | | | LSB |

Ex: Represents Hexadecimal number '3FD' in power of 16
and find Decimal equivalent.

| | | |
|--------|--------|--------|
| 16^2 | 16^1 | 16^0 |
| 3 | F | D |

$$N = 3 \times 16^2 + F \times 16^1 + D \times 16^0$$

$$= 3 \times 256 + 15 \times 16 + 13 \times 1$$

$$= (1021)_{10}$$

Ex: FDE42A.1DB9

| | | | | | | | | | | |
|--------|--------|--------|--------|--------|--------|-----------|-----------|-----------|-----------|---|
| 16^5 | 16^4 | 16^3 | 16^2 | 16^1 | 16^0 | 16^{-1} | 16^{-2} | 16^{-3} | 16^{-4} | |
| F | D | E | 4 | 2 | A | . | 1 | D | B | 9 |

$$N = 15 \times 16^5 + 13 \times 16^4 + 14 \times 16^3 + 4 \times 16^2 + 2 \times 16^1 + 10 \times 16^0 +$$

$$1 \times 16^{-1} + 13 \times 16^{-2} + 11 \times 16^{-3} + 9 \times 16^{-4}$$

$$= 16639018 + 851968 + 57344 + 1024 + 32 + 10 + 0.0625 +$$

$$0.0507 + 0.0026 + 0.00013732$$

$$= (17549396.127)_{10}$$

Relation b/w binary, decimal, hex decimal

below tables.

| Decimal | Binary | Hexa Decimal |
|---------|--------|--------------|
| 0 | 0000 | 0 |
| 1 | 0001 | 1 |
| 2 | 0010 | 2 |
| 3 | 0011 | 3 |

| <u>Decimal</u> | <u>Binary</u> | <u>Hexa Decimal</u> |
|----------------|---------------|---------------------|
| 4 | 0100 | 4 |
| 5 | 0101 | 5 |
| 6 | 0110 | 6 |
| 7 | 0111 | 7 |
| 8 | 1000 | 8 |
| 9 | 1001 | 9 |
| 10 | 1010 | A |
| 11 | 1011 | B |
| 12 | 1100 | C |
| 13 | 1101 | D |
| 14 | 1110 | E |
| 15 | 1111 | F |

Counting in Radix (Base) $r \div$

Radix (Base) r the number

character in set

$$r=2$$

0, 1

$$r=8$$

0, 1, 2, 3, 4, 5, 6, 7

$$r=10$$

0, 1, 2, 3, 4, 5, 6, 7, 8, 9

$$r=16$$

0, 1, 2, 3, 4, 5, 6, 7, 8, 9,
A, B, C, D, F

Ex: To find Decimal values of 0 to 9 by using radix 5.

t.me/jntukonlinebits

| Decimal | Radix 5 | |
|---------|---------|-----------------------------------|
| 0 | 00 | $0 \times 5^1 + 0 \times 5^0 = 0$ |
| 1 | 01 | $0 \times 5^1 + 1 \times 5^0 = 1$ |
| 2 | 02 | $0 \times 5^1 + 2 \times 5^0 = 2$ |
| 3 | 03 | $0 \times 5^1 + 3 \times 5^0 = 3$ |
| 4 | 04 | $0 \times 5^1 + 4 \times 5^0 = 4$ |
| 5 | 10 | $1 \times 5^1 + 0 \times 5^0 = 5$ |
| 6 | 11 | $1 \times 5^1 + 1 \times 5^0 = 6$ |
| 7 | 12 | $1 \times 5^1 + 2 \times 5^0 = 7$ |
| 8 | 13 | $1 \times 5^1 + 3 \times 5^0 = 8$ |
| 9 | 14 | $1 \times 5^1 + 4 \times 5^0 = 9$ |

* find the decimal equivalent of 231.231 base 4.

$$N = 2 \times 16 + 3 \times 4 + 1 \times 4 + 2 \times 4^{-1} + 3 \times 4^{-2}$$

| | | | | | |
|---|---|---|---|---|---|
| 2 | 3 | 1 | . | 2 | 3 |
|---|---|---|---|---|---|

$$= 32 + 12 + 4 + 0.5 + 0.1875$$

$$= (48.6875)_{10}$$

Number base conversion

→ The decimal, binary, octal and hexadecimal table

| Decimal | Binary | Octal | Hexa |
|---------|--------|-------|------|
| 0 | 0000 | 0 | 0 |
| 1 | 0001 | 1 | 1 |
| 2 | 0010 | 2 | 2 |

| Decimal | Binary 8421 | Octal | Hexadecimal |
|---------|----------------|-------|-------------|
| 3 | 0011 | 3 | 3 |
| 4 | 0100 | 4 | 4 |
| 5 | 0101 | 5 | 5 |
| 6 | 0110 | 6 | 6 |
| 7 | 0111 | 7 | 7 |
| 8 | 1000 | 10 | 8 |
| 9 | 1001 | 11 | 9 |
| 10 | 1010 | 12 | A |
| 11 | 1011 | 13 | B |
| 12 | 1100 | 14 | C |
| 13 | 1101 | 15 | D |
| 14 | 1110 | 16 | E |
| 15 | 1111 | 17 | F |

Conversions

- Basically binary, octal, hexadecimal conversions or 6 types
1. Binary to octal
 2. Octal to Binary
 3. Binary to Hexa
 4. Hexa to Binary
 5. Octal to Hexa
 6. Hexa to Octal

1. Binary to Octal

→ The binary numbers are 0 and 1. The octal number table given below
0 to 7 the octal number table 98 given below

| Decimal | Binary - $\frac{0}{4^2}$ |
|---------|--------------------------|
| 0 | 000 |
| 1 | 001 |
| 2 | 010 |
| 3 | 011 |
| 4 | 100 |
| 5 | 101 |
| 6 | 110 |
| 7 | 111 |

Ex: Convert $(110101010.101010)_2$ to octal

Sol:

$$\begin{array}{ccccc} \underline{110} & \underline{101} & \underline{010} & \cdot & \underline{101} & \underline{010} \\ \downarrow & \downarrow & \downarrow & & \downarrow & \downarrow \\ 6 & 5 & 2 & & 5 & 2 \end{array}$$

$$\therefore (652.52)_8$$

Ex: $(1001010.010)_2$

$$\begin{array}{ccccccccc} 100 & 101 & 010 & \cdot & 101 & 10 & 010 & 101 & \cdot 010 \underline{100} \\ \downarrow & \downarrow & \downarrow & & \downarrow & & & & \downarrow \\ 4 & 5 & 2 & & 5 & & & & 5 \end{array}$$

$$(452.5)_8$$

Ex:

Q1) Octal to Binary Conversion

t.me/jntukonlinebits

Ex: $(643.27)_8$

6 4 3 . 2 7
↓ ↓ ↓ ↓ ↓
110 100 011 010 011

$$\therefore (110100011 \cdot 010111)_2$$

Q2) Binary to Hexa Conversion

Ex: $(1101100010011011)_2$

1101 1000 1001 1011
↓ ↓ ↓ ↓
D 8 9 B

$$(D89B)_{16}$$

$$\therefore (D89B)_H$$

Q3) Hexa to Binary Conversion

Ex: Convert $(3FD)H$

3 F D
↓ ↓ ↓
0011 1111 100101

$$(0011\ 1111\ 1001)_2$$

Ex: $(F9B0 \cdot 1D8)H$

F 9 B O . 1 D 8
↓ ↓ ↓ ↓ ↓ ↓
1111 1001 1011 0000 0001 0101 1000

$$(1111\ 1001\ 1011\ 0000\ 0001\ 1101\ 1000)_2$$

Ex: Convert $(5A89.B4)_{16}$ to binary

t.me/jntukonlinebits

5 A 8 9 . B 4
↓ ↓ ↓ ↓ ↓ ↓
0101 1010 1000 1001 1011 0100

$(0101\ 1010\ 1000\ 1001\ 1011\ 0100)_2$

v) Octal to Hexadecimal:

→ The easiest way to convert octal number to Hexadecimal number in two steps.

i) convert octal number to binary form

ii) convert binary form to Hexadecimal

iii) convert binary form to its Hexadecimal equivalent.

Ex: Convert $(615)_8$ to its Hexadecimal equivalent.

i) $(615)_8$

ii) Octal - Binary:

6 1 5
↓ ↓ ↓
 $(110\ 001\ 101)_2$

iii) Binary - Hexa (110001101)

0001 1100 0001 1101
↓ ↓ ↓ D
1 8 D
 $\therefore (18D)_{16}$

Ex: $(7523.426)_8$

ii) Octal - binary

7 5 2 3 . 4 6
↓ ↓ ↓ ↓ ↓ ↓
111 101 010 011 100 010 110

0001 1110 1010 0111 0001 10110 110010110

iii) Binary - Hexa

001 1110 1010 0111 0001 10110 110010110
↓ ↓ ↓ ↓ ↓ ↓
1 E A 7 F F 6

$\therefore (1EA7F6)_{16}$

vi) Hexa to octal conversion:

t.me/jntukonlinebits

→ The hexa decimal to octal conversion two steps is there

(i) Convert Hexa to binary

(ii) Convert binary - octal

Ex: Convert $(25B)_H$ to its octal equivalent

$(25B)_H$

(i) Hexa to binary

2 5 B
↓ ↓ ↓
0010 0101 1011

(ii) binary - octal

0010 0101 1011
↓ ↓ ↓
1 3 3

$\therefore (1133)_8$

Ex: ② $(9DF6.C83)_H$

(i) Hexa to binary

9 D F 6 C 8 3
↓ ↓ ↓ ↓ ↓ ↓
1001 1101 1111 0110 1100 1000

(ii) binary - octal

1001 1101 1111 0110 1100 1000
1001 1101 1111 0110 1100 1000

010 011 011 111 1011 011 001 000
↓ ↓ ↓ ↓ ↓ ↓ ↓
2 3 3 7 3 3 1 0

$(93373310)_8$

* Convert any Radix to Decimal $\frac{1}{r}$

t.me/jntukonlinebits

In general the number can be represented as

$$N = A_{n-1} r^{n-1} + A_{n-2} r^{n-2} + \dots + A_1 r^1 + A_0 r^0 + A_{-1} r^{-1} + A_{-2} r^{-2} + \dots + A_{-m} r^{-m}$$

where N = number in decimal

A = digit

r = radix (or) base of a number system

n = The number of digits in the integer portion of number

m = The no. of digits in the fractional portion of number

① $(1101.1)_2$ to convert Decimal

② $(475.25)_8$ to convert Decimal

③ $(9B2.1A)_4$ to convert Decimal

④ $(3102.12)_4$ to Decimal

⑤ $(614.15)_7$ to Decimal

① $(1101.1)_2$

| 2^3 | 2^2 | 2^1 | 2^0 | 2^{-1} |
|-------|-------|-------|-------|----------|
| 1 | 1 | 0 | 1 | . |

$$N = 1 \times 2^3 + 1 \times 2^2 + 0 \times 2^1 + 1 \times 2^0 + 1 \times \frac{1}{2}$$

$$= (13.5)_{10}$$

② $(475.25)_8$

| 8^2 | 8^1 | 8^0 | 8^{-1} | 8^{-2} |
|-------|-------|-------|----------|----------|
| 4 | 7 | 5 | . | 2 |

| | | | | | |
|---|---|---|---|---|---|
| 4 | 7 | 5 | . | 2 | 5 |
|---|---|---|---|---|---|

$$N = 4 \times 8^2 + 7 \times 8^1 + 5 \times 8^0 + 2 \times 8^{-1} + 1 \times 8^{-2}$$

$$= (317.328)_8$$

$$\textcircled{3} \quad (9B2.1A)_{16}$$

| 16^2 | 16^1 | 16^0 | 16^{-1} | 16^{-2} |
|--------|--------|--------|-----------|-----------|
| 9 | B | 2 | . | A |

$$N = 9 \times 16^2 + B \times 16^1 + 2 \times 16^0 + 1 \times 16^{-1} + A \times 16^{-2}$$

$$= (2482.101563)_{10}$$

$$\textcircled{4} \quad (3102.12)_{12}$$

| 4^3 | 4^2 | $4^1 4^0$ | 4^{-1} | 4^{-2} |
|-------|-------|-----------|----------|----------|
| 3 | 1 | 0 2 | . | 1 2 |

$$N = 3 \times 4^3 + 1 \times 4^2 + 2 \times 1 + 1 \times 1/4 + 2 \times 1/16$$

$$= (210.375)_{10}$$

$$\textcircled{5} \quad (614.15)_{7}$$

| 7^2 | 7^1 | 7^0 | 7^{-1} | 7^{-2} |
|-------|-------|-------|----------|----------|
| 6 | 1 | . 4 | . | 1 1 5 |

$$N = 6 \times 7^2 + 1 \times 7^1 + 4 \times 7^0 + 1 \times 1/7 + 1 \times 1/49$$

$$N = (301.844)_{10}$$

Conversion of Decimal numbers to radix numbers

→ Basically the conversions of radix numbers are two type

1. successive division for integer part conversion

2. successive multiplication for fractional part conversion

1. successive division for integer part conversion


→ In this method we repeatedly divided the integer part of the decimal number by "r". Until coeff. quotient is '0'.

→ The remainder of each division becomes the numerical in the new radix.

→ The reminders are taken in the reverse order to a new radix number.

→ This means that first remainder is the least significant bit and the last significant is the most significant bit in the new radix number.

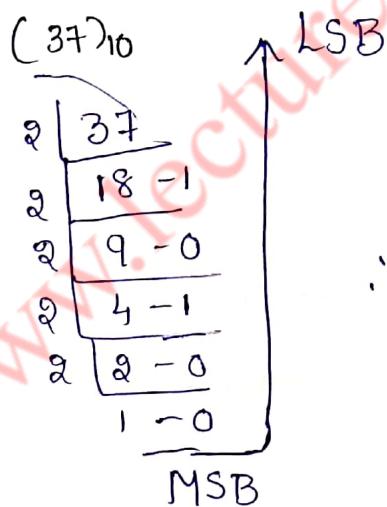Ex: Convert decimal number 37 to binary equivalent



$$\therefore (1001011)_2$$

$$\therefore (37)_{10} = (1001011)_2$$

Verification:

$$2^5 \quad 2^4 \quad 2^3 \quad 2^2 \quad 2^1 \quad 2^0 \\ 1 \quad 0 \quad 0 \quad 1 \quad 0 \quad 0 \quad 1$$

$$= 1 \times 2^5 + 1 \times 2^2 + 1 \times 2^0$$

$$= 32 + 4 + 1 \times 1$$

$$= 37$$

AM

1) $(625)_{10}$ to Binary

2) $(739)_{10}$ to "

3) $(523)_{10}$ to Octal

4) $(649)_{10}$ "

Ex :- convert decimal to octal

t.me/jntukonlinebits

(Q14)

$$\begin{array}{r} 8 \mid 214 \\ 8 \boxed{26 - 6} \\ 3 - 2 \end{array}$$

$\therefore (326)_8$

Ex :- Convert decimal number (3509) to Hexa decimal Equivalent

$$\begin{array}{r} 16 \mid 3509 \\ 16 \boxed{219 - 5} \\ 16 \boxed{13 - 11} \end{array}$$

$\therefore (DB5)_{16}$

Ex :- convert decimal to Hexa (4559)

Ex :- convert decimal to Hexa (5320)

(i) (4559)

$$\begin{array}{r} 16 \mid 4559 \\ 16 \boxed{284 - 15} \\ 16 \boxed{17 - 12} \\ 16 \boxed{1 - 1} \end{array}$$

$(15\ 12\ 11)_{16}$

$\therefore (4559) = (FCB)_{16}$

(ii) (5320)

$$\begin{array}{r} 16 \mid 5320 \\ 16 \boxed{332 - 8} \\ 16 \boxed{20 - 12} \\ 16 \boxed{1 - 4} \end{array}$$

$\therefore (5320) = (8\ 12\ 4\ 1)$

$\therefore (8\ C\ 4\ 1)_{16}$

2. Successive multiplication for fractional Part Conversion
 t.me/jntukonlinebits

→ convert 0.8125 to Binary

| fractional | Radix | Result | Recorded carry | MSB |
|------------|------------|-------------------|----------------|-----|
| 0.8125 | $\times 2$ | $= 1.625 = 0.625$ | with carry 1 | |
| 0.625 | $\times 2$ | $= 1.25 = 0.25$ | with carry 1 | |
| 0.25 | $\times 2$ | $= 0.5 = 0.5$ | with carry 0 | |
| 0.5 | $\times 2$ | $= 1.0 = 0.0$ | with carry 1 | LSB |

$$\therefore (0.8125)_{10} = (0.1101)_2$$

→ convert 0.95 to Decimal number to its binary equivalent

| fractional | Radix | Result | Recorded carry |
|------------|------------|---------------|----------------|
| 0.95 | $\times 2$ | $= 1.9 = 0.9$ | with carry 1 |
| 0.9 | $\times 2$ | $= 1.8 = 0.8$ | with carry 1 |
| 0.8 | $\times 2$ | $= 1.6 = 0.6$ | " 1 |
| 0.6 | $\times 2$ | $= 1.2 = 0.2$ | " 0 |
| 0.2 | $\times 2$ | $= 0.4 = 0.8$ | " 0 |
| 0.4 | $\times 2$ | $= 0.8 = 0.8$ | " 0 |
| 0.8 | $\times 2$ | $= 1.6 = 0.6$ | " 0 1 |

$$(0.95)_{10} = (0.1110001)_2$$

i) 625 to Binary

$$\begin{array}{r}
 2 | 625 \\
 2 | 312 - 1 \\
 2 | 156 - 0 \\
 2 | 78 - 0 \\
 2 | 39 - 0 \\
 2 | 19 - 1
 \end{array}$$

$$\begin{array}{r}
 2 | 9 - 1 \\
 2 | 4 - 1 \\
 2 | 2 - 0 \\
 2 | 1 - 0
 \end{array}$$

~~(1000111001)~~ $(1001110001)_2$ t.me/jntukonlinebits

Verification:

| | | | | | | | | |
|-------|-------|-------|-------|-------|-------|-------|-------|-------|
| 2^8 | 2^7 | 2^6 | 2^5 | 2^4 | 2^3 | 2^2 | 2^1 | 2^0 |
| 1 | 0 | 0 | 0 | 1 | 1 | 1 | 0 | 0 |

$$N = 1 \times 2^8 + 1 \times 2^4 + 1 \times 2^3 + 1 \times 2^2$$

② 739

| | | |
|---|---------|-----|
| 2 | (739) | LSB |
| 2 | 969 - 1 | |
| 2 | 184 - 1 | |
| 2 | 92 - 0 | |
| 2 | 46 - 0 | |
| 2 | 23 - 0 | |
| 2 | 11 - 1 | |
| 2 | 5 - 1 | |
| 2 | 2 - 1 | |
| 2 | 1 - 0 | MSB |

③ 523

| | | |
|---|--------|--|
| 8 | (523) | |
| 8 | 65 - 3 | |
| 8 | 8 - 1 | |
| 8 | 1 - 0 | |

$$\therefore (1013)_8$$

④ 649

| | | |
|---|--------|--|
| 8 | (649) | |
| 8 | 81 - 1 | |
| 8 | 10 - 1 | |
| 8 | 1 - 2 | |

$$(1211)_8$$

Ex: Convert 0.640625 decimal number to octal equivalent
t.me/jntukonlinebits

| Fraction | Radix | Result | Recorded with carry |
|----------|-------|---------------------------------|---------------------|
| 0.640625 | x 8 | = 5.125 = 0.125 with carry 5 | MSB |
| 0.125 | x 8 | = 1.0 = 0.0 with carry 1 | LSB |

$$\therefore (0.640625)_{10} = (0.51)_8$$

(i) (0.925284) (ii) (0.752386)

| Fraction | Radix | Result | Recorded with carry |
|----------|-------|--------------------------|---------------------|
| 0.925284 | x 8 | = 7.402272 = 0.402272 | with carry 7 |
| 0.402272 | x 8 | = 3.218176 = 0.218176 | with carry 3 |
| 0.2 | x 8 | = 1.6 = 0.6 | with carry 1 |
| 0.6 | x 8 | 4.8 | with carry 4 |
| 0.8 | x 8 | 0.8 | with carry 6 |
| 0.8 | x 8 | 6.4 0.4 | |

$$\therefore (0.925284)_{10} = (6.73146)_8$$

(i) (0.752386)

| Fraction | Radix | Result | Recording with carry |
|----------|-------|------------------------|----------------------|
| 0.752386 | x 8 | 6.019088 | with carry 6 |
| 0.01 | x 8 | = 0.01 | with carry 0 |
| 0.08 | x 8 | = 0.08 | with carry 0 |
| 0.12 | x 8 | 0.64 5.12 = 0.12 | with carry 5 |
| 0.96 | x 8 | 0.96 1.68 = 0.68 | with carry 0 |
| 0.68 | x 8 | 1.68 0.68 | with carry 1 |

* Convert 0.1289062 Decimal to Hexa Decimal
t.me/jntukonlinebits

| fraction | Radix | Result | Recorded with carry |
|-----------|-------|--------------------------|---------------------|
| 0.1289062 | x 16 | 2.0624992 = 0.0624992 | with carry 2 |
| 0.0624992 | x 16 | 0.999872 = 0.999872 | with carry 9 |
| 0.999872 | x 16 | 15.997952 = 0.997952 | with carry 15 |
| 0.997952 | x 16 | 15 | |
| fraction | Radix | Result | Recorded with carry |
| 0.1289062 | x 16 | 2.0624992 = 0.0625 | with carry 2 |
| 0.0625 | x 16 | = 1.0 0.0 | with carry 1 |

MSB ↓ LSB

$\therefore (0.1289062)_{10} = (0.21)_{16}$

(iii) $(0.15638)_{10}$ iv) $(0.29725)_{10}$ Hexa

$$0.15638 \times 16 = 2.50208$$

0.50

0.8

0.2

0.4

0.1

0.3

0.6

* Convert decimal number 35.45 to octal number

t.me/jntukonlinebits

$$q) (35.45)_{10}$$

(i) Integer part

$$\begin{array}{r} 35 \\ \times 8 \\ \hline 4 \quad 3 \end{array}$$

$$\therefore (35)_{10} = (43)_8$$

∴ (35.45)_{10} = (43.346314)_8

finally

$$\therefore (35.45)_{10} = (43.346314)_8$$

q) fractional part

| fraction | Radix | Result | Recorded with carry |
|----------|------------|--------------------|---------------------|
| 0.45 | $\times 8$ | $= 3.6$ $= 0.6$ | Carry 3 |
| 0.6 | $\times 8$ | $= 4.8$ $= 0.8$ | Carry 4 |
| 0.8 | $\times 8$ | $= 6.4$ $= 0.4$ | Carry 6 |
| 0.4 | $\times 8$ | $= 3.2$ $= 0.2$ | Carry 3 |
| 0.2 | $\times 8$ | $= 1.6$ $= 0.6$ | Carry 1 |
| 0.6 | $\times 8$ | $= 4.8$ $= 0.8$ | Carry 4 |

* Convert $(22.64)_{10}$ to Hexadecimal

(i) Convert $(24.6)_{10}$ to Binary

$$q) (22.64)_{10}$$

(i) Integer part $\div 16$

$$\begin{array}{r} 22 \\ \times 16 \\ \hline 16 \quad 6 \\ \hline 1 \quad 0 \end{array}$$

$$\therefore (22)_{10} = (106)_{16}$$

$$\begin{array}{r} 22.64 \\ \times 16 \\ \hline 16 \quad 6 \\ \hline 1 \quad 0 \end{array}$$

$$\begin{array}{r} 22.64 \\ \times 16 \\ \hline 16 \quad 6 \\ \hline 1 \quad 0 \end{array}$$

$$(10100)$$

(ii) fractional part $\div 0.64$

| fraction | Radix | Result | Recorded time: Antukonlinebits |
|----------|-------------|---------|--------------------------------|
| 0.64 | $\times 16$ | = 10.24 | with carry 10 |
| | | = 0.24 | |
| 0.24 | $\times 16$ | = 3.84 | with carry 3 |
| | | = 0.84 | |
| 0.84 | $\times 16$ | = 13.44 | with carry 13 |
| | | = 0.44 | |
| 0.44 | $\times 16$ | = 7.04 | with carry 7 |
| | | = 0.04 | |
| 0.04 | $\times 16$ | = 0.64 | with carry 0 |
| | | = 0.64 | |
| 0.64 | $\times 16$ | = 10.24 | with carry 10 |
| | | = 0.24 | |

$\therefore (0.64)_{10} = (0.103137010)_2$

finally

$\therefore (24.6)_{10} = (106.103137010)_2$

(iii) $(24.6)_{10}$

(i) Integration part : 24

$$\begin{array}{r} 2 \left[\begin{array}{r} 24 \\ - 12 - 0 \\ \hline \end{array} \right] \\ 2 \left[\begin{array}{r} 6 \\ - 3 - 0 \\ \hline 1 - 1 \end{array} \right] \end{array}$$

$$\therefore (24)_{10} = (11000)_2$$

| fraction | Radix | Result | Recorded with carry |
|----------|-------|----------------|---------------------|
| 0.6 | x 2 | = 1.2 = 0.2 | with carry 1 |
| 0.2 | x 2 | = 0.4 = 0.4 | with carry 0 |
| 0.4 | x 2 | = 0.8 | with carry 0 |
| 0.8 | x 2 | = 1.6 = 0.6 | with carry 1 |
| 0.6 | x 2 | = 1.2 = 0.8 | with carry 1 |

$$(0.6)_{10} = (10011)_2$$

$$\therefore (24.6)_{10} = (11000.10011)_2$$

(iv) (0.29725) to Hexa

| fraction | Radix | Result | Recorded with carry |
|----------|-------|---------------------|---------------------|
| 0.29725 | x 16 | = 4.756 = 0.756 | with carry 4 |
| 0.756 | x 16 | = 12.096 = 0.096 | with carry 12 |
| 0.096 | x 16 | = 15.36 = 0.36 | with carry 15 |
| 0.36 | x 16 | = 5.76 = 0.76 | with carry 5 |
| 0.76 | x 16 | = 12.16 = 0.16 | with carry 12 |
| 0.16 | x 16 | = 2.56 = 0.56 | with carry 2 |
| 0.56 | x 16 | = 8.96 = 0.96 | with carry 8 |

$$0.96 \times 16$$

$$= 15.36$$

with carry 4
f.mle/jatukononlinebits

$$0.36 \times 16$$

$$= 0.36$$

with carry 5

$$= 5.76$$

$$= 0.76.$$

$$\therefore (0.29725)_{10} = (4\text{ }1\text{ }8\text{ }1\text{ }5\text{ }5\text{ }1\text{ }2\text{ }8\text{ }1\text{ }5\text{ }5)_{16}$$

Q1 (0.15638)

| fraction | Radix | Result | Recorded with carry |
|----------|-------------|-----------------------|---------------------|
| 0.15638 | $\times 16$ | 0.50208 $= 0.502$ | with carry 2 |
| 0.502 | $\times 16$ | 8.032 $= 0.032$ | with carry 8 |
| 0.032 | $\times 16$ | 0.512 $= 0.512$ | with carry 0 |
| 0.512 | $\times 16$ | 8.192 $= 0.192$ | with carry 8 |
| 0.192 | $\times 16$ | 3.072 $= 0.072$ | with carry 3 |
| 0.072 | $\times 16$ | 1.152 $= 0.152$ | with carry 1 |
| 0.152 | $\times 16$ | 2.432 $= 0.432$ | with carry 2 |
| 0.432 | $\times 16$ | 6.912 $= 0.912$ | with carry 6 |
| 0.912 | $\times 16$ | 14.592 $= 0.592$ | with carry 4 |
| 0.592 | $\times 16$ | 9.912 $= 0.912$ | with carry 9 |
| 0.912 | $\times 16$ | 15.1552 $= 0.1552$ | with carry 15 |

$$\therefore (0.15638)_{10} = (0.808312614915)_H$$

$$= (28083 C6E9F)_H$$

Complement of numbers:

(i) 1's complement representation:

→ The 1's complement of a binary number is the number that results when we change all 1's to 0's and all 0's to 1's.

• 1's

Ex: find 1's complement of $(1101)_2$

$$(1101)_2$$

$$= 0010$$

Ex: find 1's complement of $(10111010111)_2$

$$(10111010111)_2$$

$$010001010000$$

(ii) 2's complement representation:

→ The 2's complement is the binary number that results when we add 1 to the 1's complement. It can be represented as:

$$[2's \text{ complement} = 1's \text{ complement} + 1]$$

Addition operation:

— truth table

| A | B | Sum | Carry |
|---|---|-----|-------|
| 0 | 0 | 0 | 0 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 1 |

→ The 2's complement form is used to represent a (-ve) numbers.

Ex: Find 2's complement of $(1001)_2$

t.me/jntukonlinebits

$$\begin{array}{r}
 \begin{array}{r}
 \begin{array}{r}
 1 - 0 & 0 \\
 + 1 & \\
 \hline
 1 &
 \end{array} \\
 \hline
 \begin{array}{r}
 1 - 0 & 0 & 1 \\
 + 1 & & \\
 \hline
 \end{array}
 \end{array}
 \end{array}$$

$(1001)_2$ → adding +1

$$\begin{array}{r}
 = 10110 - 1^{\text{st}} \text{ complement} \\
 = 10110 + 1 \\
 \hline
 10111
 \end{array}$$

Ex: $(1010100110)_2$

$0101011001 \rightarrow 1^{\text{st}} \text{ complement}$

$$0 \ 1 \ 0 \ 1 \ 0 \ 1 \ 1 \ 0 \ 0 \ 1$$

$+ 1 \rightarrow \text{adding } +1$

$$\hline 0 \ 1 \ 0 \ 1 \ 0 \ 1 \ 1 \ 0 \ 1 \ 0$$

$$\therefore (1010100110)_2 = (0101011010)$$

1's complement subtraction

→ For subtraction of two numbers we have two cases

(i) subtraction of smaller number from larger number

L - S

(ii) subtraction of larger number from smaller number

S - L

(i) smaller number from larger number

steps: → determine the 1's complement of the smaller number.

1. Determine the 1's complement of the smaller number.

2. Add the 1's complement of the larger number.

3. Remove the carry and adding to the result. This is called
end around the carry

t.me/jntukonlinebits

Ex: Subtract ~~100~~ $(101011)_2$ from $(111001)_2$ using the 1's
Complement method

$(101011)_2$ from $(111001)_2$ (1's complement)

(1) first we find
big number are
large number

$$\begin{array}{r} 2^5 2^4 2^3 2^2 2^1 2^0 \\ \hline 1 & 0 & 1 & 0 & 1 & 1 \end{array}$$

$$= 43$$

$$\begin{array}{r} 2^5 2^4 2^3 2^2 2^1 2^0 \\ \hline 1 & 1 & 1 & 0 & 0 & 1 \end{array}$$

$$= 57$$

L - 5

↓ calculate difference units column → 1st complement
of 101011

$$\begin{array}{r} 1 & 1 & 1 & 0 & 0 & 1 \\ 0 & 1 & 0 & 1 & 0 & 0 \\ \hline 1 & & & & & \end{array}$$

① $\begin{array}{r} 0 & 0 & 0 & 1 & 1 & 0 & 1 \\ + 1 & & & & & & \\ \hline 0 & 0 & 1 & 1 & 1 & 0 \end{array}$

↓ from bottom add +1
End around carry
↓ from bottom add +1
↓ from bottom add +1
↓ from bottom add +1
 $\therefore (001110)$

$$\begin{array}{r} 57 \\ 43 \\ \hline 14 \end{array}$$

Ex: $(101011)_2$ from $(111001)_2$ (1's complement of 0111001)

$(101011)_2$ from $(0111001)_2$

$$\begin{array}{r} 2^6 2^5 2^4 2^3 2^2 2^1 2^0 \\ \hline 1 & 1 & 0 & 1 & 0 & 1 & 1 \\ \hline 107 & & & & & & \end{array}$$

$\rightarrow 0111001$

L - 5

$$\begin{array}{r} 1 & 1 & 0 & 1 & 0 & 1 & 1 \\ 1 & 0 & 0 & 0 & 1 & 1 & 0 \\ \hline 1 & 1 & 1 & 1 & 1 & 0 & 1 \end{array}$$

① $\begin{array}{r} 0 & 1 & 1 & 0 & 0 & 1 \\ + 1 & & & & & \\ \hline 0 & 1 & 1 & 0 & 0 & 1 \end{array}$

↓ 1's complement of 0111001

$$\begin{array}{r}
 011000 \\
 + 1 \\
 \hline
 0110010
 \end{array}$$

$$\begin{array}{r}
 107 \\
 - 57 \\
 \hline
 50
 \end{array}$$

(0110010)

$$= 50_{10}$$

$+ \bar{C} =$

(ii) subtraction of large number from smaller number:

Steps: S-2

1. Determine the 1's complement of the larger number
2. Add the 1's complement of the smaller number
3. Answer is in 1's complement form, to get the answer in true form take the 1's complement and assign (ve) sign to the answer.

Ex: subtract $(111001)_2$ from $(101011)_2$ using the 1's complement

method : $(111001)_2$ from $(101011)_2$ using 1's complement

$$\begin{array}{r}
 101011 \\
 + 000110 \leftarrow 1's \text{ complement} \\
 \hline
 110001 \rightarrow 1's \text{ complement}
 \end{array}$$

101011
~~000110~~ - 14 1010110 ①

Ex: $(1111101)_2$ from $(1101011)_2$

$$\begin{array}{r} 2^6 2^5 2^4 2^3 2^2 2^1 2^0 \\ \hline 1101011 \\ - 1111101 \\ \hline 125 \end{array}$$

(a)

S-2

$$\begin{array}{r} 1101011 \\ 0000010 \rightarrow 1's \text{ complement of } (1111101) \\ \hline 1101101 \\ - 0010000 \rightarrow 1's \text{ complement} \\ \hline -18 \end{array}$$

(b)

2-S

$$\begin{array}{r} 1111101 \\ 0000000 \leftarrow 1's \\ \hline 1111101 \\ 0000000 \\ \hline 0010010 \end{array}$$

$$= 18-11$$

from GATE question

(i) subtraction of smaller number from larger number:

- Determine the 2's complement of a small number
- Add the 2's complement to the large number
- Discard the carry (or) remove the carry

Ex: subtract $(10101)_2$ from $(111001)_2$

$\begin{array}{r} 11 \\ 57 \\ \hline 2^8 \text{ complement} \end{array}$

(a) L - S

$$\begin{array}{r} 111001 \\ 010100 \\ \hline 001110 \end{array}$$

remove

$$\begin{array}{r} 101011 \\ 010100 \rightarrow 2^8 \text{ complement} \\ \hline 010010 \\ 2^8 \text{ complement} \\ 0110001 \\ 000110 \rightarrow 1^8 \\ \hline 000111 \end{array}$$

(ii) S - L

$$\begin{array}{r} 101011 \\ 000111 \\ \hline 110010 \\ 110010 \end{array}$$

$$\begin{array}{r} 001000 \\ 001010 \\ \hline 000110 \end{array}$$

(iii) subtraction of larger number from smaller number:

- Determine the 2's complement of the large number
- Add the 2's complement to the smaller one
- Answer is in the 2's complement form to get the answer in the true form to take the 2's complement

ANSWER IN THE TRUE FORM TO TAKE THE 2'S COMPLEMENT


add assign (-ve) sign to the answer

t.me/jntukonlinebits

Signed binary numbers:

→ The sign magnitude formate for 8 bit signed number is

given by

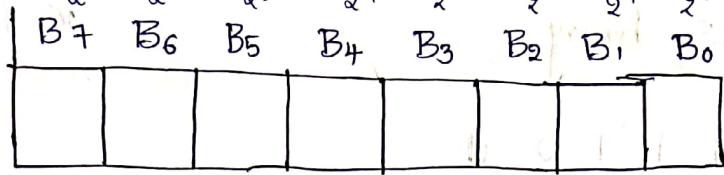

$$\text{Ex: } 1) +6 = 0000 \quad 0110$$

$$2) -14 = 1000 \quad 1110$$

$$3) +24 = 0001 \quad 1000$$

$$4) -64 = 1100 \quad 0000$$

$$5) +127 = 0111 \quad 1111$$

$$6) -128 = 1111 \quad 1111$$

→ The maximum (+ve) number +127 = 0111 1111

Binary Arithmetic

Rules for binary addition:

| A | B | Sum | Carry |
|---|---|-----|-------|
| 0 | 0 | 0 | 0 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 1 |

From

$O = (A - B)$

From

$O = (B - A)$

From

$O = (A + B)$

Ex: Add $(1010)_2$ & $(0111)_2$

www.jntukonlinebits.com
t.me/jntukonlinebits

1 0 1 0

0 0 1 1

1 1 0 1

Ex: Add 28 and 15 binary.

$$\begin{array}{r}
 1 1 1 0 0 \\
 0 1 1 1 1 \\
 \hline
 1 0 1 0 0
 \end{array}$$

$$\begin{array}{r}
 28 \\
 15 \\
 \hline
 43
 \end{array}$$

Ex: B.

Binary subtraction

| A | B | Difference | Barrow |
|---|---|------------|--------|
| 0 | 0 | 0 | 0 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 0 |

Ex: Subtract $(0101)_2$ from $(1011)_2$

$$\begin{array}{r}
 1 0 1 1 \\
 0 1 0 1 \\
 \hline
 0 1 1 0
 \end{array}$$

Hexa Decimal Arithmetic

$$① 9_{16} + 3_{16} = C_{16}$$

$$② 9_{16} + 7_{16} = (16 - 16) = 0 \text{ carry } 1$$

$$③ A_{16} + 8_{16} = (18 - 16) = 2 \text{ carry } 1$$

① Add $(3F8)_{16}$ and $(5B3)_{16}$

Add $\begin{array}{r} 3 \ F \ 8 \\ + 5 \ B \ 3 \\ \hline (9 \ A \ B)_{16} \end{array}$

② Add Hexadecimal numbers $(2FB)_{16}$, $(75D)_{16}$, $(A12)_{16}$

$(C39)_{16}$ is 16 less than $(D5A)_{16}$

$35 = (35 - 16) = 19$ carry 1
 $= (19 - 16) = 3$ carry 2

$26 = (26 - 16) = 10$ carry 1

$34 = (34 - 16) = 18$ carry 1
 $= (18 - 16) = 2$ carry 2

$$\begin{array}{r} & 7 & 5 & D \\ & A & 1 & 2 \\ C & 3 & 9 \\ \hline & 2 & 2 & A \end{array}$$

Subtraction with 15's complement

→ The 15's complement of a hexadecimal number is formed by subtracting each digit from 15

Ex: find 15's complement of $(A9B)_{16}$

$$15 \ 15 \ 15$$

$$(\rightarrow A \ 9 \ B)$$

Ex: Use the 15's complement method of subtraction to compute $(B02)_{16} - (98F)_{16}$

$$(B02)_{16} - (98F)_{16}$$

(+) Adding

(1)
$$\begin{array}{r} 6 \ 7 \ 8 \\ + 9 \ 8 \ F \\ \hline 1 \ 7 \ 3 \end{array}$$

(2)
$$\begin{array}{r} 15 \ 15 \ 15 \\ - 9 \ 8 \ F \\ \hline 6 \ 7 \ 0 \end{array}$$

Subtraction of 15's complement

t.me/jntukonlinebits

- find 15's complement of substrand
- Add to Hexadecimal numbers (1st number and 15's complement of 2nd number)
- If carry produced. In the addition, add carry to the least significant bit of the sum, otherwise find 15's complement of the sum as a result with a (-ve) sign.

Ex: Use the 15's complement method of subtraction to

Compute $(69B)_{16} - (C14)_{16}$

Step 1: 15 15 15
(+) C I 4
—————
3 E B

Step 2: 6 9 B
(+) 3 E B
—————
A 8 6

Step 3: 8 15 15 15
- A 8 6
—————
- 5 7 9

$\therefore (69B)_{16} - (C14)_{16} = (-579)_{16}$

Subtraction of 16's complement

- The 16's complement of a hexadecimal number is found by subtracting each digit from 15, and add 1.

Steps: steps for Hexadecimal subtraction using 16's complement

method.

- find 16's complement of substrand
- Add to Hexadecimal numbers (1st number & 16's complement of the 2nd number)

→ If carry 9's produced in the addition it is discarded or removed, otherwise find 16's complement of the sum as a result with a (-ve) sign

Ex: Find the 16's complement of $(A8C)_{16}$

$$\begin{array}{r}
 15 \quad 15 \quad 15 \leftarrow 15^{\text{'}}\text{s complement} \\
 - A \quad 8 \quad C \\
 \hline
 5 \quad 7 \quad 3 \\
 + 1 \\
 \hline
 5 \quad 7 \quad 4
 \end{array}$$

2. Use the 16's complement method of subtraction to compute

$$(C\text{E}B2)_{16} - (972)_{16}$$

Step 1:

$$\begin{array}{r}
 15 \quad 15 \quad 15 \leftarrow 15^{\text{'}}\text{s} \\
 - 9 \quad 7 \quad 8 \\
 \hline
 6 \quad 8 \quad D \\
 + 1 \\
 \hline
 6 \quad 8 \quad E \leftarrow 16^{\text{'}}\text{s complement}
 \end{array}$$

$$\begin{aligned}
 (16-16) &= 1 \text{ carry} \\
 (20-16) &= 4 \text{ carry} \\
 (18-16) &= 3 \text{ carry}
 \end{aligned}$$

Step 2:

$$\begin{array}{r}
 \overline{C \text{ E} B} \quad 2 \\
 + 6 \quad 8 \quad E \\
 \hline
 3 \quad 4 \quad 1
 \end{array}$$

3. Use the 16's complement method of subtraction to compute

$$(387)_{16} - (854)_{16}$$

Step 1:

$$\begin{array}{r}
 15 \quad 15 \quad 15 \\
 - 8 \quad 5 \quad 4 \\
 \hline
 7 \quad A \quad B \\
 + 1 \\
 \hline
 7 \quad A \quad C \leftarrow 16^{\text{'}}\text{s complement}
 \end{array}$$

Step 2: $(3B7)_{16} - (854)_{16}$

(+) 7 A C

$$\begin{array}{r} \\ \hline B & 6 & 3 \end{array}$$


Step 3: If NO carry

$$\begin{array}{r} 15 & 15 & 15 \\ - B & 6 & 3 \\ \hline 4 & 9 & C \\ & & 1 \end{array}$$

Step 4: $(-49D)_{16}$

$$\therefore (3B7)_{16} - (854)_{16} = (-49D)_{16}$$

Binary codes:

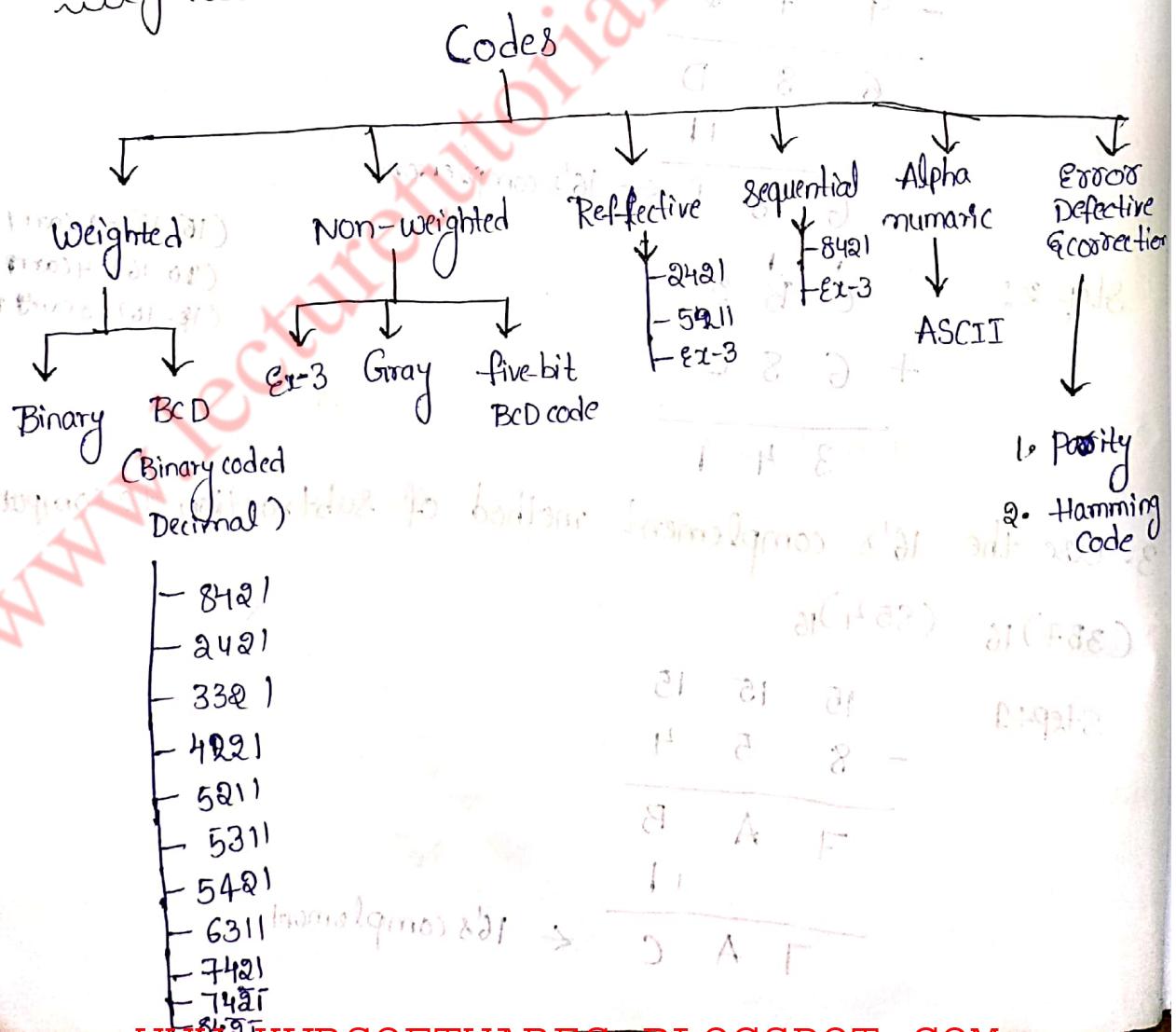

Excess Code (E_2-3)

t.me/jntukohlinebits

| Decimal | $-E_2-3$ | Binary code |
|---------|----------|-------------|
| 0 | $0+3=3$ | 0011 |
| 1 | 4 | 0100 |
| 2 | 5 | 0101 |
| 3 | 6 | 0110 |
| 4 | 7 | 0111 |

* To find binary code and Gray code of the given binary number is 1101010101

truth table of Hexa X-OR Gate

$$\begin{array}{ccc} A & \oplus & B \\ \downarrow & \oplus & \downarrow \\ C = AB + \bar{A}B \\ = A \oplus B \end{array}$$

| A | B | C = A \oplus B |
|---|---|------------------|
| 0 | 0 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 0 |

binary-gray

① $\begin{smallmatrix} \oplus & \oplus & \oplus & \oplus & \oplus & \oplus & \oplus \\ \downarrow & \downarrow & \downarrow & \downarrow & \downarrow & \downarrow & \downarrow \\ 1101010101 \end{smallmatrix}$

$\downarrow \downarrow \downarrow \downarrow \downarrow \downarrow \downarrow$

1011111110

∴ 1011111110

gray-binary

P-1-8-HA-23

$\begin{array}{ccccccccc} 1 & 1 & 0 & 1 & 0 & 1 & 0 & 1 & 0 \\ \downarrow & \oplus & \downarrow & \oplus & \downarrow & \oplus & \downarrow & \oplus & \downarrow \\ 1 & 0 & 0 & 1 & 1 & 0 & 0 & 1 & 0 \end{array}$

$\therefore 1001100110$

① BCD Addition

t.me/jntukonlinebits

Ex: BCD of 58

$$\begin{array}{r} 5 \\ \downarrow \\ 0101 \end{array} \quad \begin{array}{r} 8 \\ \downarrow \\ 1000 \end{array}$$

(i) Sum equals "9" or less with carry 0

Ex: Add 3 and 6 in BCD

$$\begin{array}{r} 3 \\ + 6 \\ \hline 9 \end{array} \quad \begin{array}{r} 0011 \\ 0110 \\ \hline 1000 \end{array} \rightarrow \text{Ans}$$

(ii) Add sum > 9 with carry 0

Ex: Add 6 and 8

$$\begin{array}{r} 6 \\ + 8 \\ \hline 14 \end{array} \quad \begin{array}{r} 0110 \\ 1000 \\ \hline 1110 \end{array} \rightarrow 14$$

↓ ↓ ↓

0110 ← Add 6

① 11

0001 0100

14 → BCD

(iii) Sum equals to 9 or less with carry 1

Ex: Add 8 + 9

$$\begin{array}{r} 8 \\ + 9 \\ \hline 17 \end{array} \quad \begin{array}{r} 1000 \\ 1001 \\ \hline 00010001 \end{array} \leftarrow \text{Invalid BCD}$$

↓ ↓ ↓

0110

00010111

17

* Perform each of the following decimal addition in 84181 BCD
t.me/jntukonlinebits

① $24 + 18$

$$\begin{array}{r} 24 \\ - 18 \\ \hline 42 \end{array}$$

$$\begin{array}{r} 0010 \\ 0100 \\ \hline 00011000 \end{array}$$

$$\begin{array}{r} 00011000 \\ \text{carry } 0 \ 110 \leftarrow \text{Add 6} \\ \hline 000100110010 \end{array}$$

$$\begin{array}{r} 000100110010 \\ \text{valid BCD} \end{array}$$

② $48 + 58$

$$\begin{array}{r} 48 \\ - 58 \\ \hline 106 \end{array}$$

$$\begin{array}{r} 0100 \\ 01011000 \\ 01001000 \\ \hline 10010000 \end{array}$$

$$\begin{array}{r} 0100 \\ \text{Add 6} \\ \hline 10100000 \\ 0110 \end{array}$$

$$\begin{array}{r} 10100000 \\ \text{Add 6} \\ \hline 10100110 \end{array}$$

③ $175 + 326$

$$\begin{array}{r} 175 \\ - 326 \\ \hline 501 \end{array}$$

$$\begin{array}{r} 000101110101 \\ 001100100110 \\ \hline 010010011011 \end{array}$$

$$\begin{array}{r} 010010011011 \\ \text{Add 6} \\ \hline 000100011010 \end{array}$$

$$\begin{array}{r}
 & 1010 \leftarrow \text{Add 6} \\
 \textcircled{1} & 0110 \\
 \hline
 & 0000
 \end{array}$$

$$\begin{array}{r}
 & 0101 \leftarrow \text{Add 6} \\
 \textcircled{2} & 0101 \\
 \hline
 & 0001
 \end{array}$$

(4) $589 + 199$

$$\begin{array}{r}
 589 \\
 199 \\
 \hline
 788
 \end{array}
 \quad
 \begin{array}{r}
 0101 1000 1001 \\
 0001 1001 1001 \\
 \hline
 100100010010
 \end{array}$$

$$\begin{array}{r}
 0110 \leftarrow \text{Add 6} \\
 0001 \\
 \hline
 0110
 \end{array}$$

$$\begin{array}{r}
 0110 0010 0010 \\
 0001 \\
 \hline
 0110 \leftarrow \text{Add 6} \\
 11 \\
 \hline
 1000
 \end{array}$$

$$\begin{array}{r}
 0010 \\
 0110 \leftarrow \text{Add 6} \\
 \hline
 11 \\
 \hline
 1000
 \end{array}$$

$$\begin{array}{r}
 0111 1000 1000 \\
 7 8 8
 \end{array}$$

BCD Subtraction:

(9) subtraction with 9's complement

| | |
|---|---|
| <u>Digits</u> 0 1 2 3 4 5 6 7 | <u>9's complement</u> 9 8 7 6 5 4 3 2 |
|---|---|

$$\begin{array}{r}
 1101 1010 \\
 0101 0010 \\
 \hline
 1000 1000
 \end{array}$$

Ans: 1000

Regular subtraction

$$\begin{array}{r} 8 \\ - 2 \\ \hline 6 \end{array}$$

$$\begin{array}{r} 8 \\ - 2 \\ \hline 6 \end{array}$$

9's complement subtraction

$$\begin{array}{r} 8 \\ - 2 \\ \hline 6 \end{array}$$

(9's complement of 2)

$$\begin{array}{r} 9 \\ - 5 \\ \hline 4 \end{array}$$

$$\begin{array}{r} 9 \\ - 5 \\ \hline 4 \end{array}$$

$$\begin{array}{r} 9 \\ - 5 \\ \hline 4 \end{array}$$

(9's complement of 5)
Result is negative

$$\begin{array}{r} 4 \\ - 1 \\ \hline 3 \end{array}$$

(9's complement
of result no)

Carry indicates

that the answer
is negative and
completed from)

* perform each of the following decimal subtraction in
8421 BCD using 9's complement method.

$$79 - 26$$

$$\begin{array}{r} 79 \\ - 26 \\ \hline 53 \end{array}$$

$$\begin{array}{r} 0111 \quad 1001 \\ 0111 \quad 0011 \xleftarrow{\text{(9's complement of 26)}} \\ \hline 1110 \quad 1100 \\ 0110 \xleftarrow{\text{Add 6}} \end{array}$$

$$\begin{array}{r} [7-2=7] \\ [6-2=3] \end{array}$$

$$\begin{array}{r} 1110 \quad 0010 \\ \hline 0101 \quad 0011 \end{array}$$

Add 6

10's complement

$$\textcircled{a} \quad \begin{array}{r} 8 \\ - 8 \\ \hline 0 \end{array}$$

$$\begin{array}{r} 8 \\ 8 \\ \hline \cancel{16} \end{array}$$

remove 10

\rightarrow 10's complement ($10-2=8$)

$$\textcircled{b} \quad \begin{array}{r} 9 \\ - 5 \\ \hline 4 \end{array}$$

$$\begin{array}{r} 9 \\ 5 \\ \hline \cancel{14} \end{array}$$

remove 10

\rightarrow 10's complement ($10-5=5$)

$$\textcircled{c} \quad \begin{array}{r} 4 \\ - 8 \\ \hline -4 \end{array}$$

$$\begin{array}{r} 4 \\ 2 \\ \hline \cancel{6} \end{array}$$

\rightarrow 10's complement of ($10-8=2$)

Result no carry indicate
that the answer is (-ve)
and in the 10's complement
form (or) incomplete form

(most significant bit)

on the left side of the

absolute value)

Consider all bits

from right to left

(most significant bit)

if there is a dot then add

possible values of all 10 bits are less than 1000

absolute complement of 1000 is 1111

1111 - 1000

(as 10 four bits of p) \rightarrow 1111 1111

1001 1110

1111 1110

0011 0110

0000 1111

PF

OE

EF

Concept of Boolean Algebra

Introduction:

→ In 1854 George Boolean introduced a systematic treatment of logic and developed for this purpose of an algebraic system Now called Boolean Algebra.

→ In 1938 C.E. Shannon introduced a two-valued Boolean Algebra called a switching Algebra

Fundamental Postulates of Boolean Algebra

| S.NO | Postulates | Comments |
|------|--|---|
| 1. | → Result of each operator is either 0 or 1 | $1, 0 \in B$ |
| 2. | a) $0+0=0, 0+1=1, 1+0=1$ b) $1 \cdot 1 = 1; 0 \cdot 1 = 0, 1 \cdot 0 = 0$ | Identity element "0" for "+" and "1" for \cdot |
| 3. | a) $(A+B) = (B+A)$ b) $(A \cdot B) = (B \cdot A)$ | Commutative law |
| 4. | a) $A \cdot (B+C) = (A \cdot B) + (A \cdot C)$ b) $A + (B \cdot C) = (A + B) \cdot (A + C)$ | Distributive law |
| 5. | a) $A + \bar{A} = 1, 0 + \bar{0} = 1, 1 + \bar{1} = 1$ b) $A \cdot \bar{A} = 0, \text{ if } \bar{0} \cdot \bar{0} = 0 \cdot 1 = 0$ $1 \cdot \bar{1} = 1 \cdot 0 = 0$ | Complement |

$$[\bar{0} = 1]$$

$$\bar{1} = 0]$$

Basic theorems and properties

t.me/jntukonlinebits

Duality:

→ The principle of Duality theorem says that starting with a boolean relation, we can derive another boolean relation by

1. changing each "OR" sign to an "AND" sign

2. changing each "AND" sign to an "OR" sign

3. Any 0 or 1 operating in the expression of boolean

function.

Ex: Dual of relation $A + \bar{A} = 1$ is $A \cdot \bar{A} = 0$

$$A + \bar{A} = 1$$

$$A \cdot \bar{A} = 0$$

Theorems:

Laws of Boolean algebra:

Boolean Expression

$$\Rightarrow A + 1 = 1$$

$$A \cdot 0 = 0$$

$$\Rightarrow A + 0 = A$$

$$A \cdot 1 = A$$

$$\bar{\bar{A}} = A$$

$$\Rightarrow A + A = A$$

$$A \cdot A = A$$

$$\bar{A} + A = 1$$

$$\Rightarrow A = A$$

$$\bar{A} + \bar{A} = 0$$

B.A law (or) Rule

Annulation

Identity

Idempotent

Double Negation

Boolean Expression

BA Law (or) Rule
t.me/jntukonlinebits

$$\Rightarrow A + \bar{A} = 1$$

Complement

$$A \cdot \bar{A} = 0$$

Commutative law

$$\Rightarrow A + B = B + A$$

$$A \cdot B = B \cdot A$$

De-morgan

$$\Rightarrow \overline{A+B} = \bar{A} \cdot \bar{B}$$

$$\overline{AB} = \bar{A} + \bar{B}$$

Boolean Algebra functions

| Function | Description | Expression |
|----------|----------------|--|
| 1. | NULL | 0 |
| 2. | Identity | 1 |
| 3. | INPUT A | A |
| 4. | INPUT B | B |
| 5. | NOT A | \bar{A} |
| 6. | NOT B | \bar{B} |
| 7. | A AND B (AND) | $A \cdot B$ |
| 8. | A AND NOT B | $A \cdot \bar{B}$ |
| 9. | NOT A AND B | $\bar{A} \cdot B$ |
| 10. | NOT AND (NAND) | $\overline{A \cdot B}$ $A \cdot A = 0$ $A \cdot A \cdot A = 0$ |
| 11. | A OR B (OR) | $A + B$ $A + A \cdot B$ $A + \bar{B}$ |
| 12. | A OR NOT B | $A + \bar{B}$ |

| Function | Description | Expression |
|----------|-----------------------|---------------------------------|
| 13. | NOT A OR B (OR) | $A + B$ |
| 14. | NOT OR (NOR) | $\overline{A + B}$ |
| 15. | Exclusive OR (X-OR) | $AB + \overline{A}B$ |
| 16. | Exclusive NOR (X-NOR) | $\overline{AB + \overline{A}B}$ |

Theorems:

① a) $A + A = A$

b) $A \cdot A = A$

② a) $A + 1 = 1$

b) $A \cdot 0 = 0$

③ a) $\overline{\overline{A}} = A$

④ a) $A + AB = A$

b) $A(A+B) = A$

⑤ a) $A + \overline{A}B = A + B$

b) $A(\overline{A} + B) = AB$

① Proof:

L.H.S

$$\begin{aligned}
 A + A &= (A+A) \cdot (1) && \left\{ \begin{array}{l} \text{if } A=0; 0+0=0 \\ \text{if } A=1; 1+1=1 \end{array} \right. \\
 &= (A+A)(A+\overline{A}) && [1 = A+\overline{A}] \\
 &= AA + A\overline{A} + AA + A\overline{A} && [A+A = 1] \\
 &= AA + A\overline{A} && [AA = A] \\
 &= A(A+\overline{A}) && [A\overline{A} = 0] \\
 &= A // && [A = A]
 \end{aligned}$$

② Proof:

L.H.S

$$\begin{aligned}
 A \cdot A &= A \cdot A + (0) && \left\{ \begin{array}{l} A \cdot A = A \\ A = 0 \Rightarrow 0 \cdot 0 = 0 \\ A = 1 \Rightarrow 1 \cdot 1 = 1 \end{array} \right. \\
 &= A \cdot A + A \cdot \overline{A} && [A \cdot \overline{A} = 0] \\
 &= A(A+\overline{A}) && [A + \overline{A} = 1] \\
 &= A(A+1) && [A \cdot 1 = A] \\
 &= A // && [A = A]
 \end{aligned}$$

$$② @ A+1=1$$

t.me/jntukonlinebits

$$\begin{aligned} \text{Proof: } & A+1 = C(A+1) \\ & = (A+\bar{A})(A+1) \\ & = A \cdot A + A + \bar{A} \cdot A + \bar{A} \\ & = A + A + 0 + \bar{A} \\ & = A + A + \bar{A} \\ & = A + \bar{A} \\ & = 1 \end{aligned}$$

$$\begin{aligned} & [A \cdot \bar{A} = 0] \\ & [A + \bar{A} = 1] \end{aligned}$$

$$\neg A + 1 = 1$$

$$\left\{ \begin{array}{l} \text{if } A=0; 0+1=1 \\ A=1; 1+1=1 \end{array} \right.$$

$$(b) A \cdot 0 = 0$$

$$\begin{aligned} \text{Proof: } & A \cdot 0 = C(A \cdot \bar{A}) \\ & = A \cdot A + A \cdot \bar{A} \\ & = A(0) \\ & = 0 \end{aligned}$$

$$(3) \bar{\bar{A}} = A$$

$$\text{Proof: if } A=0; \bar{0} = \bar{1} = 0 \quad [\bar{0}=1, \bar{1}=0]$$

$$\therefore A=1; \bar{1} = \bar{0} = 1 \quad [A=1, 1 \cdot 1 = 1]$$

$$(4) @ A+AB=A$$

$$\begin{aligned} \text{Proof: } & A+AB = A(1+B) \quad [\because 1+B=1] \\ & = A(1) \\ & = A \end{aligned}$$

$$(b) A(A+B)=A$$

$$\text{Proof: } A(A+B) = (A+AB)(A+B)$$

$$\begin{aligned} & [0 \cdot A=0] \\ & = AA + AB + AB + AB \cdot B \\ & = A + AB + A \cdot AB + AB \\ & = A + AB + AB + AB \end{aligned}$$

$$= A(1+B) + AB$$

$$= A + AB$$

$$= A(1+B)$$

$$= A \text{ II}$$

(5)(a) $A + \bar{A}B = A + B$

proof: $A + \bar{A}B = (A + \bar{A})(A + B)$

$$= A + B \quad [\because A + \bar{A} = 1]$$

(b) $A(\bar{A} + B) = AB$

proof: $A(\bar{A} + B) = A \cdot \bar{A} + AB$

$$= 0 + AB$$

$$\text{Hence } A(\bar{A} + B) = AB$$

** De-Morgan's theorem:

(i) $\overline{AB} = \bar{A} + \bar{B}$

(ii) $\overline{A+B} = \bar{A} \cdot \bar{B}$

(iii) $\overline{\overline{AB}} = \overline{\bar{A} + \bar{B}}$

| A | B | \bar{A} | \bar{B} | \overline{AB} | $\bar{A} + \bar{B}$ |
|---|---|-----------|-----------|-----------------|---------------------|
| 0 | 0 | 1 | 1 | 1 | 1 |
| 0 | 1 | 1 | 0 | 1 | 1 |
| 1 | 0 | 0 | 1 | 1 | 1 |
| 1 | 1 | 0 | 0 | 0 | 0 |

(iv) $\overline{A+B} = \bar{A} \cdot \bar{B}$

| A | B | \bar{A} | \bar{B} | $\bar{A} \cdot \bar{B}$ | $\overline{A+B}$ |
|---|---|-----------|-----------|-------------------------|------------------|
| 0 | 0 | 1 | 1 | 1 | 1 |
| 0 | 1 | 1 | 0 | 0 | 0 |
| 1 | 0 | 0 | 1 | 0 | 0 |
| 1 | 1 | 0 | 0 | 0 | 0 |

→ Consensus theorem :-

→ In simplification of Boolean Expression, an expression of the form $AB + \bar{A}C + BC$. The term BC is redundant and can be eliminated to form the equivalent expression $AB + \bar{A}C$.

→ The theorem is used for this simplification is known as Consensus theorem. and it is stated as

$$AB + \bar{A}C + BC = AB + \bar{A}C$$

Proof :-

$$L.H.S \Rightarrow AB + \bar{A}C + BC = AB + \bar{A}C + BC(1)$$

$$= AB + \bar{A}C + BC(A + \bar{A})$$

$$= AB + \underline{\bar{A}C} + \underline{BCA} + \underline{BC\bar{A}}$$

$$= ABC(1+C) + \bar{A}C(1+B)$$

$$= AB + \bar{A}C$$

* Solve the given expression using Consensus theorem

$$(Q) \bar{A}\bar{B} + AC + B\bar{C} + \bar{B}C + AB$$

$$\Rightarrow \bar{A}\bar{B} + AC + B\bar{C} + \bar{B}C(1) + AB \quad [A + \bar{A} = 1]$$

$$\Rightarrow \bar{A}\bar{B} + AC + B\bar{C} + \bar{B}C(A + \bar{A}) + AB$$

$$\Rightarrow \underline{\bar{A}\bar{B}} + \underline{AC} + \underline{B\bar{C}} + \underline{\bar{B}CA} + \underline{\bar{B}C\bar{A}} + AB$$

$$\Rightarrow \bar{A}\bar{B}(1+C) + AC(1+\bar{B}) + B\bar{C} + AB \quad [HC = 1, 1+\bar{B} = 1]$$

$$\Rightarrow \bar{A}\bar{B} + AC + B\bar{C} + AB$$

$$\Rightarrow \bar{A}\bar{B} + AC + B\bar{C} + ABC(1)$$

$$\Rightarrow \bar{A}\bar{B} + AC + B\bar{C} + AB(C + \bar{C})$$

$$\Rightarrow \bar{A}\bar{B} + \underline{AC} + \underline{B\bar{C}} + AB\bar{C} + \underline{AB\bar{C}} \quad [1+B = 1]$$

$$\Rightarrow \bar{A}\bar{B} + AC(1+B) + B\bar{C}(1+A) \quad [1+A = 1]$$

$$\Rightarrow A\bar{B} + A\bar{C} + B\bar{C}$$

Dual of consensus theorem:

The Dual form of consensus theorem is stated as

$$(A+B)(\bar{A}+C)(B+C) = (A+B)(\bar{A}+C)$$

$$(A\bar{A} + A\bar{C} + \bar{A}B + BC)(B+C) = (A\bar{A} + A\bar{C} + \bar{A}B + BC)$$

$$(0 + A\bar{C} + \bar{A}B + BC)(B+C) = (0 + A\bar{C} + \bar{A}B + BC) \quad [A \cdot \bar{A} = 0]$$

$$ABC + \bar{A}B \cdot B + BC \cdot B + AC \cdot C + \bar{A}BC + BC \cdot C = AC + \bar{A}B + BC \quad [BC + BC = BC]$$

$$BC(A+B) + \bar{A}B(B+C)$$

$$ABC + \bar{A}B \cdot B + BC + AC + \bar{A}BC + BC = AC + \bar{A}B + BC$$

$$\bar{A}B(1+C) + BC(1+A) + AC = AC + \bar{A}B + BC$$

$$\boxed{\bar{A}B + BC + AC = AC + \bar{A}B + BC}$$

Boolean function (or) switching function:

Boolean equations are constructed by connecting the boolean constants and variables with the boolean operation.

This Boolean Expressions are known as boolean formulas we use

boolean expression to describe boolean functions.


for example: If Boolean Expression $(A+B)C$ is used to describe the function of f , then boolean function is written as, $f(A, B, C) = (A+B)C$

$$f = (A+B)C$$

Let us consider the whole four variable boolean function.


Product-terms:

$$f(A, B, C, D) = A + (BC) + (ACD)$$

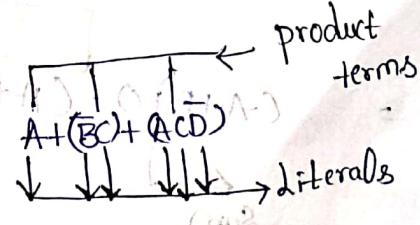

Sum-Terms:
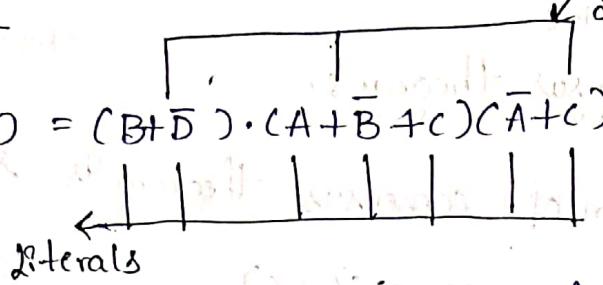
$$f(A, B, C, D) = (B + \bar{D}) \cdot (A + \bar{B} + C) \cdot (\bar{A} + C)$$



sum terms
t.me/jntukonlinebits

→ The literals and terms are arranged in the form of two rows.

1. sum of product (SOP)

2. product of sum (POS)

1. sum of products:

→ The sum of product is also called Disjunctive normal form (DNF).


Disjunctive normal formula

→ The words sum & product are described from the symbolic representation "OR" and "AND" function ($+$ and \cdot)

Ex-1

$$f(A, B, C) = AB\bar{C} + A\bar{B}\bar{C}$$

sum terms

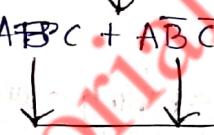

Ex-2

$$f(P, Q, R) = \bar{P}Q + Q\bar{R} + \bar{R}S$$

sum terms

products

2. Product of sum:

→ The product of sum is also called conjunctive normal form (CNF).

form (CNF) conjunctive normal formula.

→ A product of sum is any group of sum terms ANDed

together.

Ex-3

$$f(A, B, C) = (A + B + C) \cdot (\bar{A} + \bar{B} + \bar{C})$$

product

sum

$$f(P, Q, R) = (P+Q) \cdot (R+P) \cdot Q$$

t.me/jntukonlinebits

* Canonical form \Leftrightarrow (standard SOP and POS forms)

→ Basically Canonical forms are two types

1. Standard SOP (or) minterm Canonical form

2. Standard POS (or) maxterm Canonical form

1. Standard SOP \Leftrightarrow (minterm Canonical form)

$f(A, B, C) = (A\bar{B}C) + (\bar{A}BC) + (\bar{A}\bar{B}C)$

→ The SOP is given by
Each product term is consistent all literals in either completed form or uncompleted form

2. Standard POS \Leftrightarrow (maxterm)

$f(A, B, C) = (A+\bar{B}+C) \cdot (\bar{A}+B+C) \cdot (\bar{A}+\bar{B}+C)$

Each sum term consists of all literals in the completed form

* Converting SOP to standard SOP (or) POS form

Steps to convert SOP to standard SOP form

Step 1: find the missing literal in each product term if any

1. find the missing term having missing literals which term 1

2. "AND" each product term having missing literals and its complement

formed by "OR"ing the literals and its complement

3. Expand the terms by applying Distributive law and recorded

the literals in the product terms


4. Reduce the expression omitting (or) removing repeated product terms if any because $(A+A) = A$

Ex: Convert the given expression in standard SOP form
t.me/jntukonlinebits

$$f(A, B, C) = AC + AB + BC$$

Step 1: $f(A, B, C)$ = find the missing literal in each product

$$f(A, B, C) = AC + AB + BC$$

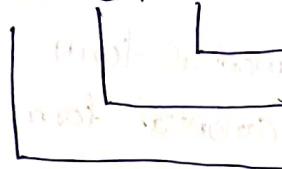

A literal is missing

C literal missing

B literal missing

Step 2: AND product terms with (missing literal + complement)

$$f(A, B, C) = AC(1) + AB(1) + BC(A + \bar{A})$$

$$[A + \bar{A} = 1]$$

$$B + \bar{B} = 1$$

$$C + \bar{C} = 1$$

$$= AC(B + \bar{B}) + AB(C + \bar{C}) + BC(A + \bar{A})$$

Step 3: Expand the term and recorded the terms

Expand :-

$$f(A, B, C) = ACB + A\bar{C}\bar{B} + ABC + AB\bar{C} + BCA + B\bar{C}A$$

Recorded :-

$$f(A, B, C) = ABC + A\bar{B}C + ABC + A\bar{B}\bar{C} + A\bar{B}C + \bar{A}BC$$

Step 4: omitting the repeated product term

$$f(A, B, C) = \underline{ABC} + \underline{A\bar{B}C} + \underline{ABC} + \underline{A\bar{B}\bar{C}} + \underline{A\bar{B}C} + \underline{\bar{A}BC}$$


$$f(A, B, C) = ABC + A\bar{B}C + A\bar{B}\bar{C} + \bar{A}BC$$

Ex: Convert the given expression in standard SOP form

$$f(A, B, C) = A + ABC$$

Step 1: find

$$f(A, B, C) = A + ABC$$

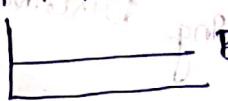

B literal missing

C literal missing

Step 2: AND product term with (missing literal + complement)

$$f(A, B, C) = AC(1) + ABC$$

$$= A(B + \bar{B})(C + \bar{C}) + ABC$$

Step 3:

$$f(A, B, C) = AB + \bar{A}\bar{B} (BC + \bar{B}C + \bar{B}\bar{C}) + ABC$$

t.me/jntukonlinebits

$$= \underline{ABC} + AB\bar{C} + A\bar{B}C + A\bar{B}\bar{C} + \underline{ABC}$$

Step 4: omitting the repeated product term

$$f(A, B, C) = ABC + AB\bar{C} + A\bar{B}C + A\bar{B}\bar{C}$$

Convert POS to standard POS form:

Step 5:

1. find the missing literals in each sum term if any.
2. OR each sum term having missing literal formed by ANDing the literal and its complement
3. Expand the terms by applying distributive law and recorded the literal in the sum terms
4. Reduce the Expression by omitting repeated sum term if any

$$A \cdot A = A$$

Ex: convert the given expression in standard POS form

$$f(A, B, C) = (A+B) \cdot (B+C) \cdot (A+C)$$

$$[A \cdot \bar{A} = 0]$$


$$[B \cdot \bar{B} = 0]$$

$$[C \cdot \bar{C} = 0]$$

Step 1: find the missing literal in each product

$$f(A, B, C) = (A+B) \cdot (B+C) \cdot (A+C)$$

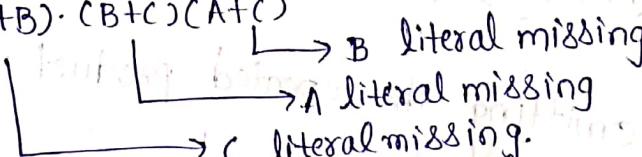[$A+(BC)=A$]
[$(A+B)(A+C)=A$]
[distribut]



Step 2: OR product term with (missing literal + complement)

$$f(A, B, C) = [(A+B) + (C \cdot \bar{C})] \cdot [(B+C) + (A \cdot \bar{A})] \cdot [(A+C) + (B \cdot \bar{B})]$$

Step 3: expand the term and recorded the terms

Expand:

$$f(A, B, C) = [(A+B+C) \cdot (A+B+\bar{C})] \cdot [(B+C+A) \cdot (B+C+\bar{A})] \cdot [(A+C+B) \cdot (A+C+\bar{B})]$$

Recorded:

$$f(A, B, C) = [\underline{A+B+C}] \cdot [\underline{A+B+\bar{C}}] \cdot [\underline{A+\bar{B}+C}] \cdot [\underline{\bar{A}+\bar{B}+\bar{C}}]$$

Step 4: omitting the repeated product term

$$f(A, B, C) = (A+B+C)(A+B+\bar{C})(A+\bar{B}+C)(\bar{A}+\bar{B}+\bar{C})$$

Ex: Convert the given expression in standard pos forms

$$f(A, B, C) = (A) \cdot (A+B+C)$$

Step 1: find the missing literal in each product

$$f(A, B, C) = A \cdot (A+B+C)$$

Step 2: B, C literals missing

Step 2: OR product term with (missing literal + complement)

$$f(A, B, C) = [A+(B \cdot \bar{B})](C \cdot \bar{C}) \cdot (A+B+C)$$

Step 3: Expand the term and recorded the terms

$$\text{Expand: } [A + (B+C) + (B\bar{C}) + (\bar{B}+C) + (\bar{B}\bar{C})] \cdot (A+B+C)$$

$$= (A+B+C) \cdot (A+B+\bar{C}) \cdot (A+\bar{B}+C) \cdot (A+\bar{B}+\bar{C})$$

Step 4: omitting the repeated product term

$$f(A, B, C) = (A+B+C) \cdot (A+B+\bar{C}) \cdot (A+\bar{B}+C) \cdot (A+\bar{B}+\bar{C})$$

$$= [(A+B+C) \cdot (A+B+\bar{C})] \cdot [(A+\bar{B}+C) \cdot (A+\bar{B}+\bar{C})]$$

$$= [(A+B+C) \cdot (A+B+\bar{C})] \cdot [(A+\bar{B}+C) \cdot (A+\bar{B}+\bar{C})]$$

$$= [(A+B+C) \cdot (A+B+\bar{C})] \cdot [(A+\bar{B}+C) \cdot (A+\bar{B}+\bar{C})]$$

M-Notations: (minterms and maxterms)

time/intukonlinebits

| Decimal No. | Binary Numbers (4x3) | Minterm (m) (SOP) | Maxterm (M) (POS) |
|-------------|-------------------------|---|---|
| 0 | 000 | $\bar{A}\bar{B}\bar{C}$ (m ₀) | A + B + C (M ₀) |
| 1 | 001 | $\bar{A}\bar{B}C$ (m ₁) | A + B + \bar{C} (M ₁) |
| 2 | 010 | $\bar{A}B\bar{C}$ (m ₂) | A + \bar{B} + C (M ₂) |
| 3 | 011 | $\bar{A}BC$ (m ₃) | A + \bar{B} + \bar{C} (M ₃) |
| 4 | 100 | A $\bar{B}\bar{C}$ (m ₄) | \bar{A} + B + C (M ₄) |
| 5 | 101 | A $\bar{B}C$ (m ₅) | \bar{A} + B + \bar{C} (M ₅) |
| 6 | 110 | A B \bar{C} (m ₆) | \bar{A} + \bar{B} + C (M ₆) |
| 7 | 111 | A B C (m ₇) | \bar{A} + \bar{B} + \bar{C} (M ₇) |

On one bit

Minterm = Complement of maxterm

$$\begin{aligned} \text{Example: } f(A, B, C) &= \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + \bar{A}BC + ABC \\ &= m_0 + m_1 + m_3 + m_6 \\ &= \sum m(0, 1, 3, 6) \end{aligned}$$

$$\begin{aligned} \text{Ex: } f(A, B, C) &= (A + B + \bar{C}) \cdot (\bar{A} + \bar{B} + \bar{C}) \cdot (\bar{A} + \bar{B} + C) \\ &= M_1 \cdot M_3 \cdot M_6 \\ &= \prod M(1, 3, 6) \end{aligned}$$

To find sum of product form to the given table

| A B C | y |
|-------|---|
| 0 0 0 | 0 |
| 0 0 1 | 0 |
| 0 1 0 | 1 |
| 0 1 1 | 1 |
| 1 0 0 | 0 |

[ABC] 98 a
input variables
[SOP, k9 1'8]

| A · B · C | y |
|-----------|---|
| 0 0 1 | 1 |
| 1 1 0 | 1 |
| 1 1 1 | 0 |

$$f(A, B, C) = \overline{A}B\overline{C} + \overline{A}B\overline{C} + A\overline{B}\overline{C}$$

$$= m_2 + m_3 + m_6$$

$$= \sum m(2, 3, 6)$$

To find the product of sum from the given table.

[Product of
sum is zero's]

| A + B + C | y |
|-----------|---|
| 0 0 0 | 1 |
| 0 0 1 | 1 |
| 0 1 0 | 0 |
| 0 1 1 | 1 |
| 1 0 0 | 1 |
| 1 0 1 | 0 |
| 1 1 0 | 1 |
| 1 1 1 | 1 |

$$f(A, B, C) = (A + \overline{B} + \overline{C}) \cdot (\overline{A} + B + \overline{C})$$

[Adding 9 & 0]

$$= M_2 \cdot M_5$$

$$= \Pi M(2, 5)$$

| | | |
|---|---|---|
| 0 | 0 | 0 |
| 0 | 0 | 0 |
| 1 | 0 | 0 |
| 0 | 1 | 0 |
| 1 | 1 | 0 |
| 0 | 0 | 1 |

Algebraic Simplifications

t.me/jntukonlinebits

1. $A \cdot \bar{A}C = 0$
2. $ABCD + ABD = ABD$
3. $A(A+B) = A$
4. $AB + ABC + ABC(D+E) = AB$
5. $XY + XYZ + XY\bar{Z} + \bar{X}YZ$
6. $\bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C$
7. $ABC + A\bar{B}C + ABC$
8. $A + \bar{A}B + A\bar{B} = A+B$

$$\text{Ex: } \overline{\bar{A}\bar{B} + \bar{A} + AB}$$

$$\Rightarrow \overline{\bar{A} + \bar{B} + \bar{A} + AB}$$

$$\Rightarrow \overline{\bar{A} + \bar{B} + AB}$$

$$\Rightarrow \overline{\bar{A} + (\bar{B}+A) \cdot (B+\bar{B})}$$

$$\Rightarrow \overline{\bar{A} + \bar{B} + A \cdot (1)}$$

$$\Rightarrow \overline{(A+\bar{A}) + \bar{B}}$$

$$\Rightarrow \overline{1 + \bar{B}}$$

$$[\bar{A}\bar{B} = \bar{A} + \bar{B}]$$

$$[\bar{B} + (AB) = \bar{B}A + (B \cdot B)]$$

$$= [(\bar{B}+A) \cdot (\bar{B}+\bar{B})]$$

$$[\bar{B} + B = 1]$$

$$[\bar{1} = 0]$$

$$\textcircled{1} \quad A \cdot \bar{A}C = 0$$

$$(A \cdot \bar{A})C = 0$$

$$(0)C = 0$$

$$A \cdot \bar{A}C = 0$$

$$\overline{\bar{A}\bar{B} + \bar{A} + AB}$$

$$\overline{\bar{A} + \bar{B} + AB}$$

$$\overline{A + AB + B\bar{B}}$$

$$\overline{A + AB}$$

$$\overline{A + \bar{B}}$$

$$\overline{B = (\bar{A}+A) \cdot (A+\bar{B})}$$

$$\overline{B = \frac{1}{1+B}}$$

$$\textcircled{2} \quad ABCD + ABD = ABD$$

$$\Rightarrow ABD(1+C)$$

$$\Rightarrow ABD$$

$$\Rightarrow ABCD + ABD = ABD$$

$$\textcircled{3} \quad A(A+B) = A$$

$$\Rightarrow A \cdot A + AB$$

$$\Rightarrow A + AB$$

$$\Rightarrow A(1+B)$$

$$\Rightarrow A$$

$$\textcircled{4} \quad AB + ABC + ABC(D+E) = AB$$

$$\Rightarrow AB + ABC + AB(D + BE)$$

$$\Rightarrow AB(1+C) + ABD + ABE$$

$$\Rightarrow AB + ABC(D+E)$$

$$\Rightarrow AB(1+D+E)$$

$$\Rightarrow AB[(1+D)+E]$$

$$\Rightarrow AB[1+E]$$

$$\Rightarrow ABC(1)$$

$$\Rightarrow AB$$

$$5. xy + x\bar{y}z + x\bar{y}\bar{z} + \bar{x}yz = y(x+z)$$

$$\Rightarrow xy(1) + x\bar{y}z + x\bar{y}\bar{z} + \bar{x}yz$$

$$\Rightarrow xy(1+\bar{z}) + x\bar{y}z + x\bar{y}\bar{z} + \bar{x}yz$$

$$\Rightarrow xy\bar{z} + x\bar{y}z + x\bar{y}\bar{z} + \bar{x}yz$$

$$\Rightarrow xy(z+\bar{z}) + xy(\bar{z}+\bar{z}) + \bar{x}yz$$

$$[H \cdot C = 1]$$

$$\Rightarrow xy + \bar{x}y + \bar{x}yz$$

$$\Rightarrow xy + \bar{x}yz$$

$$\Rightarrow y(x + \bar{x}z) \Rightarrow y((x+\bar{x}) \cdot (x+z)) \Rightarrow y(1) \cdot (x+z)$$

$$\Rightarrow y(x+z) //$$

$$\textcircled{6} \quad A\bar{B}\bar{C} + \bar{A}\bar{B}\bar{C} + \bar{A}B\bar{C}$$

$$\Rightarrow \bar{A}\bar{B}\bar{C} + \bar{A}B\bar{C} + \bar{A}B\bar{C}$$

$$\Rightarrow \bar{A}\bar{B}\bar{C} + \bar{A}B(\bar{C}+C)$$

$$\Rightarrow \bar{A}\bar{B}\bar{C} + \bar{A}B$$

$$\Rightarrow \bar{A}C(\bar{B}\bar{C} + B)$$

$$\Rightarrow \bar{A}((\bar{B}+B) \cdot (\bar{C}+B))$$

$$\Rightarrow \bar{A}(1 \cdot (\bar{C}+B))$$

$$\Rightarrow \bar{A}(\bar{C}+B)$$

$$\Rightarrow \bar{A}\bar{C} + \bar{A}B$$

$$\textcircled{7} \quad ABC + A\bar{B}C + A\bar{B}\bar{C}$$

$$ABC + A\bar{B}C + A\bar{B}\bar{C}$$

$$AC(C+B) + A\bar{B}\bar{C}$$

$$AC + AB\bar{C}$$

$$AC(C+B\bar{C})$$

$$AC((C+B) \cdot (C+\bar{C}))$$

$$AC(C+B)$$

$$AC(C+B) = AC(A+A) = A(C+A) = A$$

$$AC(A+B) = AC(A \cdot A + A \cdot B) = AC(A + AB) = AC(A(1+B)) = AC(A)$$

$$8. A + \bar{A}B + A\bar{B} = A+B$$

t.me/jntukonlinebits

$$\Rightarrow A + \bar{A}B + A\bar{B}$$

$$\Rightarrow A(1 + \bar{B}) + \bar{A}B$$

$$\Rightarrow A(1) + \bar{A}B$$

$$\Rightarrow A + \bar{A}B$$

$$\Rightarrow (A + \bar{A})(A + B)$$

$$\Rightarrow (1)(A + B)$$

$$\Rightarrow A + B //$$

Ex: Simplify the following three variable Expression by using Boolean algebra

$$Y = \Sigma m(1, 3, 5, 7)$$

$$\text{Given Data } Y = \Sigma m(1, 3, 5, 7) \\ = m_1 + m_3 + m_5 + m_7$$

$$= \bar{A}\bar{B}C + \bar{A}BC + A\bar{B}C + ABC$$

$$= \bar{A}C(\bar{B} + B) + AC(\bar{B} + B)$$

$$= \bar{A}C(1) + AC(1)$$

$$= C\bar{A} + A$$

$$= C //$$

Ex: Simplify the following three variable Expression by using Boolean algebra

$$Y = \prod M(1, 3, 5, 7)$$

$$\text{Given that } Y = \prod M(1, 3, 5, 7)$$

$$= M_1 \cdot M_3 \cdot M_5 \cdot M_7$$

$$= (A + B + \bar{C})(A + \bar{B} + \bar{C})(\bar{A} + B + \bar{C})(\bar{A} + \bar{B} + C)$$

$$= [A \cdot A + (A \cdot \bar{B}) + (A \cdot \bar{C}) + (B \cdot A) + (B \cdot \bar{B}) + (B \cdot \bar{C}) + (\bar{C} \cdot A) + (\bar{C} \cdot \bar{B}) + (\bar{C} \cdot \bar{C})] \cdot$$

$$[(\bar{A} \cdot \bar{A}) + (\bar{A} \cdot B) + (\bar{A} \cdot \bar{C}) + (B \cdot A) + (B \cdot \bar{B}) + (B \cdot \bar{C}) + (\bar{C} \cdot \bar{A}) +$$

$$[(\bar{B} \cdot \bar{C}) + (\bar{C} \cdot \bar{C})]$$

$$= ABC + A\bar{B}\bar{C} + A\bar{C} + \bar{A}\bar{B}\bar{C} + ABC + A\bar{B}\bar{C} + A\bar{C} + AB\bar{C} + A\bar{B}\bar{C} + \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}\bar{C}$$

$$BC + \bar{A}\bar{B}\bar{C} + B\bar{C} + ABC + A\bar{B}\bar{C} + AC + \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}\bar{C} + A\bar{B}\bar{C} + \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}\bar{C}$$

$$+ B\bar{C} + \bar{A}\bar{C} + \bar{A}\bar{B}\bar{C} + A\bar{C} + \bar{A}\bar{B} + B\bar{C} + \bar{A}\bar{C} + \bar{B}\bar{C} + \bar{C}$$

$$= ABC + A\bar{B}\bar{C} + A\bar{C} + \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}\bar{C} + BC + \bar{A}\bar{B}\bar{C} + B\bar{C} + \bar{A}\bar{C} + \bar{A}\bar{B} + \bar{C}$$

$$= BC(A + \bar{A}) + \bar{B}\bar{C}(HA) + \bar{C}(A + \bar{A}) + \bar{A}\bar{B}(HC) + \bar{C}(HB) + \bar{A}\bar{B}\bar{C}$$

$$= BC + \bar{B}\bar{C} + \bar{C} + \bar{A}\bar{B} + \bar{C} + \bar{A}\bar{B}\bar{C}$$

$$= \bar{A}\bar{B} + \bar{A}\bar{B}\bar{C} + \bar{C} //$$

Ex-2 Simplify the following three variable expression. Convert the expression into minterm complementary form.

$$y = \Pi_M(1, 3, 5, 7)$$

Sol: The given expression is maxterm $y = \Pi_M(1, 3, 5, 7)$.

To convert given sequences to minterm complementary form

minterm = Complementary of Maxterm

The minterm is given by $= \Sigma_m(0, 2, 4, 6)$

$$y = \Sigma_m(0, 2, 4, 6) = \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}\bar{C}$$

$$= m_0 + m_2 + m_4 + m_6 = \bar{A}\bar{C}(B + \bar{B}) + \bar{A}\bar{C}(B + \bar{B})$$

$$= \bar{A}\bar{C}(B + \bar{B}) + \bar{A}\bar{C}(B + \bar{B}) = \bar{A}\bar{C}$$

$$= \bar{A}\bar{C} + \bar{A}\bar{C} = \bar{C}(A + \bar{A})$$

$$= \bar{C}(A + \bar{A}) = \bar{C} //$$

(M) * transform each of the following Canonical expression into its other Canonical form & its decimal notations.

$$(q) f(x, y, z) = \Sigma_m(1, 3, 5)$$

$$(q) f(x, y, z) = \Pi_M(0, 2, 5, 6, 7, 8, 9, 11, 12)$$

$$(q) f(x, y, z) = \Sigma_m(1, 3, 5)$$

$$f(x, y, z) = \Pi_M(0, 2, 4, 6, 7)$$

$$= M_0 \cdot M_2 \cdot M_4 \cdot M_6 \cdot M_7 (x + y + z) \cdot (x + \bar{y} + z) \cdot (\bar{x} + y + z) \cdot (\bar{x} + \bar{y} + z) \cdot (\bar{x} + \bar{y} + \bar{z})$$

$$= (x + y + z) \cdot (A\bar{B} + \bar{C}) \cdot (A + B + C) \cdot (\bar{A} + B + C) \cdot (\bar{A} + \bar{B} + \bar{C})$$

$$f(\omega, x, y, z) = \overline{IM}(0, 2, 5, 6, 7, 8, 9, 11, 12)$$

$$f(w, x, y, z) = \text{PI}_N(0, 8, 15, 6, 7, 8, 9, 11, 12)$$

$$= \sum m(1, 3, 4, \cancel{10}, 14, 15)$$

$$= m_1 + m_3 + m_4 + m_{10} + m_{13} + m_{14} + m_{15}$$

$$= \bar{w}\bar{x} + \bar{z}y\bar{w} + \bar{z}y\bar{x}w + z\bar{y}x\bar{w} + z\bar{y}\bar{x}\bar{w} + z\bar{y}xw$$

$$= \bar{w}x\bar{z}(y\bar{z}+y) + wxz(y\cdot 1) + wy\bar{z}(x+\bar{x}) + \bar{w}x\bar{y}\bar{z}$$

$$= \bar{\omega} \bar{x} z + \omega x z + \omega y \bar{z} + \bar{\omega} x \bar{y} \bar{z}$$

| Decimal NO | Binary number | minterm t.m.e/jntukonlinebits | Maxterm |
|------------|---------------|----------------------------------|---|
| 8 | 1000 | $A \bar{B} \bar{C} \bar{D}$ | $\bar{A} + \bar{B} + \bar{C} + \bar{D}$ |
| 9 | 1001 | $A \bar{B} \bar{C} D$ | $\bar{A} + \bar{B} + \bar{C} + D$ |
| 10 | 1010 | $A \bar{B} C \bar{D}$ | $\bar{A} + B + \bar{C} + D$ |
| 11 | 1011 | $A \bar{B} C D$ | $\bar{A} + B + \bar{C} + \bar{D}$ |
| 12 | 1100 | $A B \bar{C} \bar{D}$ | $\bar{A} + \bar{B} + C + \bar{D}$ |
| 13 | 1101 | $A B \bar{C} D$ | $\bar{A} + \bar{B} + C + D$ |
| 14 | 1110 | $A B C \bar{D}$ | $\bar{A} + \bar{B} + \bar{C} + \bar{D}$ |
| 15 | 1111 | $A B C D$ | $\bar{A} + \bar{B} + \bar{C} + D$ |

UNIT-III

t.me/jntukonlinebits

Gate - Level Minimization

Map :-

→ The map method gives us a systematic approach for simplifying a boolean expression. The map method first proposed by Veitch and modified by Karnaugh, hence it is known as the Veitch-Karnaugh diagram or the Karnaugh map (K-map).

One-variable, two-variable, three variable and four variable

Maps :-

$$1 \text{ Variable} = 2^1 = 2 \text{ cells}$$



$$2 \text{ Variable} = 2^2 = 4 \text{ cells}$$

$$3 \text{ Variable} = 2^3 = 8 \text{ cells}$$


$$4 \text{ Variable} = 2^4 = 16 \text{ cells}$$

$$\begin{aligned}1 \text{ Var} &= 2^1 = 2 \text{ cells} \\2 \text{ Var} &= 2^2 = 4 \text{ cells} \\3 \text{ Var} &= 2^3 = 8 \text{ cells} \\4 \text{ Var} &= 2^4 = 16 \text{ cells}\end{aligned}$$

1 Variable K-Map :-

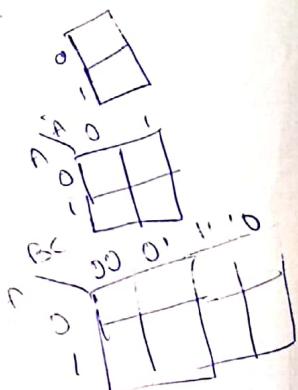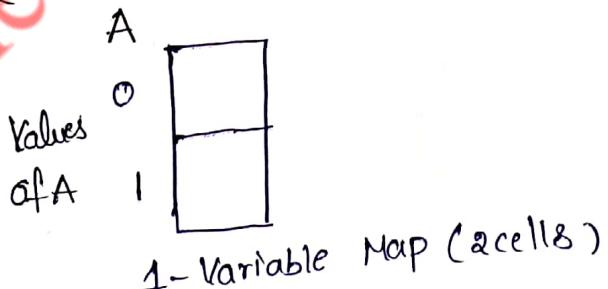

2-Variable K-Map :-

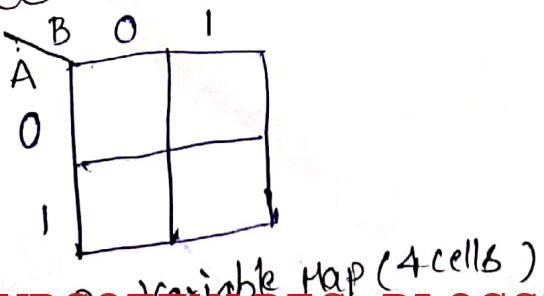

3-variable K-map

t.me/jntukonlinebits

| | BC | 00 | 01 | 11 | 10 |
|---|----|----|----|----|----|
| A | 0 | | | | |
| | 1 | | | | |

3-variable K-map (8 cells)

4-variable K-map

| | CD | 00 | 01 | 11 | 10 |
|----|----|----|----|----|----|
| AB | 00 | | | | |
| | 01 | | | | |

Values of CD

in gray code

4-variable K-map (16 cells)

1-variable

| | | |
|---|-----------|-------------|
| 0 | \bar{A} | $\bar{A} 0$ |
| 1 | A | $A 1$ |

2-variable

| | B | \bar{B} | B |
|---|---|-------------------|-------------|
| A | 0 | $\bar{A} \bar{B}$ | $\bar{A} B$ |
| | 1 | $A \bar{B}$ | $A B$ |

3-variable

| | BC | $\bar{B}\bar{C}$ | $\bar{B}C$ | BC | $B\bar{C}$ |
|---|----|-------------------------|-------------------|-------------------|-------------------|
| A | 0 | $\bar{A}\bar{B}\bar{C}$ | $\bar{A}\bar{B}C$ | $\bar{A}B\bar{C}$ | $\bar{A}B\bar{C}$ |
| | 1 | $A\bar{B}\bar{C}$ | $A\bar{B}C$ | ABC | $A\bar{B}C$ |

4-variable

| $\bar{A}\bar{B}$ | $\bar{C}\bar{D}$ | $\bar{C}D$ | $C\bar{D}$ | CD |
|------------------|--------------------------------------|--------------------------------------|--------------------------|--------------------------|
| $\bar{A}B$ | $\bar{A}\bar{B}\bar{C}\bar{D}$ 0 | $\bar{A}B\bar{C}\bar{D}$ 1 | $A\bar{B}C\bar{D}$ 3 | $AB\bar{C}\bar{D}$ 2 |
| $\bar{A}B$ | $\bar{A}BC\bar{D}$ 4 | $\bar{A}B\bar{C}\bar{D}$ 5 | $\bar{A}BCD$ 7 | $AB\bar{C}\bar{D}$ 6 |
| AB | $\bar{A}\bar{B}\bar{C}\bar{D}$ 12 | $\bar{A}\bar{B}\bar{C}\bar{D}$ 13 | $\bar{A}BCD$ 15 | $ABC\bar{D}$ 14 |
| $A\bar{B}$ | $\bar{A}BC\bar{D}$ 8 | $\bar{A}\bar{B}\bar{C}\bar{D}$ 9 | $AB\bar{C}\bar{D}$ 11 | $AB\bar{C}\bar{D}$ 10 |

Representation of Truth table on k-map

two-variable k-map

→ The representation of two variable truth table on k-map is given below

| A | B | y |
|---|---|---|
| 0 | 0 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 0 |

| A | B | 0 | 1 |
|---|---|---|---|
| 0 | 0 | 0 | 1 |
| 1 | 1 | 1 | 0 |

| A | B | 0 | 1 |
|---|---|---|---|
| 0 | 0 | 1 | 0 |
| 1 | 1 | 0 | 0 |

| A | B | 0 | 1 |
|---|---|---|---|
| 0 | 0 | 1 | 0 |
| 1 | 1 | 0 | 0 |

Three-variable k-map

| A | B | C | y |
|---|---|---|---|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 1 |
| 1 | 0 | 1 | 1 |
| 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 1 |

| A | BC | 00 | 01 | 11 | 10 |
|---|----|----|----|----|----|
| 0 | 0 | 0 | 0 | 0 | 1 |
| 1 | 1 | 1 | 1 | 0 | 0 |

| A | BC | 00 | 01 | 11 | 10 |
|---|----|----|----|----|----|
| 0 | 0 | 0 | 1 | 1 | 2 |
| 1 | 1 | 1 | 1 | 0 | 0 |

four-variable K-maps

t.me/jntukonlinebits

| A | B | C | D | y |
|---|---|---|---|---|
| 0 | 0 | 0 | 0 | 1 |
| 0 | 0 | 0 | 1 | 0 |
| 0 | 0 | 1 | 0 | 0 |
| 0 | 0 | 1 | 1 | 1 |
| 0 | 1 | 0 | 0 | 1 |
| 0 | 1 | 0 | 1 | 1 |
| 0 | 1 | 1 | 0 | 0 |
| 0 | 1 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 1 | 0 |
| 1 | 0 | 1 | 0 | 1 |
| 1 | 0 | 1 | 1 | 0 |
| 1 | 1 | 0 | 0 | 1 |
| 1 | 1 | 0 | 1 | 0 |
| 1 | 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 1 | 1 |

| AB | CD | 00 | 01 | 11 | 10 |
|------|------|----|----|----|----|
| 0000 | 0000 | 1 | 0 | 1 | 0 |
| 0001 | 0001 | 0 | 1 | 0 | 1 |
| 0011 | 0011 | 1 | 1 | 1 | 0 |
| 0010 | 0010 | 0 | 1 | 0 | 1 |
| 0101 | 0101 | 1 | 1 | 0 | 1 |
| 0111 | 0111 | 0 | 1 | 1 | 0 |
| 0100 | 0100 | 1 | 0 | 1 | 1 |
| 1101 | 1101 | 0 | 1 | 1 | 1 |
| 1111 | 1111 | 1 | 1 | 1 | 1 |
| 1100 | 1100 | 1 | 0 | 1 | 0 |
| 1011 | 1011 | 0 | 1 | 1 | 1 |
| 1000 | 1000 | 1 | 0 | 0 | 0 |
| 0110 | 0110 | 0 | 1 | 0 | 0 |
| 0100 | 0100 | 0 | 0 | 1 | 0 |
| 0010 | 0010 | 1 | 0 | 0 | 1 |
| 0001 | 0001 | 0 | 1 | 0 | 0 |
| 0011 | 0011 | 1 | 1 | 0 | 0 |
| 0000 | 0000 | 1 | 0 | 1 | 0 |
| 0001 | 0001 | 0 | 1 | 0 | 1 |
| 0011 | 0011 | 1 | 1 | 1 | 0 |
| 0010 | 0010 | 0 | 1 | 0 | 1 |
| 0101 | 0101 | 1 | 1 | 0 | 1 |
| 0111 | 0111 | 0 | 1 | 1 | 0 |
| 0100 | 0100 | 1 | 0 | 1 | 1 |
| 1101 | 1101 | 0 | 1 | 1 | 1 |
| 1111 | 1111 | 1 | 1 | 1 | 1 |
| 1100 | 1100 | 1 | 0 | 1 | 0 |
| 1011 | 1011 | 0 | 1 | 1 | 1 |
| 1000 | 1000 | 1 | 0 | 0 | 0 |
| 0110 | 0110 | 0 | 1 | 0 | 0 |
| 0100 | 0100 | 0 | 0 | 1 | 0 |
| 0010 | 0010 | 1 | 0 | 0 | 1 |
| 0001 | 0001 | 0 | 1 | 0 | 0 |
| 0011 | 0011 | 1 | 1 | 0 | 0 |
| 0000 | 0000 | 1 | 0 | 1 | 0 |
| 0001 | 0001 | 0 | 1 | 0 | 1 |
| 0011 | 0011 | 1 | 1 | 1 | 0 |
| 0010 | 0010 | 0 | 1 | 0 | 1 |
| 0101 | 0101 | 1 | 1 | 0 | 1 |
| 0111 | 0111 | 0 | 1 | 1 | 0 |
| 0100 | 0100 | 1 | 0 | 1 | 1 |
| 1101 | 1101 | 0 | 1 | 1 | 1 |
| 1111 | 1111 | 1 | 1 | 1 | 1 |
| 1100 | 1100 | 1 | 0 | 1 | 0 |
| 1011 | 1011 | 0 | 1 | 1 | 1 |
| 1000 | 1000 | 1 | 0 | 0 | 0 |
| 0110 | 0110 | 0 | 1 | 0 | 0 |
| 0100 | 0100 | 0 | 0 | 1 | 0 |
| 0010 | 0010 | 1 | 0 | 0 | 1 |
| 0001 | 0001 | 0 | 1 | 0 | 0 |
| 0011 | 0011 | 1 | 1 | 0 | 0 |

| CD | CD | CD | CD |
|------------|----|----|----|
| AB | 1 | 0 | 1 |
| $\bar{A}B$ | 0 | 1 | 3 |
| $\bar{A}B$ | 1 | 1 | 0 |
| AB | 4 | 5 | 7 |
| $\bar{A}B$ | 12 | 13 | 15 |
| AB | 0 | 0 | 1 |
| $\bar{A}B$ | 8 | 9 | 11 |

Plot Boolean Expression $y = ABC + ABC + \bar{A}\bar{B}C$ on the k-map

| A | B | C | y |
|---|---|---|---|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 0 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 1 |


| BC | 00 | 01 | 11 | 10 |
|----|----|----|----|----|
| 0 | 0 | 1 | 0 | 0 |
| 0 | 0 | 1 | 3 | 2 |
| 1 | 0 | 0 | 1 | 1 |
| 1 | 0 | 5 | 7 | 6 |

Ex: Plot Boolean expression $y = \overline{A}B\overline{C}\overline{D} + A\overline{B}C\overline{D} + \overline{A}BC\overline{D} + A\overline{B}CD + ABC\overline{D}$ on the K-map.

$$y = \overline{A}B\overline{C}\overline{D} + A\overline{B}C\overline{D} + \overline{A}BC\overline{D} + A\overline{B}CD + ABC\overline{D}$$

$$= 0100 + 1010 + 0110 + 1011 + 1101$$
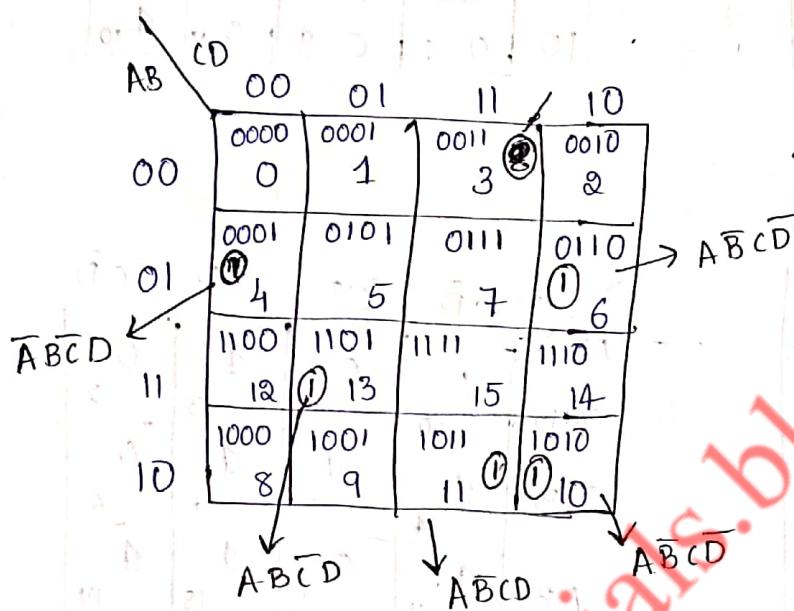
$$= m_4 + m_{10} + m_6 + m_{11} + m_{13}$$



Representation of standard pos on k-map

Three variable K-map

| A | B | C | Maxterm (M) |
|---|---|---|---|
| 0 | 0 | 0 | $\overline{A} + B + C$ (M_0) |
| 0 | 0 | 1 | $\overline{A} + B + \overline{C}$ (M_1) |
| 0 | 1 | 0 | $A + \overline{B} + C$ (M_2) |
| 0 | 1 | 1 | $A + \overline{B} + \overline{C}$ (M_3) |
| 1 | 0 | 0 | $\overline{A} + B + C$ (M_4) |
| 1 | 0 | 1 | $\overline{A} + B + \overline{C}$ (M_5) |
| 1 | 1 | 0 | $A + \overline{B} + C$ (M_6) |
| 1 | 1 | 1 | $A + \overline{B} + \overline{C}$ (M_7) |

Four Variable K-map

t.me/jntukohlinebits


| A | B | C | D | Maxterm (M) |
|---|---|---|---|--|
| 0 | 0 | 0 | 0 | $A+B+C+D \quad (M_0)$ |
| 0 | 0 | 0 | 1 | $A+B+C+\bar{D} \quad (M_1)$ |
| 0 | 0 | 1 | 0 | $A+B+\bar{C}+D \quad (M_2)$ |
| 0 | 0 | 1 | 1 | $A+B+\bar{C}+\bar{D} \quad (M_3)$ |
| 0 | 1 | 0 | 0 | $\bar{A}+\bar{B}+C+D \quad (M_4)$ |
| 0 | 1 | 0 | 1 | $\bar{A}+\bar{B}+C+\bar{D} \quad (M_5)$ |
| 0 | 1 | 1 | 0 | $\bar{A}+\bar{B}+\bar{C}+D \quad (M_6)$ |
| 0 | 1 | 1 | 1 | $\bar{A}+\bar{B}+\bar{C}+\bar{D} \quad (M_7)$ |
| 1 | 0 | 0 | 0 | $\bar{A}+\bar{B}+C+\bar{D} \quad (M_8)$ |
| 1 | 0 | 0 | 1 | $\bar{A}+\bar{B}+C+D \quad (M_9)$ |
| 1 | 0 | 1 | 0 | $\bar{A}+\bar{B}+\bar{C}+D \quad (M_{10})$ |
| 1 | 0 | 1 | 1 | $\bar{A}+\bar{B}+\bar{C}+\bar{D} \quad (M_{11})$ |
| 1 | 1 | 0 | 0 | $\bar{A}+\bar{B}+C+\bar{D} \quad (M_{12})$ |
| 1 | 1 | 0 | 1 | $\bar{A}+\bar{B}+C+D \quad (M_{13})$ |
| 1 | 1 | 1 | 0 | $\bar{A}+\bar{B}+\bar{C}+D \quad (M_{14})$ |
| 1 | 1 | 1 | 1 | $\bar{A}+\bar{B}+\bar{C}+\bar{D} \quad (M_{15})$ |

Ex:- plot Boolean Expression $y = (A+\bar{B}+C)(A+\bar{B}+\bar{C})(\bar{A}+\bar{B}+C)(\bar{A}+\bar{B}+\bar{C})$

on the K-map:

$$y = M_2 \cdot M_3 \cdot M_6 \cdot M_1$$

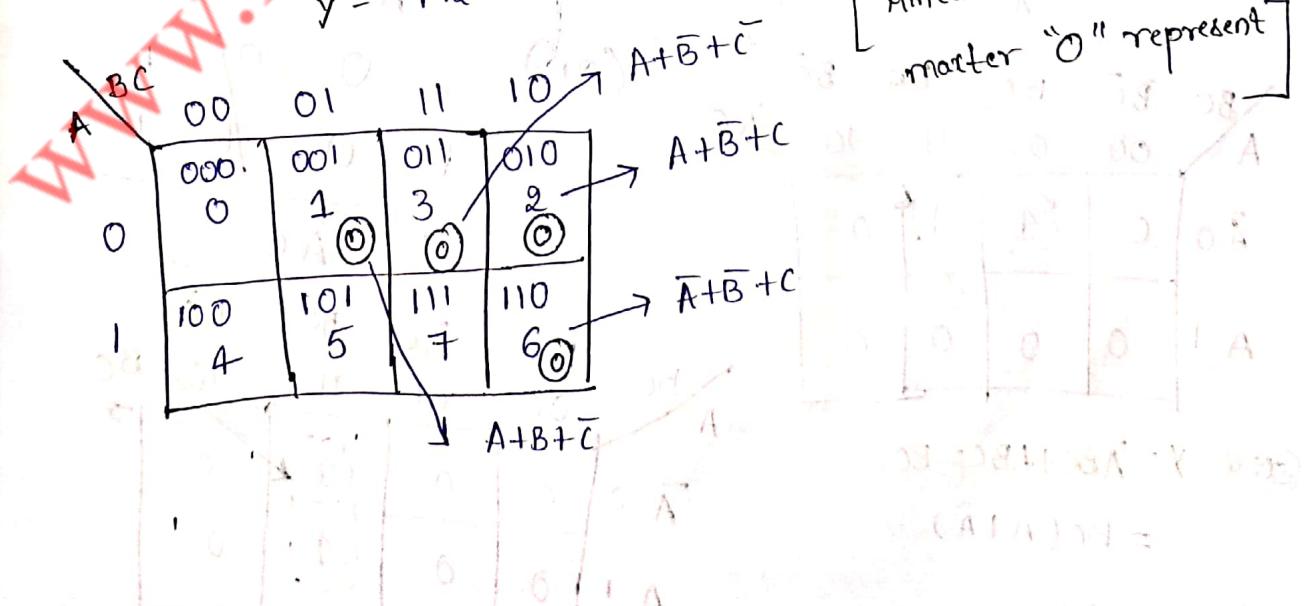Maxterm 1 "1" represent
Maxterm 0 "0" represent



Ex-5 plot Boolean Expression $y = (A+B+C+\bar{D})(A+\bar{B}+\bar{C}+D)(A+\bar{B}+\bar{C}+\bar{D})$
t.me/jntukonlinebits

$$(\bar{A}+\bar{B}+C+\bar{D})(\bar{A}+\bar{B}+\bar{C}+D)$$

$$Y = (A+B+C+\bar{D}) \cdot (\bar{A}+\bar{B}+\bar{C}+D) (\bar{A}+\bar{B}+\bar{C}+\bar{D}) (\bar{A}+\bar{B}+\bar{C}+D)$$

$$Y = M_1 \cdot M_6 \cdot M_3 \cdot M_{13} \cdot M_{14}$$

| | | CD | AB | 00 | 01 | 11 | 10 | |
|----|----|------|----|------|------|------|------|-------------------------------|
| | | CD | AB | 0000 | 0001 | 0011 | 0010 | $(A+B+C+\bar{D})$ |
| | | CD | AB | 00 | 01 | 11 | 10 | $A+\bar{B}+\bar{C}+D$ |
| 00 | 00 | 0000 | 0 | 4 | 0 | 3 | 2 | |
| 01 | 01 | 0100 | 4 | 5 | 7 | 6 | 0 | $(A+\bar{B}+\bar{C}+D)$ |
| 11 | 11 | 1100 | 12 | 13 | 15 | 14 | 0 | $(\bar{A}+\bar{B}+\bar{C}+D)$ |
| 10 | 10 | 1000 | 8 | 9 | 11 | 10 | 0 | $\bar{A}+\bar{B}+C+\bar{D}$ |

Grouping cells for simplification:

Grouping two adjacent ones (pair)

$$\text{Ex-6 } y = \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C \\ = \bar{A}C(\bar{B} + B) \\ = \bar{A}C$$

| | | BC | $\bar{B}\bar{C}$ | $\bar{B}C$ | $B\bar{C}$ | BC |
|------------|---|----|------------------|------------|------------|------|
| | | A | 00 | 01 | 11 | 10 |
| $\bar{A}0$ | 0 | 0 | 1 | 1 | 0 | 0 |
| A 1 | 1 | 0 | 0 | 0 | 0 | 0 |

(or)

$$\begin{array}{r} 0 \quad 0 / 1 \\ 0 \quad 1 / 1 \\ \hline \bar{A}C \end{array}$$

| | | BC | $\bar{B}\bar{C}$ | $\bar{B}C$ | $B\bar{C}$ | BC |
|------------|---|----|------------------|------------|------------|------|
| | | A | 00 | 01 | 11 | 10 |
| $\bar{A}0$ | 0 | 0 | 0 | 1 | 0 | 0 |
| A 1 | 1 | 0 | 0 | 0 | 1 | 0 |

$$\text{Ex-7 } Y = \bar{A}BC + ABC = BC \\ = BC(A + \bar{A}) \\ = BC$$

Scanned by CamScanner

$$\text{Ex: } ③ \quad Y = A\bar{B}\bar{C} + A\bar{B}C$$

$$= A\bar{C}(\bar{B} + B)$$

$$= A\bar{C}$$

| | $\bar{B}\bar{C}$ | $\bar{B}C$ | BC | $B\bar{C}$ |
|-----------|------------------|------------|------|------------|
| \bar{A} | 0 | 0 | 0 | 0 |
| A | 1 | 1 | 0 | 1 |

$$\text{Ex: } ④ \quad Y = \bar{A}\bar{B}\bar{C}D + A\bar{B}\bar{C}D$$

$$= \bar{B}\bar{C}D(A + \bar{A})$$

$$= \bar{B}\bar{C}D$$

| | $\bar{C}\bar{D}$ | $\bar{C}D$ | CD | $C\bar{D}$ |
|------------------|------------------|------------|------|------------|
| $\bar{A}\bar{B}$ | 00 | 01 | 11 | 10 |
| $\bar{A}B$ | 00 | 10 | 10 | 00 |
| $A\bar{B}$ | 10 | 00 | 00 | 00 |
| AB | 11 | 11 | 00 | 00 |

$$\text{Ex: } ⑤ \quad Y = \bar{A}\bar{B}C + \bar{A}BC + ABC$$

$$= \bar{A}\bar{B}C + \bar{A}BC + \bar{ABC} + ABC$$

$$= \bar{A}C(\bar{B} + B) + BC(\bar{A} + A)$$

$$= \bar{A}C + BC$$

| | $\bar{B}\bar{C}$ | $\bar{B}C$ | BC | $B\bar{C}$ |
|-----------|------------------|------------|------|------------|
| \bar{A} | 0 | 1 | 1 | 0 |
| A | 0 | 0 | 1 | 0 |

A B C

[OR]

Grouping four adjacent ones (quad)

| | $\bar{B}\bar{C}$ | $\bar{B}C$ | BC | $B\bar{C}$ |
|-----------|------------------|------------|------|------------|
| \bar{A} | 00 | 01 | 11 | 10 |
| A | 0 | 0 | 0 | 0 |

| | | |
|---|----|---|
| 0 | 10 | 0 |
| 0 | 0 | 0 |

Ex-2

t.me/jntukonlinebits

| AB | CD | $\bar{C}D$ | CD | $C\bar{D}$ |
|------------------|----|------------|----|------------|
| $\bar{A}\bar{B}$ | 00 | 01 | 11 | 10 |
| 00 | 0 | 0 | 1 | 0 |
| 01 | 0 | 0 | 1 | 0 |
| 11 | 0 | 0 | 1 | 0 |
| 10 | 0 | 0 | 1 | 0 |

② $y = CD$

Ex-3

| AB | CD | $\bar{C}D$ | CD | $C\bar{D}$ | $\bar{C}\bar{D}$ |
|------------------|----|------------|----|------------|------------------|
| $\bar{A}\bar{B}$ | 00 | 01 | 11 | 10 | 00 |
| 00 | 0 | 0 | 1 | 1 | 0 |
| 01 | 0 | 1 | 1 | 1 | 0 |
| 11 | 0 | 1 | 1 | 1 | 0 |
| 10 | 0 | 0 | 0 | 0 | 0 |

③ $y = BD$

Ex-4

| AB | CD | $\bar{C}D$ | CD | $C\bar{D}$ | $\bar{C}\bar{D}$ |
|------------------|----|------------|----|------------|------------------|
| $\bar{A}\bar{B}$ | 00 | 01 | 11 | 10 | 00 |
| 00 | 0 | 0 | 0 | 0 | 0 |
| 01 | 0 | 0 | 0 | 0 | 0 |
| 11 | 1 | 0 | 0 | 1 | 1 |
| 10 | 1 | 0 | 0 | 1 | 1 |

$y = \bar{AD}$

Ex-5

| AB | CD | $\bar{B}\bar{D}$ | $\bar{B}D$ | $B\bar{D}$ | BD |
|------------------|----|------------------|------------|------------|------|
| $\bar{A}\bar{B}$ | 00 | 1 | 0 | 0 | 1 |
| $\bar{A}B$ | 01 | 0 | 0 | 0 | 0 |
| $A\bar{B}$ | 11 | 0 | 0 | 0 | 0 |
| AB | 10 | 1 | 0 | 0 | 1 |

Ans: $y = \bar{B}\bar{D}$

Ex-6

| AB | CD | $\bar{C}\bar{D}$ | $\bar{C}D$ | $C\bar{D}$ | CD |
|------------------|----|------------------|------------|------------|------|
| $\bar{A}\bar{B}$ | 00 | 0 | 0 | 0 | 0 |
| $\bar{A}B$ | 01 | 0 | 0 | 0 | 0 |
| $A\bar{B}$ | 11 | 1 | 1 | 1 | 1 |
| AB | 10 | 0 | 1 | 1 | 1 |

Group 1 \rightarrow AB
Group 2 \rightarrow AD
Group 3 \rightarrow AC

(b) $y = AB + AD + AC$

Grouping eight adjacent ones (Octet)

| AB | CD | $\bar{C}\bar{D}$ | $\bar{C}D$ | $C\bar{D}$ | CD |
|------------------|----|------------------|------------|------------|------|
| $\bar{A}\bar{B}$ | 00 | 0 | 0 | 0 | 0 |
| $\bar{A}B$ | 01 | 1 | 1 | 1 | 1 |
| $A\bar{B}$ | 11 | 1 | 1 | 1 | 1 |
| AB | 10 | 0 | 0 | 0 | 0 |

(a) $y = B$

| AB | CD | $\bar{C}\bar{D}$ | $\bar{C}D$ | $C\bar{D}$ | CD |
|------------------|----|------------------|------------|------------|------|
| $\bar{A}\bar{B}$ | 00 | 0 | 1 | 1 | 0 |
| $\bar{A}B$ | 01 | 0 | 1 | 1 | 0 |
| $A\bar{B}$ | 11 | 0 | 1 | 1 | 0 |
| AB | 10 | 0 | 1 | 1 | 0 |

(b) $y = D$

| \bar{AB} | \bar{CD} | \bar{CD} | \bar{CD} | \bar{CD} | \bar{CD} |
|------------|------------|------------|------------|------------|------------|
| \bar{AB} | 00 | 01 | 11 | 10 | |
| \bar{AB} | 00 | 11 | 11 | 11 | |
| \bar{AB} | 01 | 0 | 0 | 0 | |
| \bar{AB} | 11 | 0 | 0 | 0 | |
| \bar{AB} | 10 | 1 | 1 | 1 | |

tme/jntukonlinebits

| \bar{AB} | \bar{CD} | \bar{CD} | \bar{CD} | \bar{CD} | \bar{CD} |
|------------|------------|------------|------------|------------|------------|
| \bar{AB} | 00 | 01 | 11 | 10 | |
| \bar{AB} | 00 | 0 | 0 | 11 | |
| \bar{AB} | 01 | 11 | 0 | 0 | |
| \bar{AB} | 11 | 11 | 0 | 0 | |
| \bar{AB} | 10 | 11 | 0 | 11 | |

| A | B | C | D |
|---|---|---|---|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 0 | 1 |
| 0 | 0 | 1 | 1 |
| 0 | 0 | 1 | 0 |
| 1 | 0 | 0 | 0 |
| 0 | 0 | 0 | 1 |
| 0 | 0 | 1 | 1 |
| 1 | 0 | 1 | 0 |

\bar{B}

| A | B | C | D |
|---|---|---|---|
| 0 | 0 | 0 | 0 |
| 0 | 1 | 0 | 0 |
| 1 | 1 | 0 | 0 |
| 0 | 0 | 1 | 0 |
| 0 | 0 | 1 | 1 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 1 | 0 |

Simplifications of SOP Expressions

→ from the above discussion we can outline generalized procedure to simplify Boolean Expressions as follows:

1. plot the k-map and place 1's in those cells corresponding to the 1's in the truth table or sum of product expression; place 0's in other cells.

2. check the k-map for adjacent 1's and encircle those 1's which are not adjacent to any other 1's; these are called isolated 1's.

3. check for those 1's which are adjacent to only one other 1 and encircle such pairs.

t.me/jntukonlinebits

4. check for quads and octets of adjacent 1's even if it contains some 1's that have already been encircled. while doing this make sure that there are minimum no. of groups.

5. combine any pairs necessary to include any 1's that have not yet been grouped.

6. From the simplified expression by summing product terms of all groups.

Ex: minimize the expression $Y = A\bar{B}C + \bar{A}\bar{B}C + A\bar{B}C + A\bar{B}\bar{C} + \bar{A}\bar{B}\bar{C}$

$$\begin{aligned} Y &= 101 + 001 + 011 + 100 + 000 \\ &= m_5 + m_1 + m_3 + m_6 + m_0 \\ &= \sum m(5, 3, 4, 0) \end{aligned}$$

Step 1: The k-map for three variables and its ploted according to the given expression.

| | | $\bar{B}\bar{C}$ | $\bar{B}C$ | BC | $B\bar{C}$ |
|------------|---|------------------|------------|------------|------------|
| | | 00 | 01 | 11 | 10 |
| $A\bar{B}$ | 0 | 000 ① 0 | 001 ① 1 | 011 ① 3 | 010 2 |
| | 1 | 100 ① 4 | 101 ① 5 | 111 7 | 110 6 |
| A | 0 | 000 ① 0 | 001 ① 1 | 011 ① 3 | 010 2 |
| | 1 | 100 ① 4 | 101 ① 5 | 111 7 | 110 6 |

Step 2: There are no isolated 1's

Step 3: 1 in the cell 3 adjacent only to 1 in the cell 4. This pair is combined and referred to as group 1

Step 4: There are no octet, but there are a quad cells 0, 1, 4 and 5 from a quad.

This quad is combined and referred to as a group.

Step 5: All ~~the~~ have already been grouped

| | | $\bar{B}\bar{C}$ | $\bar{B}C$ | BC | $B\bar{C}$ |
|------------|---|------------------|------------|----------|------------|
| | | 00 | 01 | 11 | 10 |
| $A\bar{B}$ | 0 | 000 1 | 001 1 | 011 1 | 010 0 |
| | 1 | 100 1 | 101 1 | 111 0 | 110 0 |
| A | 0 | 000 1 | 001 1 | 011 1 | 010 0 |
| | 1 | 100 1 | 101 1 | 111 0 | 110 0 |

Step 6: Each group generates a term

In Expression for y . In group 1 B Variable
is eliminated and in group 2 Variables
A and C are eliminated and we get

$$y = \overline{A}C + \overline{B}$$

| | BC | $\overline{B}\overline{C}$ | $\overline{B}C$ | BC | $B\overline{C}$ | |
|---|----|----------------------------|-----------------|----|-----------------|----|
| A | 00 | 01 | 11 | 10 | 01 | AC |
| B | 1 | 1 | 1 | 0 | 0 | |
| 1 | 1 | 1 | 1 | 0 | 0 | |
| 1 | 1 | 1 | 1 | 0 | 0 | |
| 1 | 1 | 1 | 1 | 0 | 0 | |
| 1 | 1 | 1 | 1 | 0 | 0 | |
| 1 | 1 | 1 | 1 | 0 | 0 | |

Ex: minimize the Expression

$$y = \overline{A}B\overline{C}\overline{D} + \overline{A}B\overline{C}D + A\overline{B}\overline{C}\overline{D} + A\overline{B}\overline{C}D + A\overline{B}C\overline{D}$$

$$= 0100 + 0101 + 1100 + 1101 + 1001 + 0010$$

$$= m_4 + m_5 + m_9 + m_{13} + m_7 + m_2$$

$$= \sum m(4, 5, 9, 13, 7, 2)$$

| | | CD | $\overline{C}\overline{D}$ | $\overline{C}D$ | CD | $C\overline{D}$ | $C\overline{D}$ | Group ③ |
|--|--|----------------------------|----------------------------|-----------------|----|-----------------|-----------------|---------|
| | | AB | 00 | 01 | 11 | 10 | 00 | Group ① |
| | | $\overline{A}\overline{B}$ | 00 | 01 | 11 | 10 | 11 | Group ② |
| | | 00 | 0 | 1 | 3 | 2 | 1 | |
| | | 01 | 4 | 5 | 7 | 6 | 0 | |
| | | 11 | 18 | 13 | 15 | 14 | 1 | |
| | | 10 | 8 | 9 | 11 | 10 | 0 | |

| G ₁ | | | | G ₂ | | | | G ₃ | | | |
|----------------|---|---|---|----------------|---|---|---|----------------|---|---|---|
| A | B | C | D | A | B | C | D | A | B | C | D |
| 0 | 1 | 0 | 0 | 1 | 0 | 0 | 0 | 1 | 1 | 0 | 1 |
| 0 | 1 | 0 | 1 | 1 | 0 | 0 | 1 | 1 | 0 | 0 | 1 |
| 1 | 1 | 0 | 0 | 1 | 1 | 0 | 1 | 0 | 1 | 0 | 1 |
| 1 | 1 | 0 | 1 | 1 | 1 | 0 | 0 | 0 | 1 | 0 | 0 |

$$y = \overline{A}\overline{B}C\overline{D} + A\overline{C}D + B\overline{C}$$

* Simplify the logic function specified by the truth table by using the Karnaugh map method. y is the output variable and A, B and C are the input variables.

| A | B | C | y |
|---|---|---|---|
| 0 | 0 | 0 | 1 |
| 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 0 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 1 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 1 |

$$Y = \bar{A}\bar{B}C + \bar{A}B\bar{C} + A\bar{B}\bar{C} + ABC$$

$$\begin{aligned} &= m_0 + m_3 + m_4 + m_7 \\ &= \sum m(0, 3, 4, 7) \end{aligned}$$

| | | BC | | A |
|---|---|------------------|------------------|---|
| | | 00 | 10 | |
| A | 0 | 0 4 4 1 | 1 1 5 7 | |
| | 1 | 2 3 6 7 | 1 1 6 7 | |

| Group 1 | | Group 2 | |
|------------------------------------|-----|------------------------|-----|
| 0/0 | 0/0 | 0/0 | 1/1 |
| 0/0 | 1/1 | 1/1 | 1/1 |
| <u>$\bar{B}\bar{C}$</u> | | <u>BC</u> | |

$$\therefore Y = \bar{B}\bar{C} + BC$$

Ex: Reduce the following function using K-map technique.

$$f(A, B, C, D) = \sum m(0, 1, 4, 8, 9, 10)$$

$$= m_0 + m_1 + m_4 + m_8 + m_9 + m_{10}$$

$$= \bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}\bar{C}D + \bar{A}\bar{B}C\bar{D} + A\bar{B}\bar{C}\bar{D} + A\bar{B}\bar{C}D + A\bar{B}C\bar{D}$$

| AB\CD | 00 | 01 | 11 | 10 |
|-------|----|----|----|----|
| 00 | 0 | 1 | 3 | 2 |
| 01 | 4 | 5 | 7 | 6 |
| 11 | 12 | 13 | 15 | 14 |
| 10 | 8 | 9 | 11 | 10 |

Group 2

Group 3

Group 1

Group 1

Group 2

t.me/jntukonlinebits

$$\begin{array}{l} A \quad B \quad C \quad D \\ \hline 1 & 0 & 0 & 0 \\ 1 & 0 & 0 & 0 \\ \hline \end{array}$$

$A \bar{B} \bar{D}$

$$\begin{array}{l} A \quad B \quad C \quad D \\ \hline 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 1 \\ 1 & 0 & 0 & 0 \\ 1 & 0 & 0 & 1 \\ \hline \end{array}$$

$\bar{B} \bar{C}$

$$\begin{array}{l} A \quad B \quad C \quad D \\ \hline 0 & 1 & 0 & 0 \\ \bar{A} \quad B \quad \bar{C} \quad D \\ \hline \end{array}$$

Group 3

Product of sum simplification:

1. plot the k-map and place 0s in those cells corresponding to the 0s in the truth table or minterms in the product of sum expression.
 2. check the k-map for adjacent 0s and encircle those 0s which are not adjacent to any other 0s. These are called isolated 0s.
 3. check for those 0s which are adjacent to only one other 0 and encircle such pairs.
 4. check for quads and octets of adjacent 0s even if it contains some 0s that have already been encircled. while doing this make sure that there are minimum no. of groups.
 5. Combine any pairs necessary to include any 0s that have not yet been grouped.
 6. From the simplified pos expression for F by taking product of sum terms of all the groups.
- To get familiar with these steps we will solve some Examples.

Ex: minimize the Expression

$$y = (A+B+\bar{C})(A+\bar{B}+\bar{C})(\bar{A}+\bar{B}+C)(\bar{A}+B+C)(A+B+C)$$

$$= (\cancel{001})(\cancel{011})$$

$$= (A+B+\bar{C}) = M_1$$

$$(A+\bar{B}+\bar{C}) = M_3$$

$$(A+\bar{B}+\bar{C}) = M_7$$

$$(A+B+C) = M_0$$

$$(\bar{A}+B+C) = M_4$$

Step 1: (a) shows the k-map for three variables A, B, C and minterms plotted according to given minterms.

| | BC | 00 | 01 | 11 | 10 |
|---|----|----|----|----|----|
| A | 0 | 0 | 0 | 0 | 0 |
| C | 0 | 4 | 5 | 7 | 6 |
| B | 1 | 0 | 0 | 0 | 0 |

tme/intukonlinebits

Step 2: Three are no isolated 0s

Step 3: 0 in the cell 4 is adjacent only to 0 in the cell 0 and 0 in cell 7 is adjacent only to 0 in the cell 3. These two pairs are combined and referred to as group 1 and group 2 respectively.

| | BC | 00 | 01 | 11 | 10 |
|---|----|----|----|----|----|
| A | 0 | 0 | 1 | 3 | 2 |
| C | 0 | 4 | 5 | 7 | 6 |
| B | 1 | 0 | 0 | 0 | 0 |

Step 4: There are no quads and octets

Step 5: The 0 in the cell 1 can be combined with 0 in the cell 3 to be from a pair. This pair is referred to as group 3.

| | BC | 00 | 01 | 11 | 10 |
|---|----|----|----|----|----|
| A | 0 | 0 | 1 | 3 | 2 |
| C | 0 | 4 | 5 | 7 | 6 |
| B | 1 | 0 | 0 | 0 | 0 |

Step 6: In group 1 and in group 2, A is eliminated, where in group 3 variable B is eliminated and we get

$$\begin{array}{c} \text{Group 1} \quad \text{Group 2} \quad \text{Group 3} \\ \hline A \quad B \quad C & A \quad B \quad C & A \quad B \quad C \\ \hline 0 \quad 0 \quad 0 & 0 \quad 1 \quad 1 & 0 \quad 1 \quad 1 \\ \hline 1 \quad 0 \quad 0 & 1 \quad 1 \quad 1 & 0 \quad 1 \quad 1 \\ \hline \overline{BC} & \overline{BC} & \overline{AC} \end{array}$$

$$\bar{Y} = \overline{BC} + BC + \overline{AC}$$

$$\bar{Y} = Y = \overline{BC} + BC + \overline{AC} \quad [\text{According to DeMorgan's}]$$

$$Y = \overline{\overline{BC}} + BC + \overline{AC}$$

$$= (\overline{\overline{B}}\overline{C}) \cdot (\overline{B}\overline{C}) \cdot (\overline{A}\overline{C})$$

$$= (\overline{\overline{B}} + \overline{C}) \cdot (\overline{B} + \overline{C}) \cdot (\overline{A} + \overline{C})$$

$$Y = (B + C)(\overline{B} + \overline{C})(\overline{A} + \overline{C})$$

$$\begin{array}{ccccccccc} 1 & 1 & 0 & 1 & 0 & 1 & 1 & 0 & 1 \\ 0 & 1 & 1 & 0 & 1 & 0 & 0 & 1 & 1 \\ 1 & 1 & 1 & 1 & 1 & 1 & 1 & 1 & 1 \\ 0 & 1 & 1 & 1 & 1 & 1 & 1 & 1 & 1 \end{array}$$

$$\begin{array}{ccccccccc} 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \end{array}$$

$$\begin{array}{ccccccccc} 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \end{array}$$

$$\begin{array}{ccccccccc} 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \\ 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 & 0 \end{array}$$

Ex: Minimize the following expression in the pos form
f.me/jntukonlinebits

$$X = (\bar{A} + \bar{B} + C + D)(\bar{A} + \bar{B} + \bar{C} + D)(\bar{A} + \bar{B} + \bar{C} + \bar{D})(\bar{A} + B + C + D)(A + \bar{B} + \bar{C} + D) \\ (\bar{A} + \bar{B} + \bar{C} + \bar{D})(A + B + C + D)(\bar{A} + \bar{B} + C + \bar{D})$$

Sol: $(\bar{A} + \bar{B} + C + D) = M_{12}$, $(\bar{A} + \bar{B} + \bar{C} + D) = M_{14}$, $(\bar{A} + \bar{B} + \bar{C} + \bar{D}) = M_{15}$

$$(\bar{A} + B + C + D) = M_8, (A + \bar{B} + \bar{C} + D) = M_6, (A + \bar{B} + \bar{C} + \bar{D}) = M_7$$

$$(A + B + C + D) = M_0 \text{ and } (\bar{A} + \bar{B} + C + \bar{D}) = M_{13}$$

Step 1: Shows the k-map for four variable and it plotted according to given max terms

Step 2: There are no isolated 1's

Step 3: 0 in the cell 0 is adjacent

Only to 0 in the cell 11 this pair is combined and referred to as group 1

Step 4: There are two quads cells 12, 13, 14 and 15 form a quad

1 and cells 6, 7, 14, 15 forms a quad 2. These two quads are referred to as group 2 and group 3, respectively.

Step 5: All 0s have already been grouped

Step 6: In group 1, Variable A is eliminated

In group 2, Variable C and D are eliminated and 01

in group 3 variable A and D are eliminated.

∴ we get simplified pos Expression

| | | CD | C+D | C+D̄ | C̄+D | C̄+D̄ |
|------|----|----|-----|------|------|-------|
| | | AB | 00 | 01 | 11 | 10 |
| A+B | 00 | 0 | 1 | 3 | 2 | |
| | | 0 | | | | |
| A+B̄ | 01 | 4 | 5 | 7 | 6 | |
| | | 0 | | 0 | 0 | |
| A+B | 10 | 12 | 13 | 15 | 14 | |
| | | 0 | 0 | 0 | 0 | |
| A+B̄ | 11 | 8 | 9 | 11 | 10 | |
| | | 0 | | | | |

| | | CD | Group 1 | | |
|--|----|----|---------|----|----|
| | | AB | 00 | 01 | 11 |
| | 00 | 0 | 1 | 3 | 2 |
| | 01 | 0 | | | |
| | 10 | 4 | 5 | 7 | 6 |
| | 11 | 0 | | 0 | |
| | 11 | 12 | 13 | 15 | 14 |
| | 10 | 0 | 0 | 0 | 0 |
| | 11 | 8 | 9 | 11 | 10 |
| | 10 | 0 | | | |

| Group 1 | | |
|---|---|----|
| A | B | CD |
| 0 | 0 | 00 |
| 1 | 0 | 00 |
| <u>$\bar{B} \bar{C} \bar{D}$</u> | | |

| Group 2 | | |
|---------|---|----|
| A | B | CD |
| 1 | 1 | 00 |
| 1 | 1 | 01 |
| 1 | 1 | 11 |
| 1 | 1 | 10 |

| Group 3 | | |
|---------|---|----|
| A | B | CD |
| 0 | 1 | 11 |
| 0 | 1 | 10 |
| 1 | 1 | 11 |
| 1 | 1 | 10 |

$$\bar{Y} = \overline{BCD} + AB + BC$$

$$y = \bar{Y} = \overline{BCD} + AB + BC$$

$$Y = (B+C+D) \cdot (\bar{A}+\bar{B}) \cdot (\bar{B}+\bar{C})$$

Incompletely Specified functions (Don't Care terms or conditions)

e.g:

| A | B | C | Y |
|---|---|---|---|
| 0 | 0 | 0 | 0 |
| 1 | 0 | 1 | 1 |
| 0 | 1 | 0 | 0 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 1 |
| 1 | 1 | 0 | X |
| 1 | 1 | 1 | X |

Sol:

| A | BC | | 00 | 01 | 11 | 10 |
|---|----|----|----|----|----|----|
| | 00 | 01 | 11 | 10 | 11 | 10 |
| 0 | 0 | 1 | 1 | 1 | 1 | 0 |
| 1 | 4 | 5 | X | X | X | X |

Don't Care Conditions

Group 1

| A | BC | | 00 | 01 | 11 | 10 |
|---|----|----|----|----|----|----|
| | 00 | 01 | 11 | 10 | 11 | 10 |
| 0 | 0 | 1 | 1 | 1 | 1 | 0 |
| 1 | 4 | 5 | X | X | X | X |

Group 1

$$\therefore Y = C$$

| A | B | C |
|---|---|---|
| 0 | 0 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 1 |
| | | C |

Describing Incomplete Boolean function


t.me/jntukonlinebits

$$\text{Ex: } f(A, B, C) = \sum m(0, 2, 4) + d(1, 5)$$

$$f(A, B, C) = \prod M(2, 5, 7) + d(1, 3)$$

$$f(A, B, C) = \sum m(0, 2, 4) + d(1, 5)$$

| | | BC | 00 | 01 | 11 | 10 |
|---|---|----|----|----|----|----|
| | | A | 0 | 1 | 3 | 2 |
| 0 | 0 | 1 | X | | | 1 |
| | 1 | 4 | 5 | 7 | | 6 |

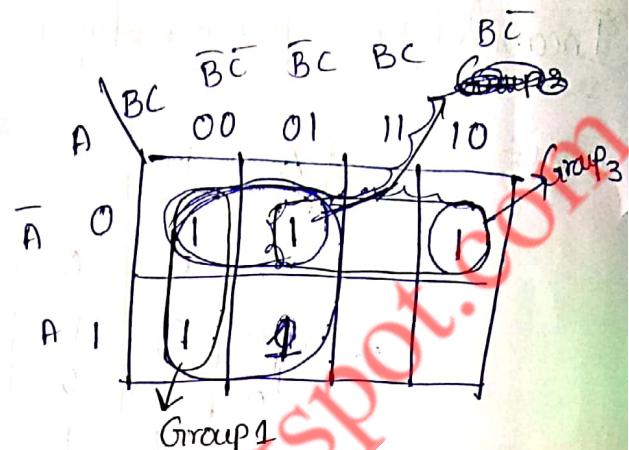


$$\begin{array}{c}
 G_1 \\
 \begin{array}{c} A \\ \diagup B \\ \diagdown C \end{array} \\
 \begin{array}{cc} 0 & 0 \\ 1 & 0 \end{array} \\
 \hline \overline{B} \overline{C}
 \end{array}
 \quad
 \begin{array}{c}
 G_2 \\
 \begin{array}{c} A \\ \diagup B \\ \diagdown C \end{array} \\
 \begin{array}{cc} 0 & 0 \\ 0 & 1 \end{array} \\
 \hline \overline{A} \overline{B} \quad 0
 \end{array}$$

$$\begin{array}{c}
 \text{Group 1} \\
 Y = \overline{B} \overline{C} + \overline{A} \overline{B} + \overline{B} \overline{C} \\
 \begin{array}{c} A \quad B \quad C \\ 0 \quad 0 \quad 0 \\ 0 \quad 0 \quad 1 \\ 1 \quad 0 \quad 0 \\ 1 \quad 0 \quad 1 \end{array} \\
 \hline \overline{B} \quad \text{Group 1}
 \end{array}$$

$$f(A, B, C) = \prod M(2, 5, 7) + d(1, 3)$$

| | | BC | 00 | 01 | 11 | 10 |
|---|---|----|----|----|----|----|
| | | A | 0 | 1 | 3 | 2 |
| 0 | 0 | 0 | X | X | | 0 |
| | 1 | 4 | 5 | 7 | | 6 |

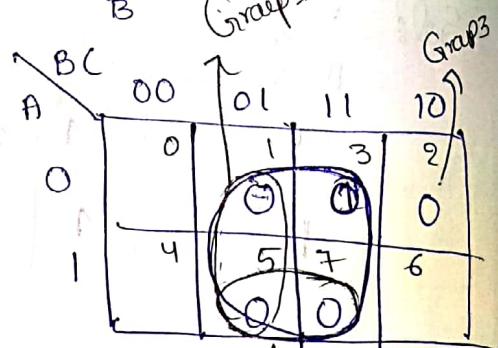

$$\begin{array}{c}
 G_1 \\
 \begin{array}{c} A \quad B \quad C \\ \diagup B \quad \diagdown C \end{array} \\
 \begin{array}{cc} 0 & 0 \\ 1 & 0 \end{array} \\
 \hline \overline{B} \overline{C}
 \end{array}
 \quad
 \begin{array}{c}
 G_2 \\
 \begin{array}{c} A \quad B \quad C \\ \diagup A \quad \diagdown C \end{array} \\
 \begin{array}{cc} 1 & 0 \\ 1 & 1 \end{array} \\
 \hline \overline{A} \overline{B} \quad 0
 \end{array}
 \quad
 \begin{array}{c}
 G_3 \\
 \begin{array}{c} A \quad B \quad C \\ \diagup A \quad \diagdown C \end{array} \\
 \begin{array}{cc} 0 & 1 \\ 1 & 0 \end{array} \\
 \hline \overline{A} \overline{B} \quad 0
 \end{array}$$

$$\begin{array}{c}
 G_1 \\
 \begin{array}{c} A \quad B \quad C \\ \diagup A \quad \diagdown C \end{array} \\
 \begin{array}{cc} 0 & 0 \\ 0 & 1 \\ 1 & 0 \\ 1 & 1 \end{array} \\
 \hline C
 \end{array}$$

$$y = \overline{A} \overline{B} \overline{C} + \overline{A} \overline{B} C //$$

Don't care conditions in logic design

t.me/jntukonlinebits

| | A | B | C | D | P |
|----|---|---|---|---|---|
| 0 | 0 | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 0 | 1 | 1 |
| 2 | 0 | 0 | 1 | 0 | 1 |
| 3 | 0 | 0 | 1 | 1 | 0 |
| 4 | 0 | 1 | 0 | 0 | 1 |
| 5 | 0 | 1 | 0 | 1 | 0 |
| 6 | 0 | 1 | 1 | 0 | 0 |
| 7 | 0 | 1 | 1 | 1 | 1 |
| 8 | 1 | 0 | 0 | 0 | 1 |
| 9 | 1 | 0 | 0 | 1 | 0 |
| 10 | 1 | 0 | 1 | 0 | 1 |
| 11 | 1 | 0 | 1 | 1 | 1 |
| 12 | 1 | 1 | 0 | 0 | 1 |
| 13 | 1 | 1 | 0 | 1 | 1 |
| 14 | 1 | 1 | 1 | 0 | 1 |
| 15 | 1 | 1 | 1 | 1 | 1 |

$$P = \Sigma m(1, 2, 4, 7, 8) + \Sigma d(10, 11, 12, 13, 14, 15)$$

Ex: find the reduced SOP form of the following function.

$$f(A, B, C, D) = \Sigma m(1, 3, 7, 11, 15) + \Sigma d(0, 2, 4)$$

$$f(A, B, C, D) = \Sigma m(1, 3, 7, 11, 15) + \Sigma d(0, 2, 4)$$

| | AB | CD | 00 | 01 | 11 | 10 |
|----|----|----|----|----|----|----|
| 00 | X | 0 | 1 | 1 | 2 | 1 |
| 01 | X | 4 | 5 | 7 | 6 | |
| 11 | | 12 | 13 | 15 | 14 | |
| 10 | | 8 | 9 | 14 | 10 | |


| AB | CD | 00 | 01 | 11 | 10 | G ₁₁ | G ₂ |
|----|----|----|----|----|----|--|---|
| 00 | | 1 | 1 | 1 | 1 | A B C D 0 0 0 0 0 0 0 1 0 0 1 1 0 1 1 1 1 1 1 1 | A B C D 0 0 0 0 0 0 0 1 0 0 1 1 0 1 1 1 0 0 1 0 1 0 1 1 1 1 1 1 1 0 1 1 1 1 0 1 1 1 1 0 1 0 0 1 1 0 1 0 1 1 0 0 1 0 0 0 |
| 01 | | 0 | | 1 | | | |
| 11 | | | | 1 | | | |
| 10 | | | | 1 | | | |

$$\therefore Y = \bar{A}\bar{B} + CD$$

Ex: Reduce the following function using K-map technique t.me/jntukonlinebits

$$f(A, B, C, D) = \sum m(5, 6, 7, 12, 13) + \sum d(4, 9, 14, 15)$$

| | | CD | 00 | 01 | 10 | 11 |
|----|----|----|----|----|----|----|
| | | AB | 00 | 01 | 10 | 11 |
| AB | CD | 00 | 0 | 1 | 3 | 2 |
| | | 01 | 4 | 5 | 7 | 6 |
| AB | CD | 10 | X | 1 | 1 | X |
| | | 11 | 12 | 13 | 15 | 14 |
| AB | CD | 10 | 8 | 9 | 11 | 10 |
| | | 11 | X | | | |

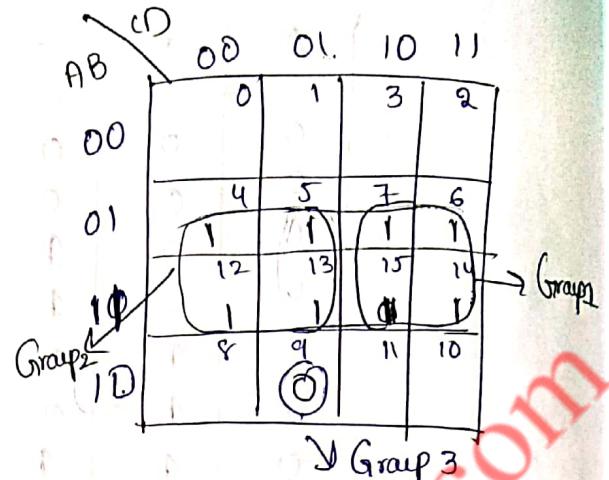

G₁

G₂

$$\begin{array}{l} A \ B \ C \ D \\ \hline 0 \ 1 \ 0 \ 0 \\ 0 \ 1 \ 0 \ 1 \\ 1 \ 0 \ 0 \ 0 \\ 1 \ 0 \ 0 \ 1 \end{array}$$

$$\begin{array}{l} A \ B \ C \ D \\ \hline 0 \ 1 \ 1 \ 0 \\ 0 \ 1 \ 1 \ 1 \\ 1 \ 1 \ 1 \ 0 \\ 1 \ 1 \ 1 \ 1 \end{array}$$

$$\begin{array}{l} A \ B \ C \ D \\ \hline 1 \ 0 \ 0 \ 1 \\ 1 \ 0 \ 1 \ 0 \end{array}$$

$$Y = A\bar{B}\bar{C}\bar{D} + B\bar{C}\bar{D} + BC$$

Ex: Reduce the following function by using K-map technique

$$f(A, B, C, D) = \overline{\sum m(0, 3, 4, 7, 8, 10, 12, 14)} + \overline{\sum d(2, 6)}$$

| | | CD | 00 | 01 | 11 | 10 |
|----|----|----|----|----|----|----|
| | | AB | 00 | 01 | 11 | 10 |
| AB | CD | 00 | 0 | 1 | 0 | X |
| | | 01 | 0 | 5 | 7 | 6 |
| AB | CD | 11 | 0 | 1 | 1 | 0 |
| | | 10 | 12 | 13 | 15 | 14 |
| AB | CD | 10 | 8 | 9 | 11 | 10 |
| | | 11 | X | | | |


| | | CD | 00 | 01 | 11 | 10 | |
|----|----|----|----|----|----|----|--|
| | | AB | 00 | 01 | 11 | 10 | |
| AB | CD | 00 | 0 | 0 | 10 | | |
| | | 01 | 0 | 0 | 10 | | |
| AB | CD | 11 | 0 | 0 | 10 | | |
| | | 10 | 0 | 0 | 10 | | |
| | | 11 | 0 | 0 | 10 | | |
| | | 10 | 0 | 0 | 10 | | |

$$X = \bar{D} + \bar{A}C$$

$$\begin{aligned} Y &= \bar{Y} = \overline{\bar{D} + \bar{A}C} \\ &= (\bar{D}) \cdot (\bar{A}C) \\ &= D \cdot (A + \bar{C}) \end{aligned}$$

$$* f(A, B, C, D) =$$

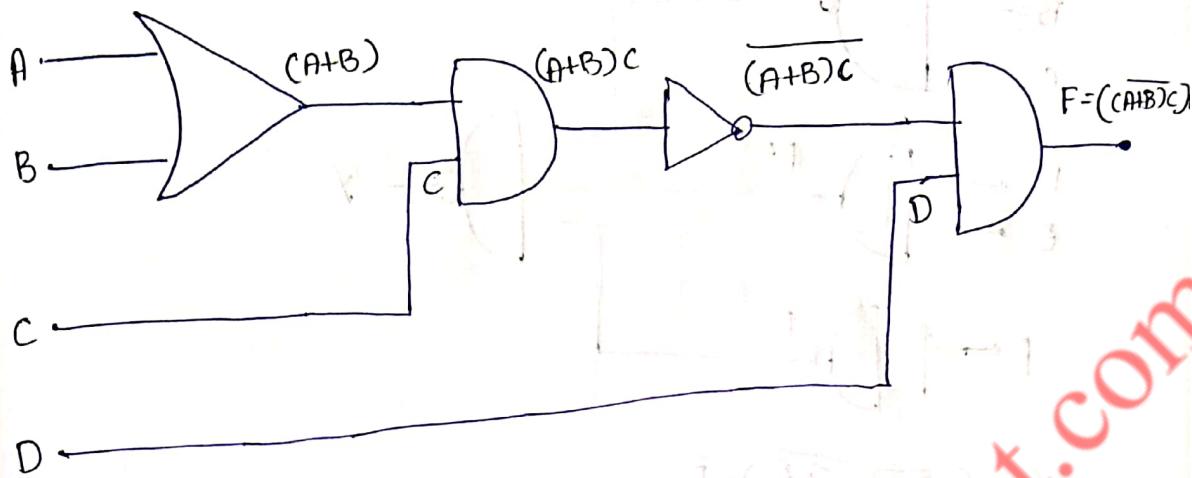
Ex: $F = \overline{(A+B)}C D$ to implement logic Design?




NAND to NAND Implementation:

$$Y = ABC + DEF$$


(i) AND - OR

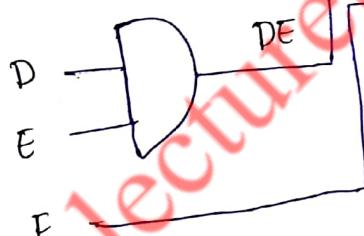

(ii) NAND - Bubble OR

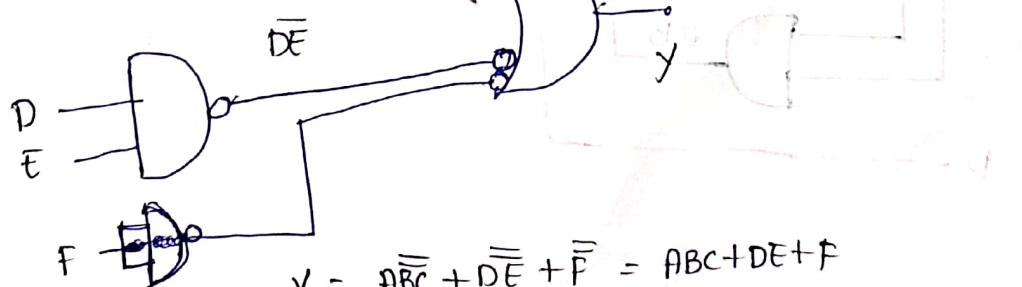
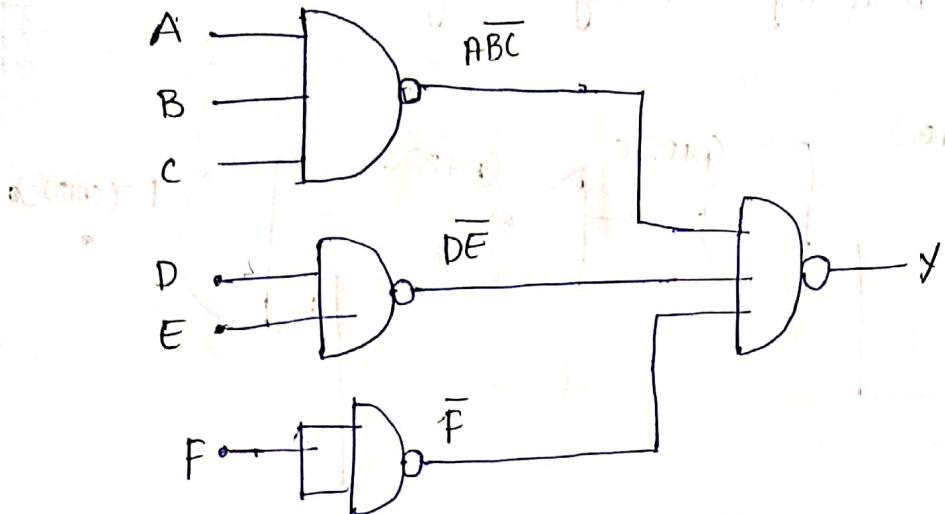
$$y = \overline{ABC} + \overline{DE} + \overline{F} = ABC + DEF$$




$$\begin{aligned}
 Y &= (\overline{ABC}) \cdot (\overline{DE}) \cdot \overline{F} \\
 &= (\overline{\overline{ABC}}) + (\overline{\overline{DE}}) + \overline{F} \\
 &= ABC + DE + F
 \end{aligned}$$

Ex: $y = Ac + ABC + \overline{ABC} + AB + D$ Implement the following Boolean function with NAND to NAND logic.


$$\begin{aligned}
 y &= AC + ABC + \overline{ABC} + AB + D \\
 &= AC + BC(A + \overline{A}) + AB + D \\
 y &= AC + BC + AB + D
 \end{aligned}$$

(Q) AND - OR

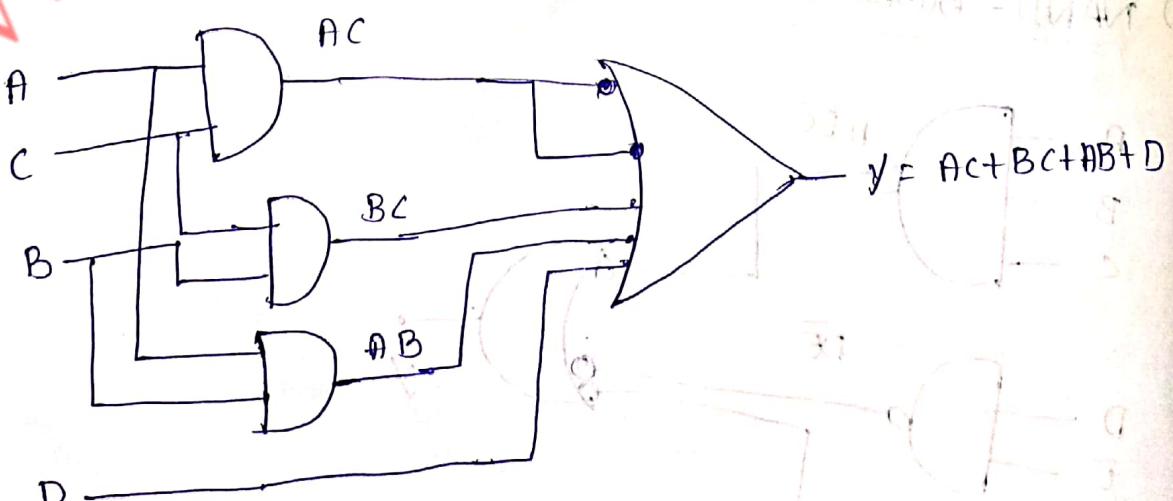


(9) NAND - Bubble OR

t.me/jntukonlinebits

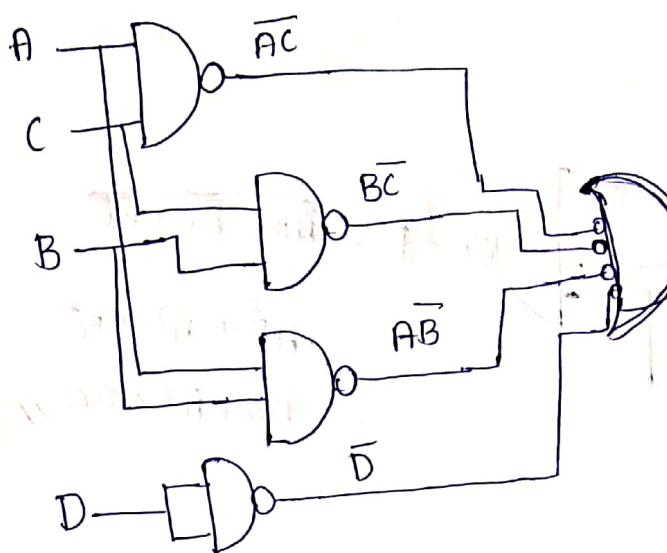

$$\begin{aligned}y &= \overline{\overline{AC}} + \overline{\overline{BC}} + \overline{\overline{AB}} + \overline{D} \\&= AC + BC + AB + D\end{aligned}$$

(99) NAND - NAND

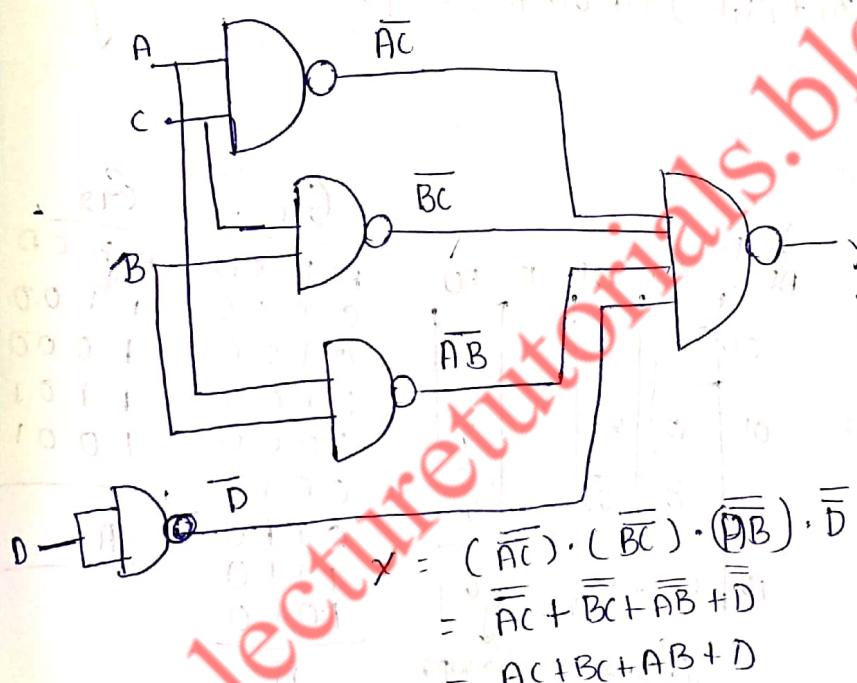


$$\begin{aligned}x &= (\overline{\overline{AC}}) \cdot (\overline{\overline{BC}}) \cdot (\overline{\overline{AB}}) \cdot \overline{D} \\&= \overline{\overline{AC}} + \overline{\overline{BC}} + \overline{\overline{AB}} + \overline{D} \\&= AC + BC + AB + D\end{aligned}$$

E.g. Implementation the following Boolean Expression with NAND-NAND

Logic. $F(A, B, C) = \sum m(0, 1, 3, 5)$

| | | BC | | G1 | G2 | |
|---|---|----|----|----|----|--|
| | | 00 | 01 | 11 | 10 | |
| A | 0 | 0 | 1 | 1 | 0 | |
| | 1 | 4 | 5 | 7 | 6 | |
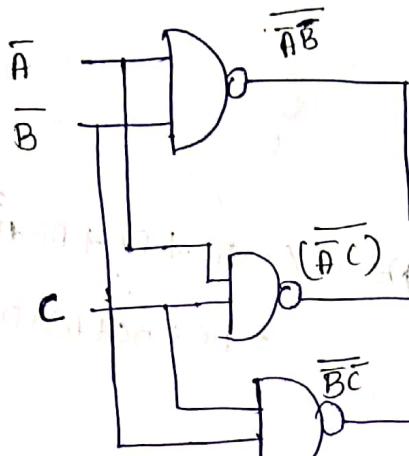
$$F(A, B, C) = \overline{A}\overline{B} + \overline{A}\overline{C} + \overline{B}\overline{C}$$



$$F = \overline{A}\overline{B} + \overline{A}C + \overline{BC},$$

$$\begin{aligned} F &= \overline{A}\overline{B} \cdot \overline{AC} \cdot \overline{BC} \\ &= \overline{A}\overline{B} + \overline{AC} + \overline{BC} \\ &= \overline{A}\overline{B} + \overline{A}\overline{C} + \overline{BC} // \end{aligned}$$

Ex: ① Find the reduced pos form of the following Equation
 $f(A,B,C,D) = \sum m(1,3,7,11,15) + d(0,2,5)$ Implement and using
 NAND logic?

| CD | 00 | 01 | 11 | 10 |
|----|----|----|----|----|
| AB | 00 | 11 | 13 | 02 |
| 00 | 0 | 1 | 1 | x |
| 01 | 0 | x | 1 | 0 |
| 11 | 0 | 0 | 1 | 0 |
| 10 | 0 | 0 | 1 | 0 |

| CD | 00 | 01 | 11 | 10 |
|----|----|----|----|----|
| AB | 00 | 01 | 11 | 10 |
| 00 | 0 | 1 | 1 | 0 |
| 01 | 0 | x | 1 | 0 |
| 11 | 0 | 0 | 1 | 0 |
| 10 | 0 | 0 | 1 | 0 |

Group 2 Group 1

| G ₁₁ | G ₁₂ |
|-----------------|-----------------|
| A B CD | A B CD |
| 0 0 0 0 | 1 1 0 0 |
| 0 1 0 0 | 1 0 0 0 |
| 1 1 0 0 | 1 1 0 1 |
| 1 0 0 0 | 1 0 0 1 |
| 0 0 1 0 | 0 0 1 0 |
| 0 1 1 0 | 0 1 1 0 |
| 1 1 1 0 | 1 1 1 0 |
| 1 0 1 0 | 1 0 1 0 |
| | <u>D</u> |

$$\bar{x} = \bar{D} + A\bar{C}$$

$$Y = \bar{x} = (\bar{D})(\bar{A}\bar{C})$$


$$\therefore Y = D \cdot (\bar{A} + C)$$

Ex: ② Using k-map, determine the minimal sop expression and
 realize the simplified expression using NAND logic?

$$f(w,x,y,z) = \text{ITM}(0,2,3,7,8,9,10)$$

$$\text{at: } f(w,x,y,z) = \sum m(1,4,5,6,11,12,13,14,15)$$

$$\therefore Y = D \cdot (\bar{A} + C)$$

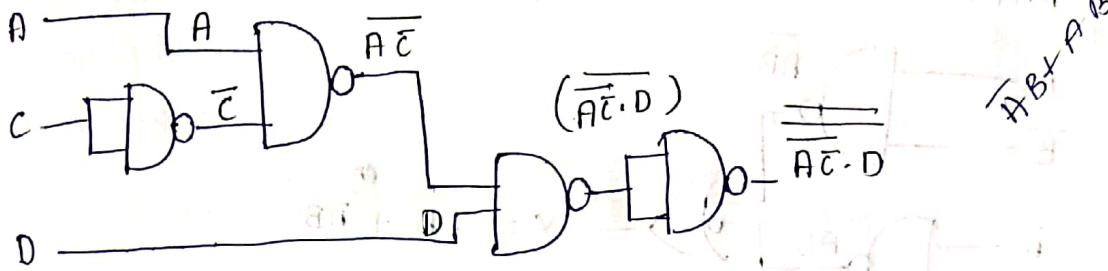

$$Y = (\bar{A}\bar{C} \cdot D)$$

$$= (\bar{A} + \bar{C}) \cdot D$$

$$Y = (\bar{A} + C) \cdot D //$$


Eg: To implement X-OR gate by using NAND-NAND logic gate

$$Y = A\bar{B} + \bar{A}B$$


The X-OR gate function is two inputs and one output. The i/p variables are A and B.

The o/p variable Y
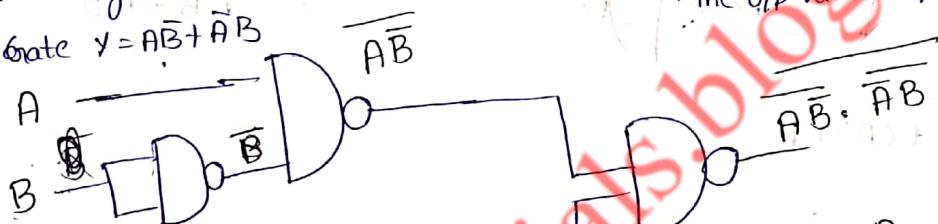
$$\text{X-OR gate } Y = A\bar{B} + \bar{A}B$$




NAND-NAND

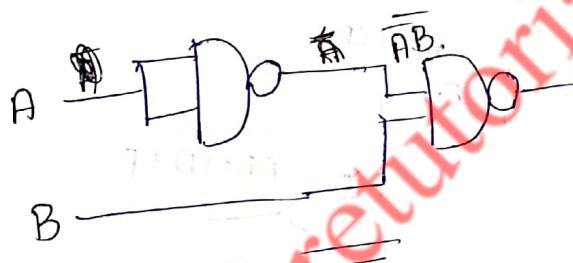

$$Y = \bar{A}\bar{B} + \bar{A}B$$


$$Y = A\bar{B} + \bar{A}B //$$

(a) AND-OR

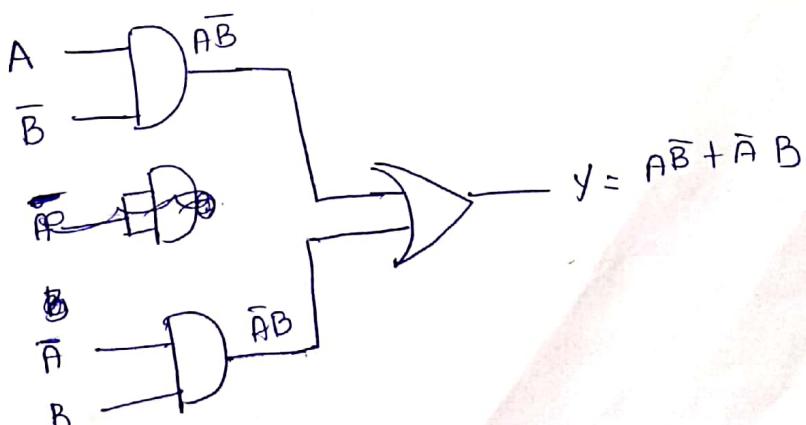


(ii) NAND - Bubbled OR


$$Y = A\bar{B} + \bar{A}B$$

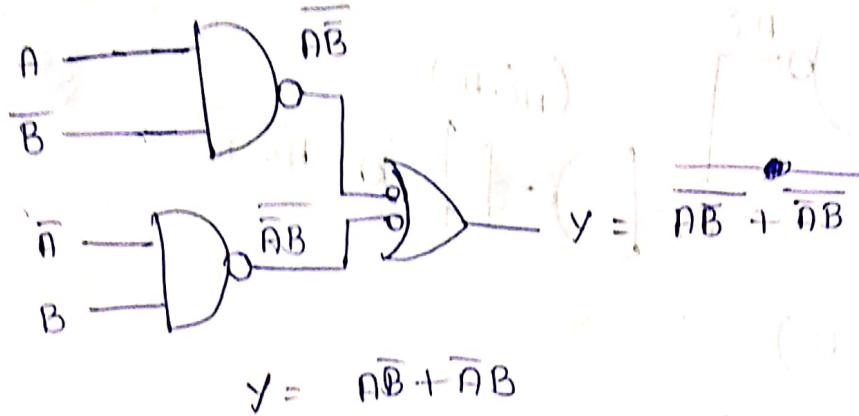

(iii) NAND-NAND

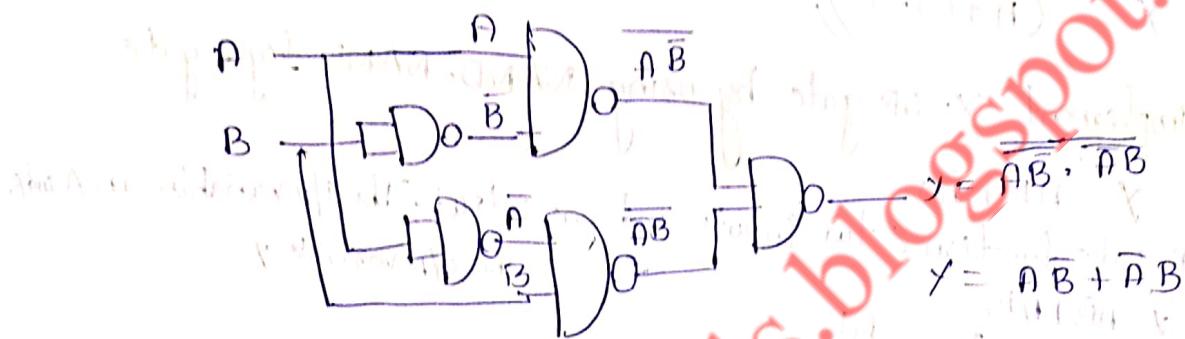
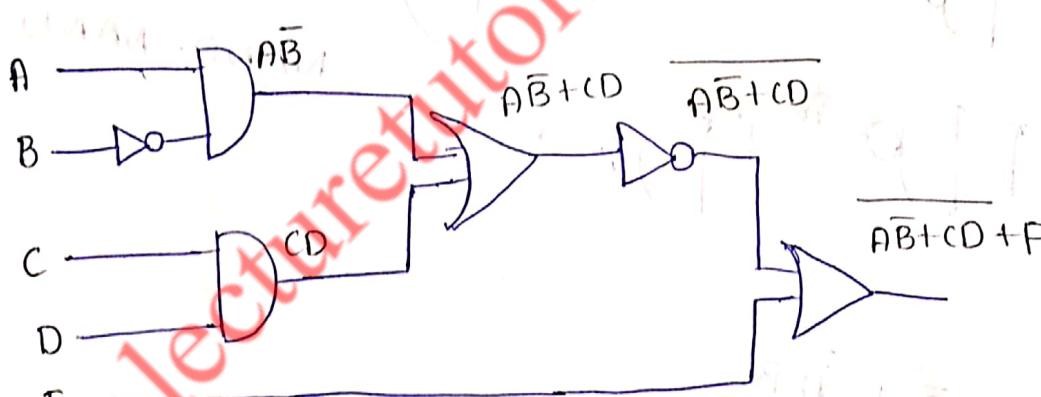
$$\text{Ex: } (\overline{AB} + \overline{CD}) + F$$



Ex: Implement the following function with NAND-to-NAND logic

$$f(A, B, C, D) = \sum_m(0, 1, 3, 5)$$

$$y = AC + BC + AB + D$$

NOR - NOR Implementation:

t.me/jntukonlinebits


(i) OR-AND

(ii) NOR-Bubbled AND


(iii) NOR-NOR

$$\text{Ex: } y = (A+B+C) \cdot (D+E) \cdot F$$


(i) OR-AND

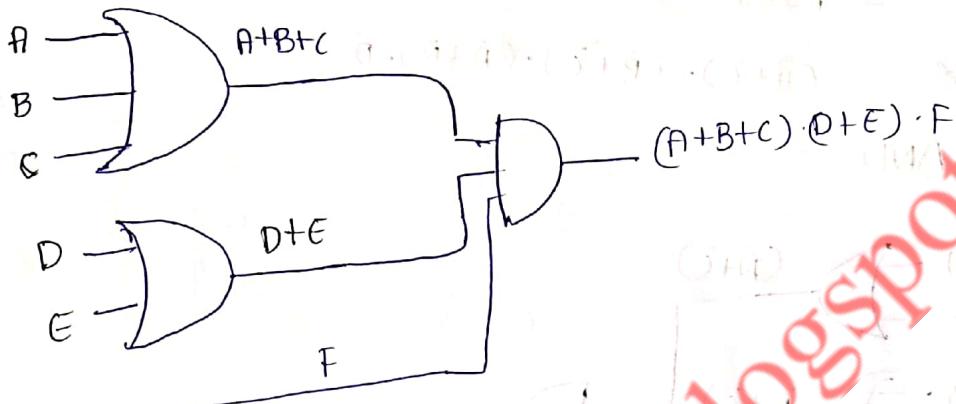

(ii) NOR-Bubbled AND

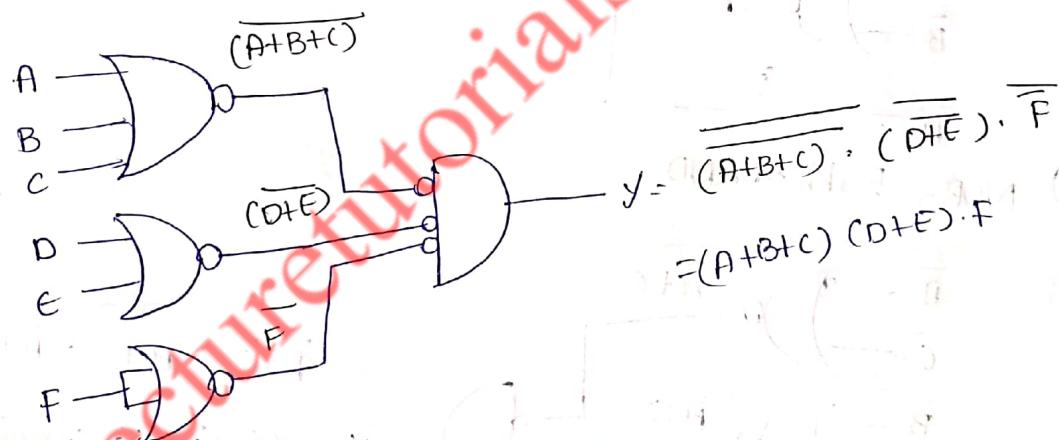

(iii) NOR-NOR

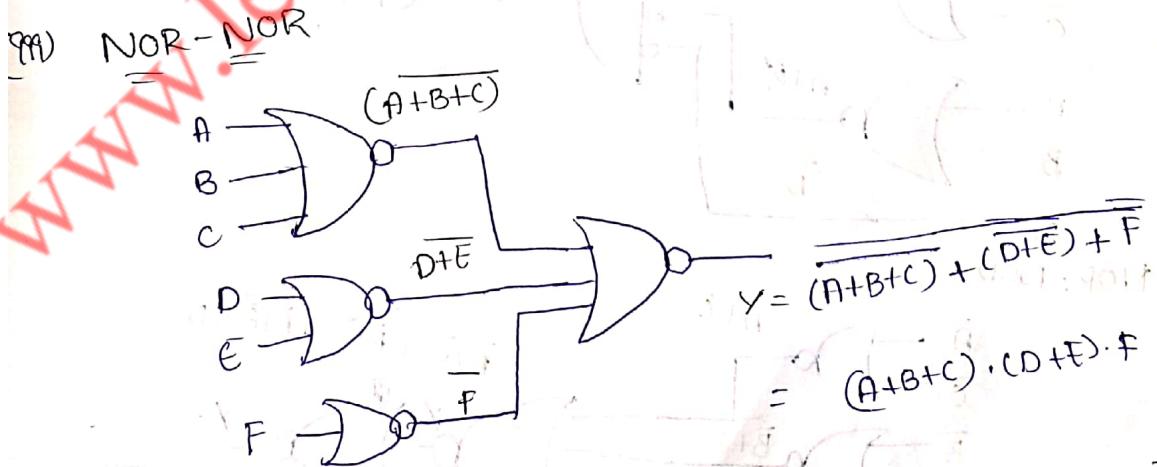

$$\begin{aligned} \because \overline{A+B} &= \overline{A} \cdot \overline{B} \\ \overline{\overline{A}} &= A \end{aligned}$$

Ex :- Implement the following Boolean function with NOR-NOR logic
 t.me/jntukonlinebits

$$Y = AC + BC + AB + D$$

The given Boolean Expression

$$Y = AC + BC + AB + D$$


Assumption . By using duality theorem

$$\bar{Y} = \overline{AC + BC + AB + D}$$

$$= (\bar{A}\bar{C}) \cdot (\bar{B}\bar{C}) \cdot (\bar{A}\bar{B}) \cdot \bar{D}$$


$$\bar{Y} = (\bar{A} + \bar{C}) \cdot (\bar{B} + \bar{C}) \cdot (\bar{A} + \bar{B}) \cdot \bar{D}$$

(i) OR-AND

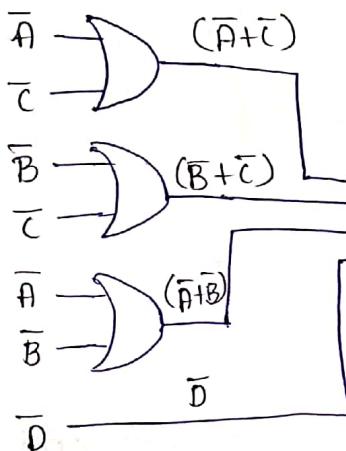

$$\bar{Y} = (\bar{A} + \bar{C}) \cdot (\bar{B} + \bar{C}) \cdot (\bar{A} + \bar{B}) \cdot \bar{D}$$


(ii) NOR-Bubbled AND

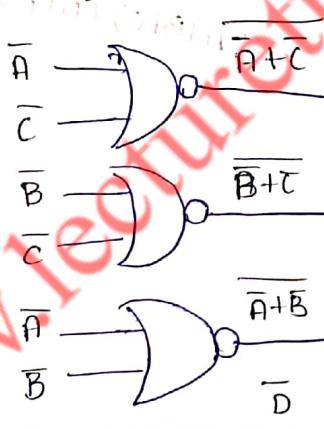

$$\bar{Y} = (\bar{A} + \bar{C}) \cdot (\bar{B} + \bar{C}) \cdot (\bar{A} + \bar{B}) \cdot \bar{D}$$

999

NOR=NOR

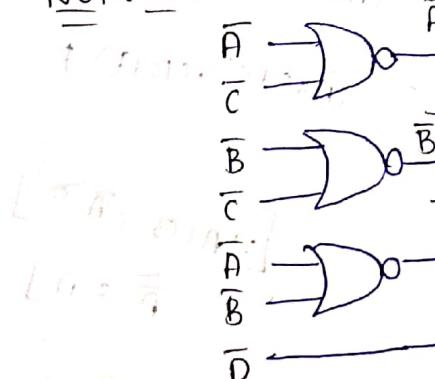

$$\bar{Y} = (\bar{A} + \bar{C}) + (\bar{B} + \bar{C}) + (\bar{A} + \bar{B}) + \bar{D}$$

$$Y =$$

$$\bar{A} + \bar{C} + \bar{B} + \bar{C} + \bar{A} + \bar{B} + \bar{D}$$

$$\bar{Y} = (\bar{A} + \bar{C}) \cdot (\bar{B} + \bar{C}) \cdot (\bar{A} + \bar{B}) \cdot \bar{D}$$

$$\bar{Y} = (A + C) \cdot (B + C) \cdot (A + B) \cdot D$$

$$\bar{Y} = (\bar{A} + \bar{C}) \cdot (\bar{B} + \bar{C}) \cdot (\bar{A} + \bar{B}) \cdot \bar{D}$$

$\therefore \bar{A} + \bar{B} = \bar{A} \cdot \bar{B} = AB$
t.me/jntukonlinebits

$$Y = AC + BC + AB + D$$

Ex: Implement the following Boolean function with NOR-NOR logic

$$f(A, B, C) = \prod_M(0, 2, 4, 5, 6)$$

Ex: Implement the X-NOR gate by using only NOR gate ($AB + \bar{A}\bar{B}$)

| | | BC | 00 | 01 | 11 | 10 |
|---|--|----|----|----|----|----|
| | | A | 0 | 0 | 1 | 0 |
| | | C | 0 | 1 | 0 | 1 |
| 0 | | | 0 | 0 | 1 | 0 |
| 1 | | | 0 | 1 | 0 | 1 |

↓
 G_1 ↓
 G_2

$$\begin{array}{c} G_1 \\ \hline A & B & C \\ 0 & 0 & 0 \\ 1 & 0 & 0 \\ \hline \end{array} \quad \begin{array}{c} G_2 \\ \hline A & B & C \\ 0 & 0 & 0 \\ 1 & 0 & 0 \\ 1 & 0 & 1 \\ \hline \end{array} \quad \begin{array}{c} G_3 \\ \hline A & B & C \\ 0 & 1 & 0 \\ 1 & 1 & 0 \\ \hline \end{array}$$

$$\bar{B}\bar{C} \cdot \bar{A}\bar{B}$$


$$Y = \overline{\bar{B}\bar{C} + A\bar{B} + BC}$$

$$\bar{Y} = \overline{\bar{B}\bar{C} + A\bar{B} + BC}$$


$$= (\bar{B} + \bar{C}) \cdot (\bar{A} + \bar{B}) \cdot (\bar{B} + \bar{C})$$

$$Y = (B+C) \cdot (\bar{A}+B) \cdot (\bar{B}+C)$$

(i) OR-AND

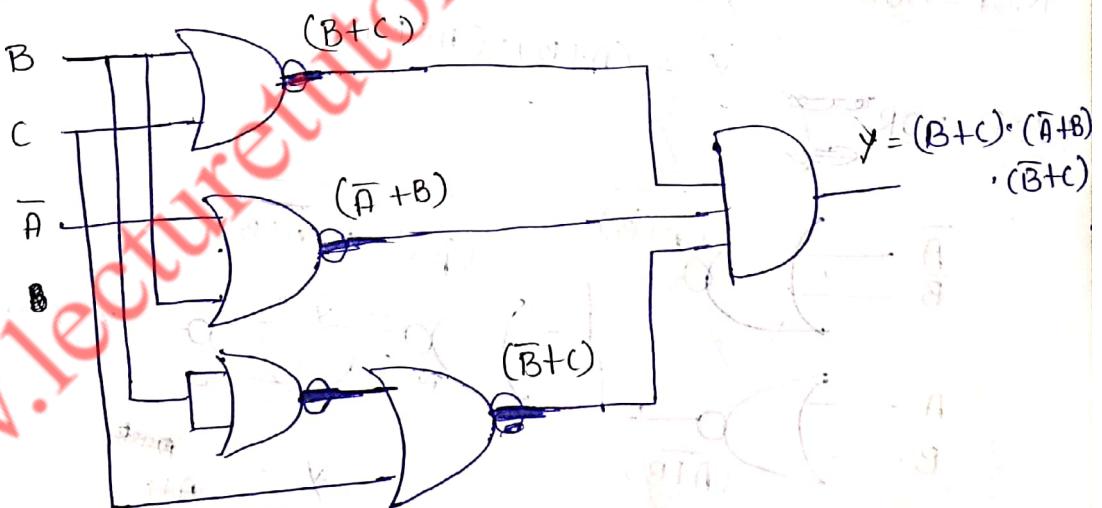


(ii) NOR-Bubbled AND

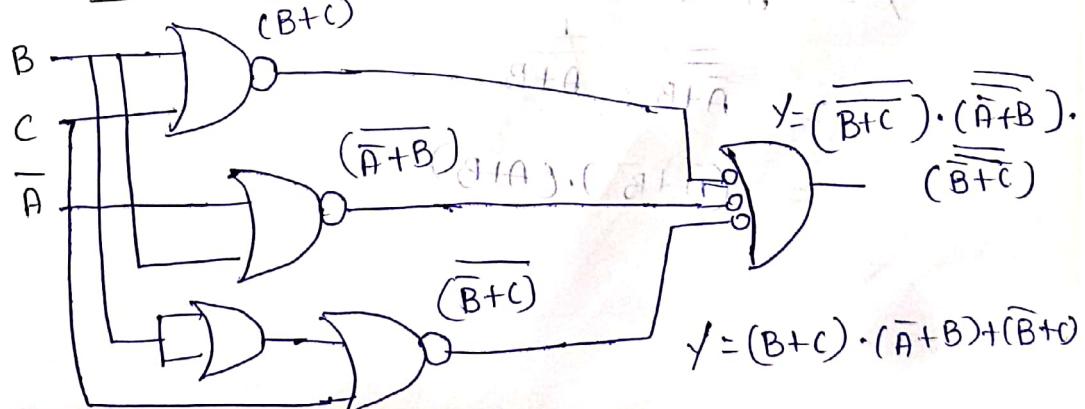

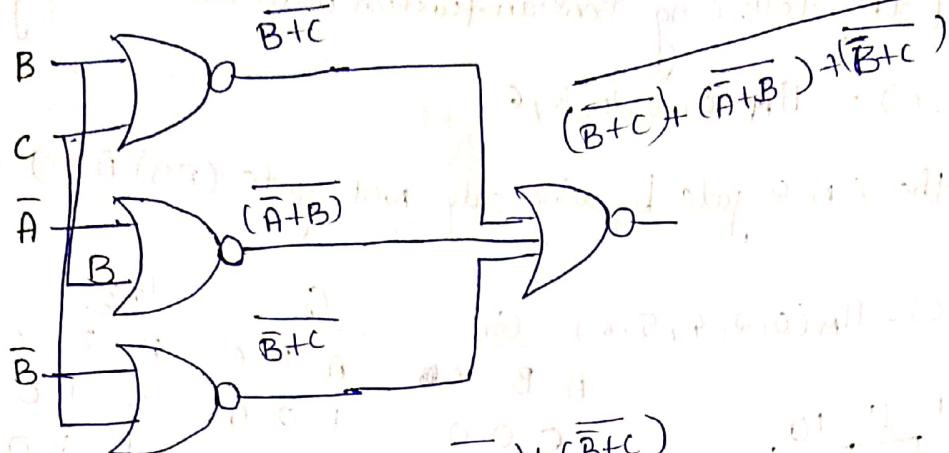(iii) NOR-NOR

t.me/jntukonlinebits

$$Y = (B+C) \cdot (\bar{A}+B) \cdot (\bar{B}+C)$$



$$\begin{aligned} Y &= (\bar{B}+C) + (\bar{A}+B) + (\bar{B}+C) \\ &= (\bar{B}+C) \cdot (\bar{A}+B) \cdot (\bar{B}+C) \end{aligned}$$

$$Y = (\bar{B}+C) \cdot (\bar{A}+B) \cdot (\bar{B}+C)$$

- ② Implement the X-NOR gate by using only NOR gate
The X-NOR gate function has two inputs and one output. The input variables are A and B and the output variable is Y


$$Y = AB + \bar{A}\bar{B}$$

NOR-NOR


$$Y = \bar{A}B + \bar{A}\bar{B}$$

$$Y = (\bar{A}+\bar{B}) \cdot (A+B)$$

(NOR+NOR)
(OR)

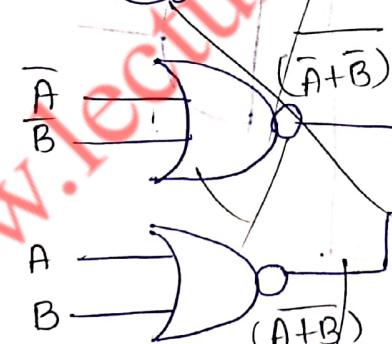
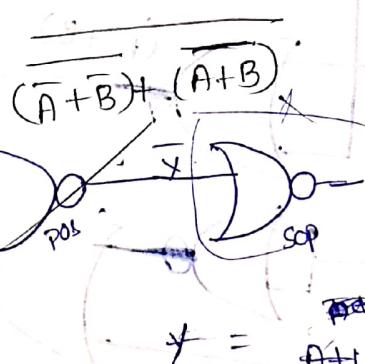
$$\bar{Y} = \bar{\bar{A}} + \bar{B} + (\bar{A}+B)$$



$$Y = AB + \bar{A}\bar{B}$$


$$Y = \bar{A} + \bar{B}$$

$$\begin{aligned} & (8)(i) \cdot (5)(ii) \cdot (5)(iv) \\ & (5)(v) = ((\bar{A}+\bar{B}) \cdot (A+B)) \cdot ((\bar{A}+\bar{B}) \cdot (A+B)) \end{aligned}$$

Q1: Implement the $\bar{A} \oplus B$

A-TING

t.me/jntukonlinebits

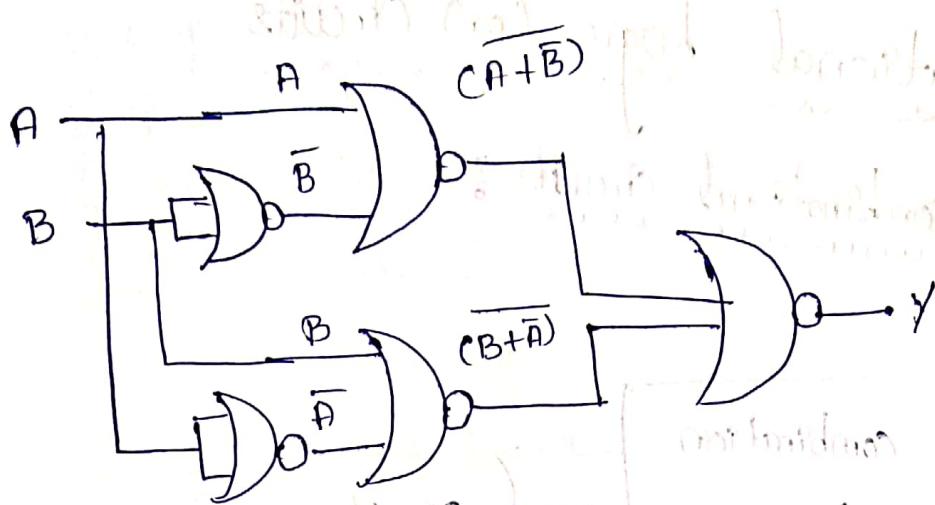

$$y = \overline{(A+B)} + \overline{(B+A)}$$

$$y = \overline{\overline{(A+B)}} \cdot \overline{\overline{(B+A)}}$$

$$y = (A+\bar{B})(B+\bar{A})$$

$$= AB + \bar{B}\bar{B} + \bar{A}\bar{A} + \bar{A}\bar{B}$$

$$= AB + \bar{A}\bar{B}$$

(as $\bar{B}\bar{B} = 0$
and $\bar{A}\bar{A} = 0$)

open - QP - S3


open - QP - S3

closed - S3

open - QP - S3

closed - S3

closed - S3

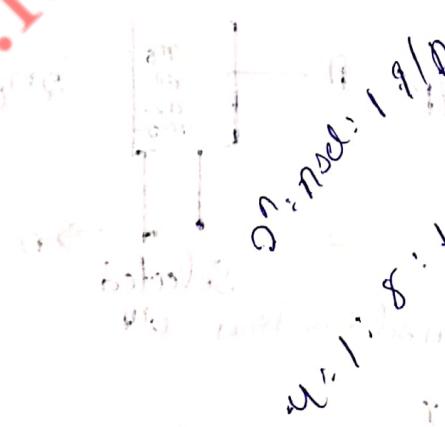


| | | | |
|---|---|---|---|
| 0 | 0 | 0 | A |
| 0 | 1 | 1 | B |
| 1 | 0 | 0 | |
| 1 | 1 | 1 | y |

UNIT-4

t.me/jntukonlinebits

Combinational logic (or) Circuits

Block diagram of combinational circuits

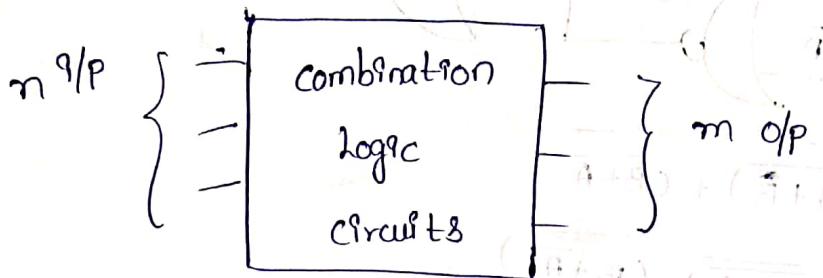

Topics:

1. Half - Adder

- 2 - I/P - 2 O/P

2. Half - Sub

- 2 - I/P - 2 O/P

3. Full - adder

- 3 - I/P - 2 O/P

4. Full - Sub

- 3 - I/P - 2 O/P


5. Decoder -

n - I/P - 2^n O/P


$$Ex: 2 - I/P - 2^2 = 4 O/P$$

$$Ex: 3 - I/P - 2^3 = 8 O/P$$

3:8 Decoder

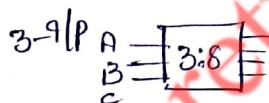

6. Encode - $2^n I/P - n O/P$

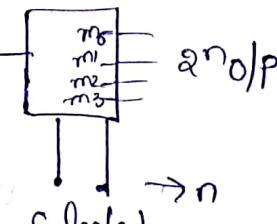

7. $n: 2^n - O/P$ - multiplex - MUX - n selection lines

8. $n: 2^n - I/P$ - De-multiplex - De-Mux


9. Priority Encoder

| A | B | S | C |
|---|---|---|---|
| 0 | 0 | 0 | 0 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 1 |


Combinational Circuits

- When logic gates are connected together to produce a specified output for all possible combinations of input variables, with no storage involved, certain specified combinations of input variables, with no storage involved, the resulting circuit is called as combinational logic circuit. The remaining ϵ resulting circuit is called as combinational logic circuit. In combinational logic the output variables are at all times dependent on the combination of input variables.

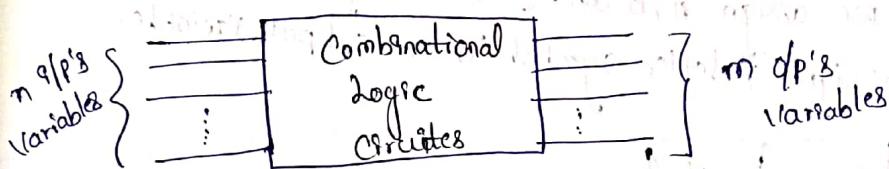The block diagram of input n combination circuit is given below



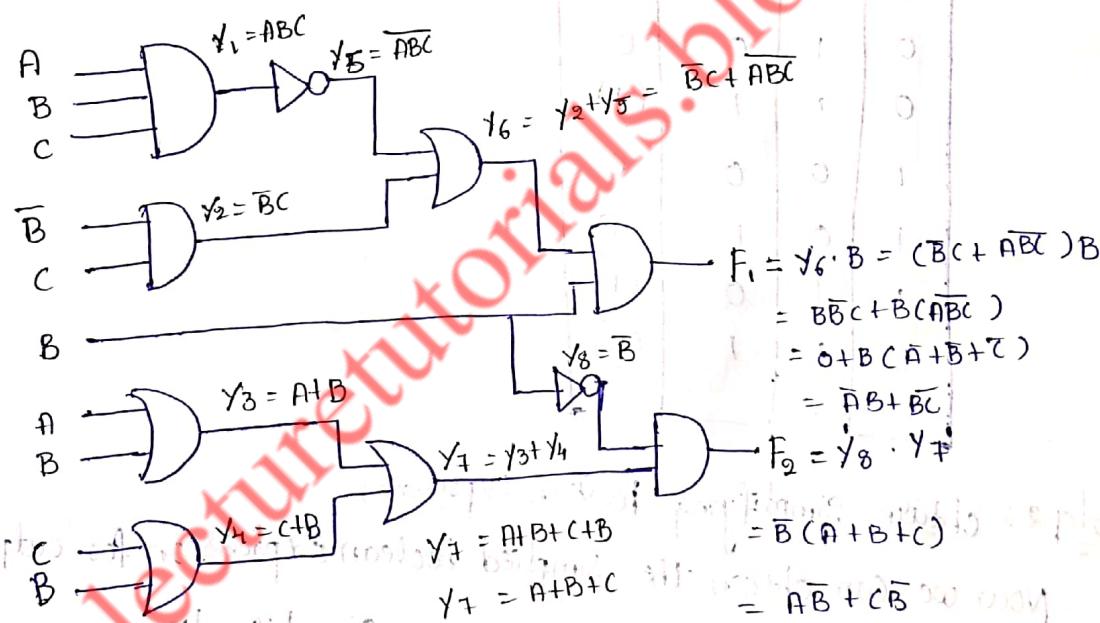Analysis Procedure :-
To obtain the boolean function for output of the given circuit



| ABC | \bar{B} | y_1 | y_2 | y_3 | y_4 | y_5 | y_6 | y_7 | y_8 | F_1 | F_2 |
|-------|-----------|-------|-------|-------|-------|-------|-------|-------|-------|-------|-------|
| 0 0 0 | 1 | 0 | 0 | 0 | 0 | 1 | 1 | 0 | 1 | 0 | 0 |
| 0 0 1 | 1 | 0 | 1 | 0 | 0 | 1 | 1 | 1 | 0 | 0 | 0 |
| 0 1 0 | 0 | 0 | 0 | 1 | 1 | 1 | 1 | 0 | 1 | 1 | 1 |
| 0 1 1 | 0 | 0 | 0 | 1 | 1 | 1 | 1 | 1 | 0 | 0 | 1 |
| 1 0 0 | 1 | 0 | 0 | 1 | 0 | 1 | 1 | 1 | 0 | 0 | 0 |
| 1 0 1 | 1 | 0 | 1 | 0 | 1 | 1 | 1 | 0 | 0 | 1 | 0 |
| 1 1 0 | 0 | 0 | 0 | 1 | 1 | 1 | 1 | 0 | 0 | 0 | 0 |
| 1 1 1 | 0 | 1 | 0 | 1 | 1 | 0 | 0 | 0 | 1 | 0 | 0 |

Design procedure:

- Example of problem :-
- * Design a combinational logic circuit with three input variables that will produce a logic one output when more than one input variables are logic one.

Step 1 : Derive the truth table for given statement

The given problem specifies that there are three input variables and only one output variable. We assign A, B and C letter symbols to three input variables and assign "Y" letter symbol to one output variable.


Step 1

| A | B | C | Y |
|---|---|---|---|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 0 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 1 |
| 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 1 |

Step 2 : obtain simplifying boolean expression


Now we can obtain the simplified boolean expression for output

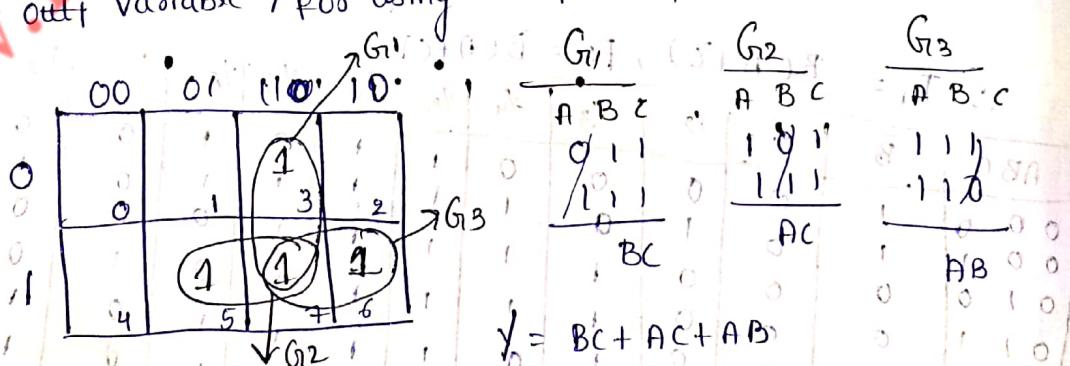for out variable Y for using K-map simplification



Step 3 : Draw the logic diagram

We are going to draw various combinational circuits to the above boolean expression

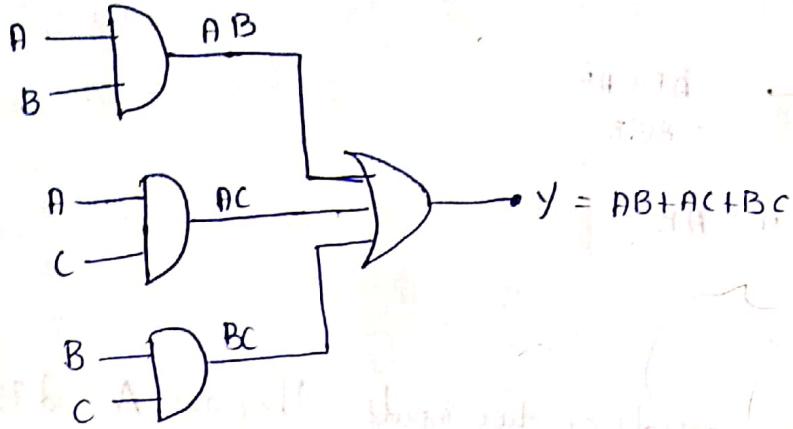Design of Adders

→ Digital computers perform various arithmetic operations like the addition of two binary digits. This simple addition consists of four elementary operations, namely

$$\begin{aligned} 0+0 &= 0 \\ 0+1 &= 1 \\ 1+0 &= 1 \\ 1+1 &= (10)_2 \end{aligned} \quad \left. \begin{array}{l} \\ \\ \end{array} \right\}$$

Half adder


→ The Half Adder consists of two input variables and two output variables. Assign A and B as input variables and sum (S) and carry (C) as output variables.

$$A, B = 1/p \text{ variables}$$

$$S, C = 0/p \text{ variables}$$

Truth table

| A | B | S | C |
|---|---|---|---|
| 0 | 0 | 0 | 0 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 1 |

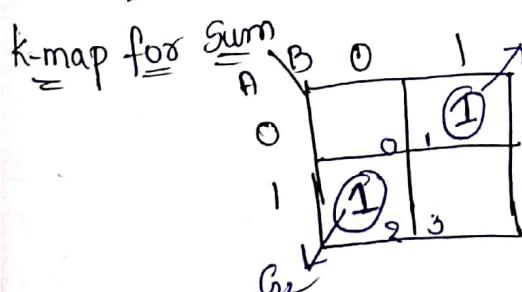


$$\begin{aligned} S &= \overline{AB} + AB \\ &= A \oplus B \end{aligned}$$

$$C = AB$$



for S

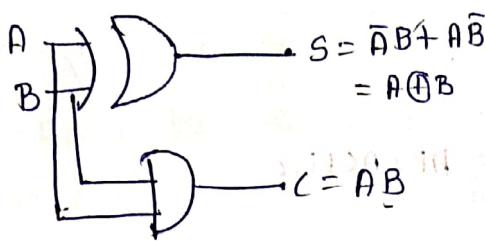
⑨ Half - subtraction:

→ The Half subtraction consists of two inputs they are A and B and two outputs they are difference (D) and borrow (B).

→ The truth table

| A | B | D (difference) | B (borrow) |
|---|---|-------------------|---------------|
| 0 | 0 | 0 | 0 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 0 |


K-map for D

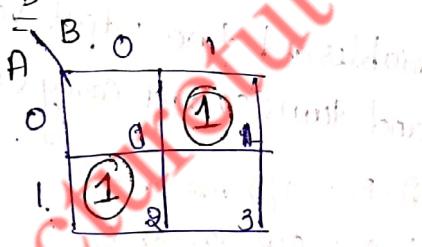


$$D = A \bar{B} + \bar{A}B$$

$$= A \oplus B$$

Logic Diagram

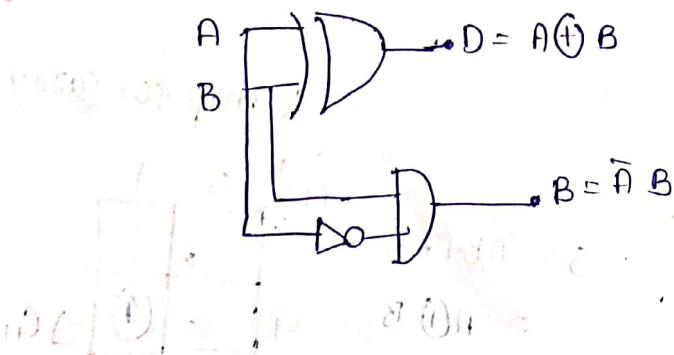

K-map for B

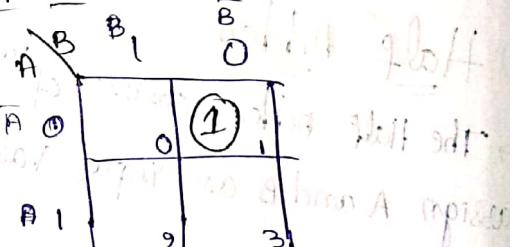

$$B = \bar{A}B$$

iii) Full-Adder:

→ In full-adder consists of three inputs they are A, B, C and 3 outputs are sum and carry.


| A | B | C | S (sum) | C (Carry) |
|---|---|---|---------|-----------|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 | 0 |
| 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 1 | 0 | 1 |
| 1 | 0 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 | 1 |
| 1 | 1 | 0 | 0 | 1 |
| 1 | 1 | 1 | 1 | 1 |

K-map for C

$$C = AB + BC + CA$$

K-map for S

$$S = A \oplus B \oplus C$$

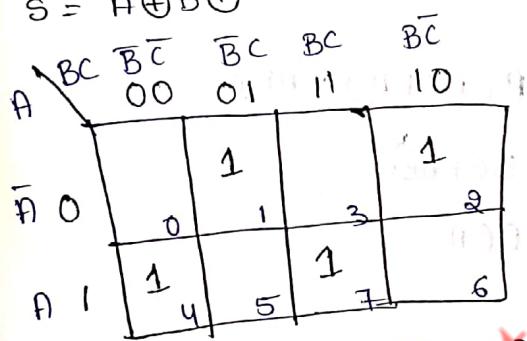

$$S = \overline{A}\overline{B}C + \overline{A}B\overline{C} + A\overline{B}\overline{C} + ABC$$



$$= C(\overline{A}\overline{B} + AB) + \overline{C}(\overline{A}B + A\overline{B})$$

$$S = C(A \oplus B) + \overline{C}(A \oplus B)$$

$$S = C(\overline{A} \oplus B) + \overline{C}(A \oplus B)$$

$$S = A \oplus B \oplus C$$

Logic Diagram:

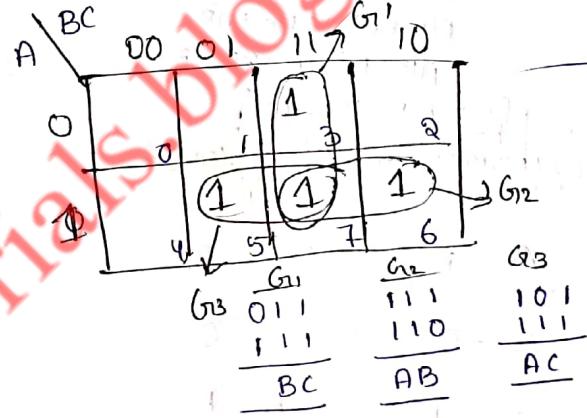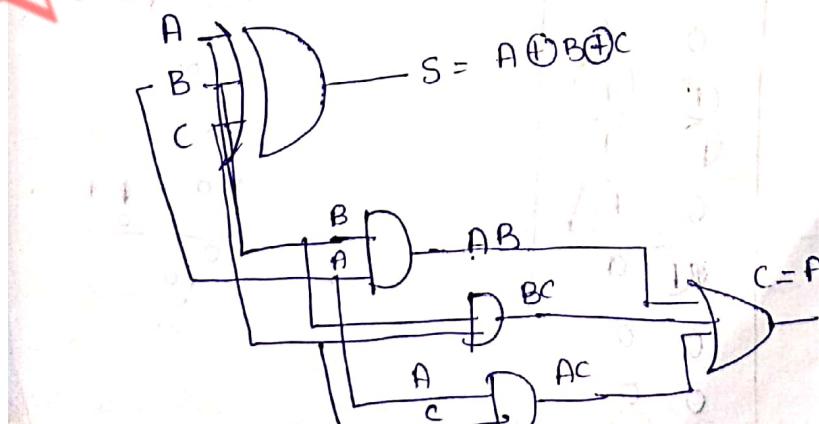


$$C = AB + BC + CA$$

$$= \cancel{ABC} + \cancel{ABC} + \cancel{ABC} + \cancel{ABC}$$

$$= \cancel{ABC} + \cancel{ABC} + \cancel{ABC} + \cancel{ABC}$$

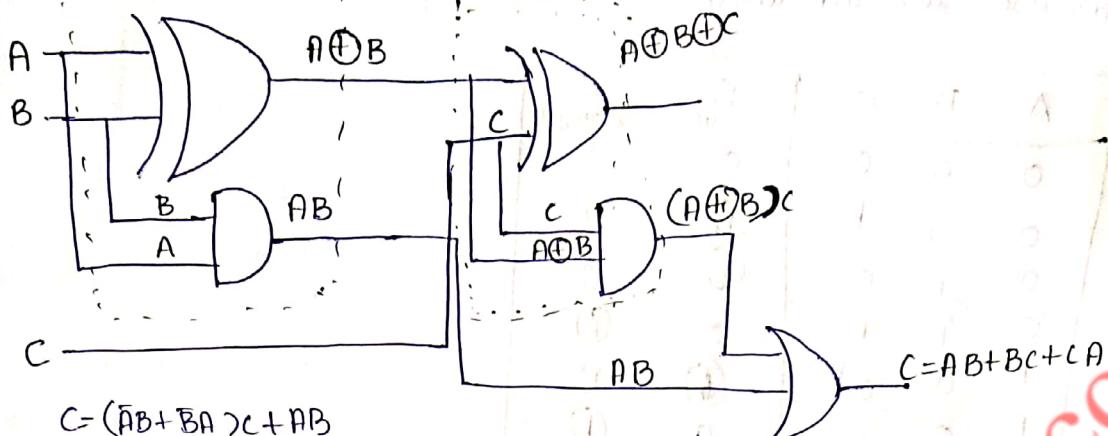* To Design full Adder by using two to-thp adders and OR gate.



$$\begin{aligned}
 C &= (\bar{A}B + \bar{B}A)C + AB \\
 &= ABC(1+C) + C(\bar{A}B + A\bar{B}) \\
 &= AB + ABC + \bar{A}BC + A\bar{B}C \\
 &= AB + \cancel{ABC}(A+\bar{A}) + A\bar{B}C \\
 &= AB + BC + \cancel{A}\bar{B}C \\
 &= AB(1+C) + BC + \bar{A}\bar{B}C \\
 &= AB + ABC + BC + \bar{A}\bar{B}C \\
 &= AB + BC + AC(B + \bar{B})
 \end{aligned}$$

Subtraction Operations:

| A | B | D | B |
|---|----|-----|---|
| 0 | -0 | = 0 | 0 |
| 0 | -1 | = 1 | 1 |
| 1 | -0 | = 1 | 0 |
| 1 | -1 | = 0 | 0 |

Full-subtraction

→ It consists of three inputs two outputs they are A,B,C & the inputs D,B & the out puts

| A | B | C | D | B |
|---|---|---|---|---|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 | 1 |
| 0 | 1 | 0 | 1 | 1 |
| 1 | 0 | 1 | 0 | 1 |
| 1 | 0 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 | 0 |
| 1 | 1 | 0 | 0 | 0 |

| | | |
|-----|----|----|
| 0-1 | 11 | 00 |
| 0 | 11 | 00 |
| 1 | 01 | 01 |
| 0 | 01 | 01 |
| 1 | 00 | 00 |

| | | K-map for D | | | |
|---|---|------------------|------------|------------|------|
| | | $\bar{B}\bar{C}$ | $\bar{B}C$ | $B\bar{C}$ | BC |
| | | 00 | 01 | 11 | 10 |
| A | 0 | 1 | 1 | 1 | 1 |
| | 1 | 1 | 1 | 1 | 1 |

$$D = \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + A\bar{B}\bar{C} + ABC$$



$$= ((\bar{A}\bar{B} + AB) + \bar{C}(\bar{A}B + A\bar{B}))$$

$$= C(A \oplus B) + \bar{C}(A \oplus B)$$

$$= C(\overline{A \oplus B}) + \bar{C}(A \oplus B)$$

$$= A \oplus B \oplus C$$

Logic diagram

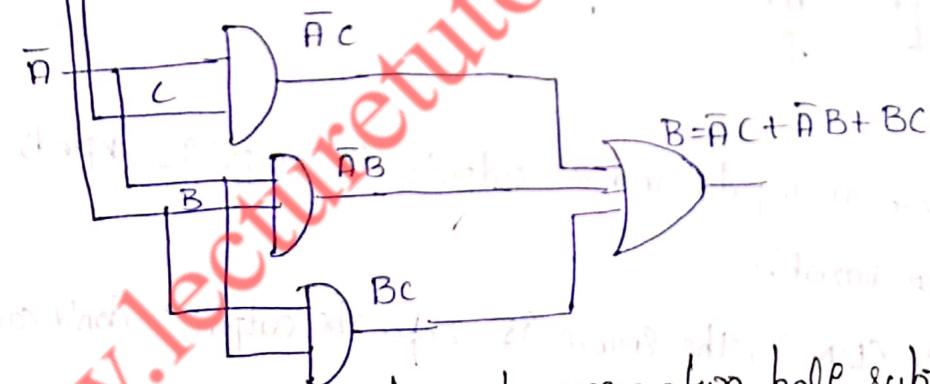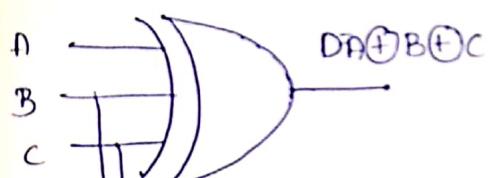

| | | K-map for B | | | |
|---|---|------------------|------------|------------|------|
| | | $\bar{B}\bar{C}$ | $\bar{B}C$ | $B\bar{C}$ | BC |
| | | 00 | 01 | 11 | 10 |
| A | 0 | 1 | 1 | 1 | 1 |
| | 1 | 0 | 1 | 1 | 1 |

$$B = \bar{A}\bar{B}\bar{C} + \bar{A}B\bar{C} + \bar{A}\bar{B}C + ABC$$


$$= \frac{G_1}{A \bar{B} C} \quad \frac{G_2}{\bar{A} \bar{B} \bar{C}} \quad \frac{G_3}{\bar{A} B \bar{C}}$$

$$\begin{array}{c} G_1 \\ \hline 0 & 0 & 1 \\ 0 & 0 & 1 \\ 0 & 1 & 1 \\ \hline \bar{A} B \end{array}$$

$$\begin{array}{c} G_2 \\ \hline 0 & 1 & 1 \\ 0 & 1 & 0 \\ 1 & 1 & 1 \\ \hline \bar{B} C \end{array}$$

$$B = \bar{A}C + \bar{A}B + BC$$

One OR gate

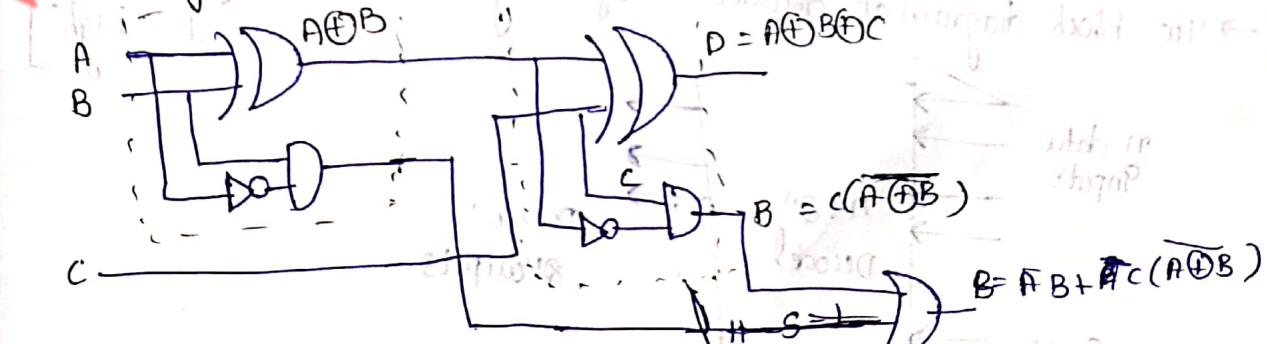

$$\begin{aligned}
 B &= c(\overline{A} \oplus B) + \bar{A}B \\
 &= c(\overline{A} \oplus B) + \bar{A}B \\
 &= c(\overline{A}\bar{B} + AB) + \bar{A}B \\
 &= \bar{A}\bar{B}c + ABC + \bar{A}B
 \end{aligned}$$

$$B = \bar{A}B + BC + \bar{A}C$$

$$\begin{aligned}
 B &= \overline{\bar{A}B} + \overline{(C \oplus B)} \\
 &= \bar{A}B + C(A \oplus B) \\
 &= \bar{A}B + C(\bar{A}\bar{B} + AB) \\
 &= \bar{A}B + (\bar{A}\bar{B} + ABC) \\
 &= \bar{A}BC(1+c) + \bar{A}\bar{B}c + ABC \\
 &= \bar{A}B + \underline{\bar{A}BC} + \underline{\bar{A}\bar{B}c} + \underline{ABC} \\
 &= \bar{A}B + BC(\bar{A} + A) + \bar{A}BC \\
 &= \bar{A}B + BC + \bar{A}BC \\
 &= \bar{A}BC(1+c) + BC + \bar{A}\bar{B}c \\
 &= \bar{A}B + \bar{A}BC + BC + \bar{A}\bar{B}c \\
 &= \bar{A}B + BC + \bar{A}C(B + \bar{B}) \\
 \boxed{B = \bar{A}B + BC + \bar{A}C}
 \end{aligned}$$


Decoder

→ The Decoder has n inputs and 2^n outputs. The output is depends upon enable input variable.

→ If the Enable is (EN), the Enable is zero the output is don't care condition.

→ If the Enable is '1' the output is on state.

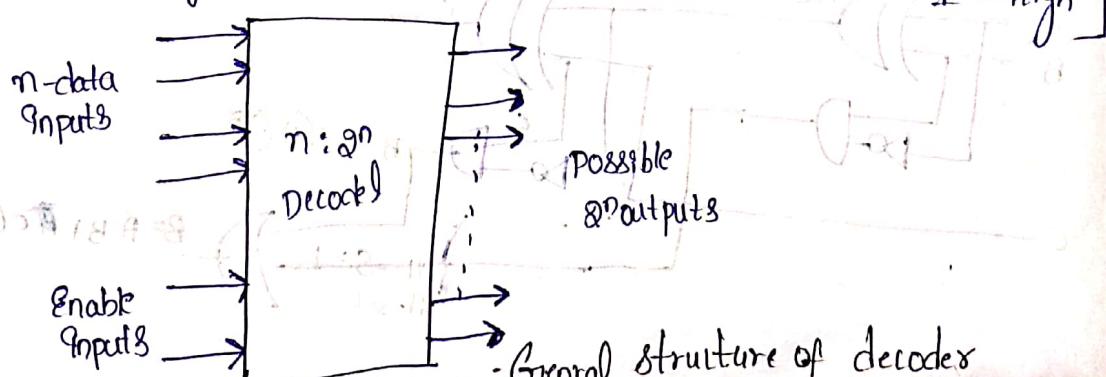→ The block diagram of decoder is given by



[0 - Low
1 - High]


Binary Decoder

time/jntukonlinebits

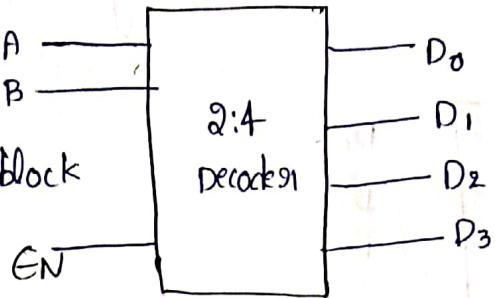2:4 Decoder:

Truth table:


The 2:4 Decoder block diagram is given by



2:4 Decoder


Truth table:

| Inputs | | | outputs | | | |
|--------|---|---|----------------|----------------|----------------|----------------|
| EN | A | B | D ₃ | D ₂ | D ₁ | D ₀ |
| 0 | X | X | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 0 | 0 | 0 | 1 |
| 1 | 0 | 1 | 0 | 0 | 1 | 0 |
| 1 | 1 | 0 | 0 | 1 | 0 | 0 |
| 1 | 1 | 1 | 1 | 0 | 0 | 0 |

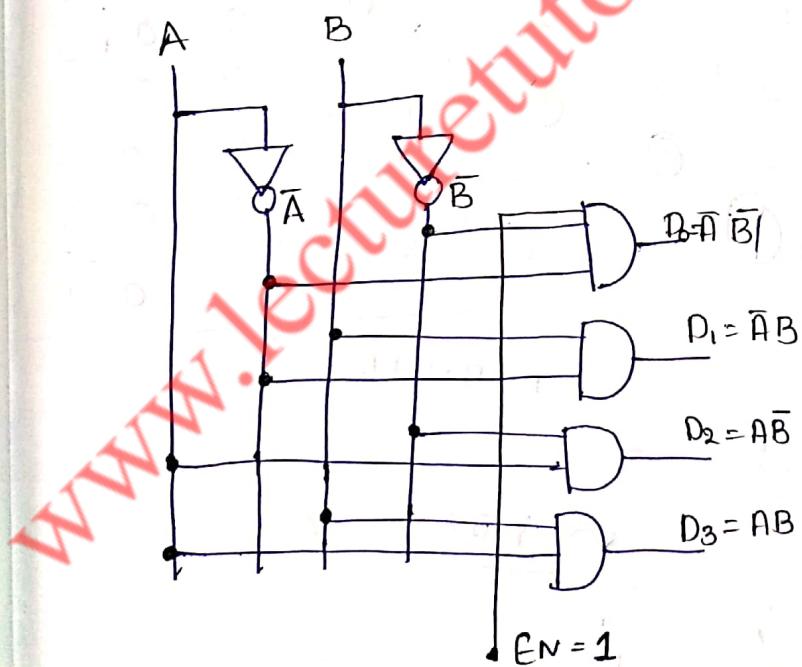


3:8 Decoder \div The 3:8 Decoder is given by


t.me/jntukonlinebits

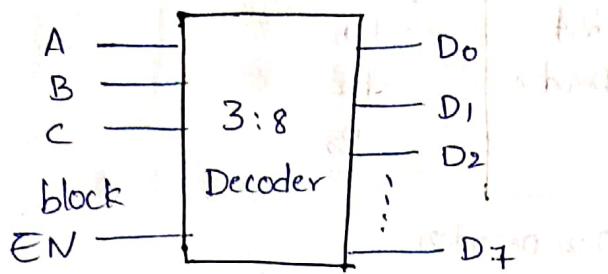


Truth Table

| Input | | | | Output | | | | | | | |
|-------|---|---|---|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|
| EN | A | B | C | D ₇ | D ₆ | D ₅ | D ₄ | D ₃ | D ₂ | D ₁ | D ₀ |
| 0 | X | X | X | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 |
| 1 | 0 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 1 | 0 | 1 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 0 |
| 1 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 1 | 1 | 0 | 1 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 0 |
| 1 | 1 | 1 | 0 | 0 | 0 | 1 | 0 | 0 | 0 | 0 | 0 |
| 1 | 1 | 1 | 1 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |

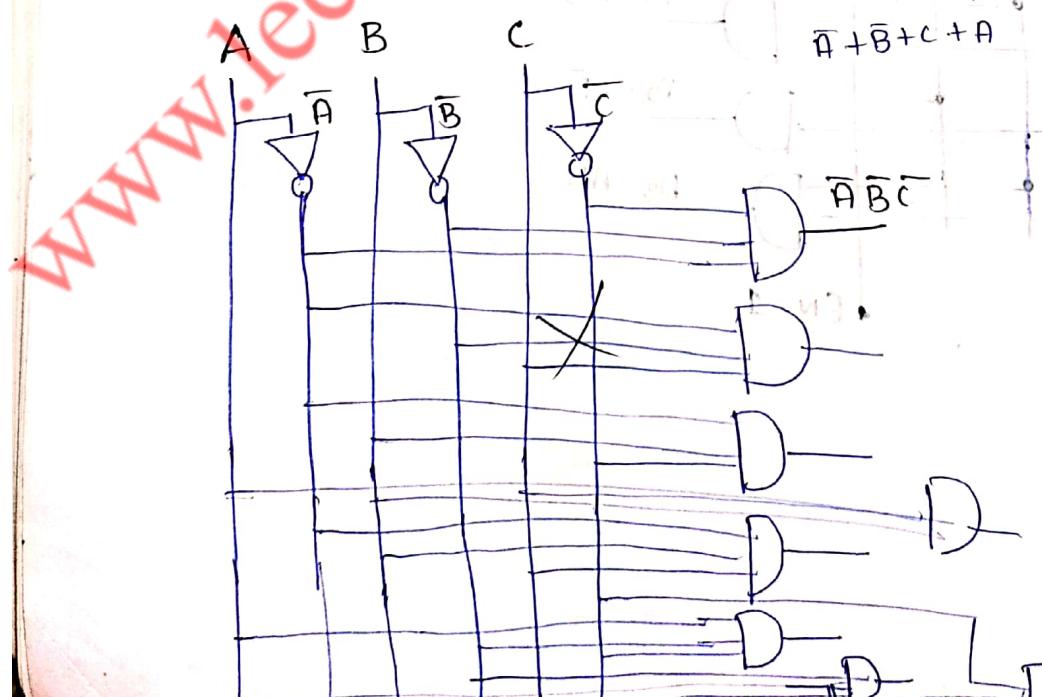

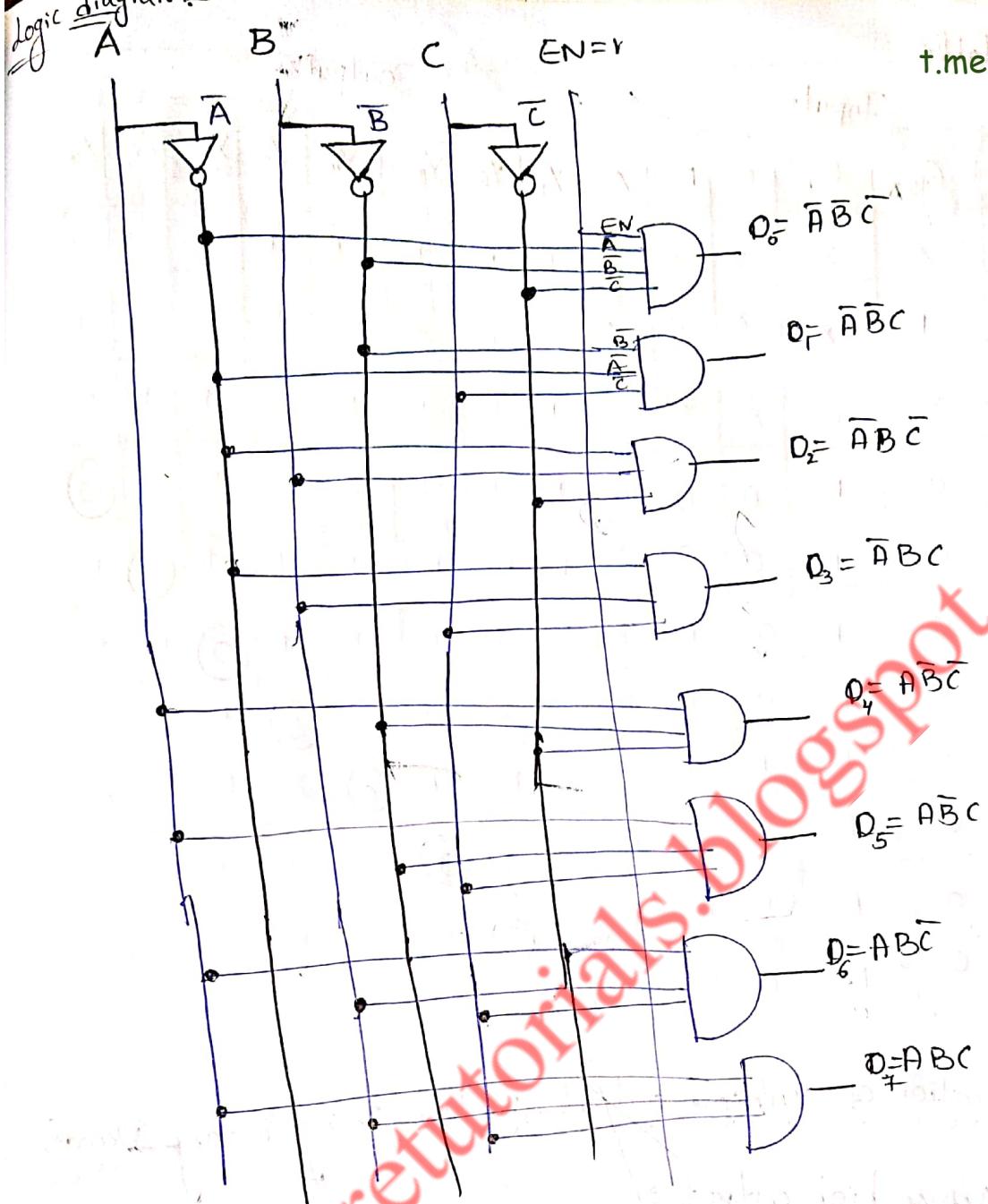

The 74x138 3 to 8 Decoder
=

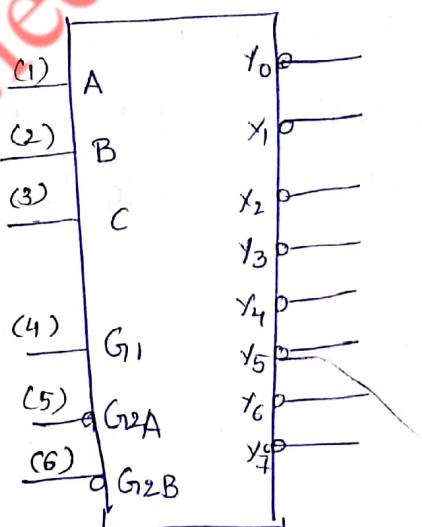

Logic symbol

| Inputs | | | | | | outputs | | | | | | | |
|----------|----------|-------|---|---|---|-------------|-------------|-------------|-------------|-------------|-------------|-------------|-------------|
| G_{12} | G_{12} | G_1 | C | B | A | \bar{Y}_1 | \bar{Y}_6 | \bar{Y}_5 | \bar{Y}_4 | \bar{Y}_3 | \bar{Y}_2 | \bar{Y}_1 | \bar{Y}_0 |
| 1 | x | x | x | x | x | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 |
| x | 1 | x | x | x | x | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 |
| x | x | 0 | x | x | x | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 |
| 0 | 0 | 1 | 0 | 0 | 0 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 0 |
| 0 | 0 | 1 | 0 | 0 | 0 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 0 |
| 0 | 0 | 1 | 0 | 1 | 0 | 1 | 1 | 1 | 1 | 1 | 1 | 0 | 1 |
| 0 | 0 | 1 | 0 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 0 | 1 |
| 0 | 0 | 1 | 1 | 0 | 0 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 |
| 0 | 0 | 1 | 1 | 0 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 |
| 0 | 0 | 1 | 1 | 1 | 0 | 1 | 1 | 1 | 1 | 1 | 1 | 1 | 1 |
| 0 | 0 | 1 | 1 | 1 | 1 | 0 | 1 | 1 | 1 | 1 | 1 | 1 | 1 |
| 0 | 0 | 1 | 1 | 1 | 1 | 0 | 1 | 1 | 1 | 1 | 1 | 1 | 1 |

Realization of Multiple output function using Binary Decodes,


For Active high output :-

Sop function implementation

When decoder output is active high, it generates minterms (product terms) for input variables i.e. it makes selected output logic 1.

In such case to implement Sop function we have to take sum of selected product terms generated by decoder. This can be implemented by ORing the selected decoder outputs, as shown in the fig 5.62. The fig 5.62 shows the implementation of function $f = \sum M(1, 2, 3, 7)$ using 3:8 decoder with active high outputs.


0 - low - off state
1 - high - on

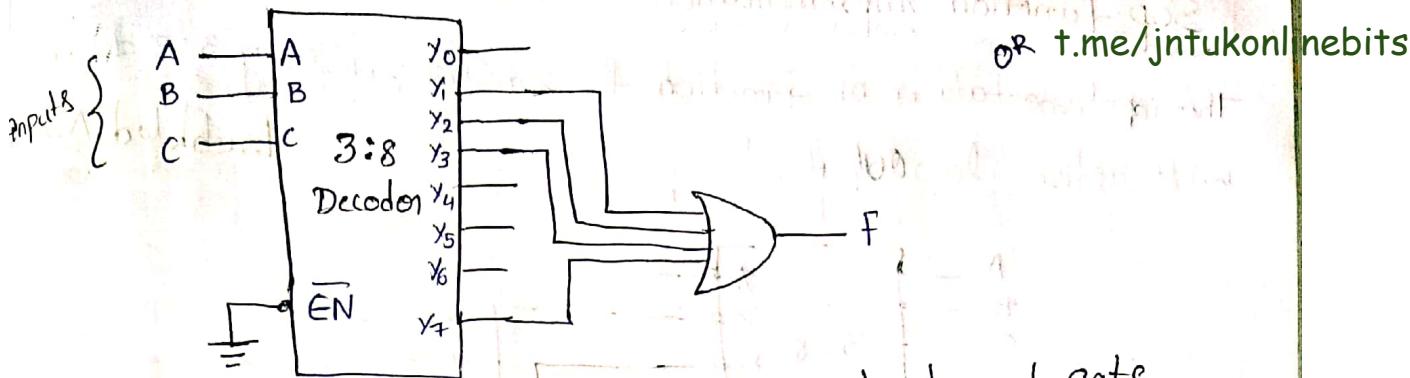

Single output function implementation using decoder and gate

POS Function Implementation

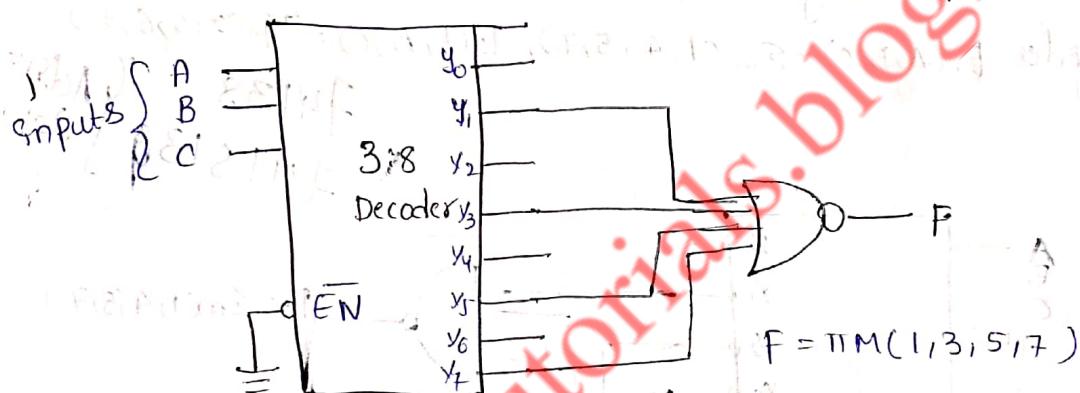The implementation of a function $f = \prod M(1,3,5,7)$ using 3:8 decoder with active high outputs.




Implementation of pos function using decoders

for Active low Output

= POS function implementation

The implementation of function $f = \prod M(1,3,5,7)$ using 3:8 decoder with active low outputs

Bubbled AND

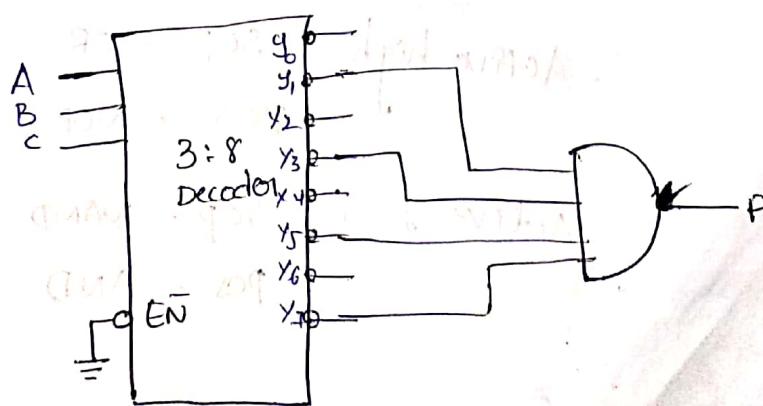


Implementation of pos function using decoders

SOP function implementation

<https://t.me/jntukonlinebits>

the implementation of function $f = \sum m(1, 2, 5, 7)$ using 3:8 decoder with active low outputs


Bubbled NAND Gate

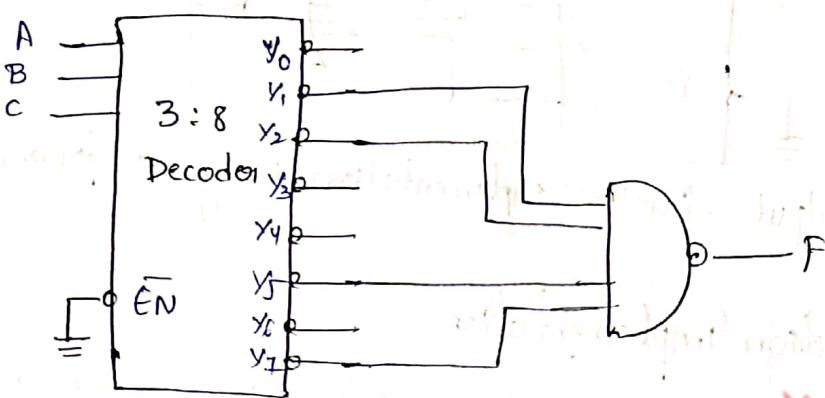

Implementation of SOP function using decoder

Ex: Implement following multiple output function using 74LS138 and external gates. $F_1(A, B, C) = \sum m(1, 4, 5, 7)$; $F_2(E, B, C) = \sum m(2, 3, 6, 7)$

74138 {Active
74LS138 } Low

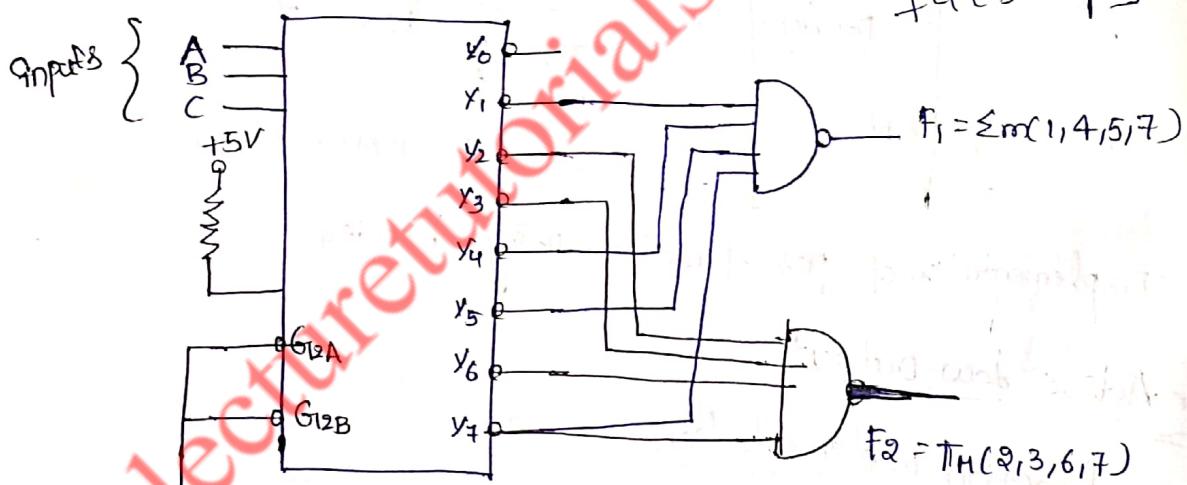

Active high - SOP - OR
POS - NOR


Active low - SOP - NAND
POS - AND

Encoder ($2^n q/p - n o/p$)

t.me/jntukonlinebits

→ The Encoder qt consists of 2^n inputs and n outputs

Block diagram:

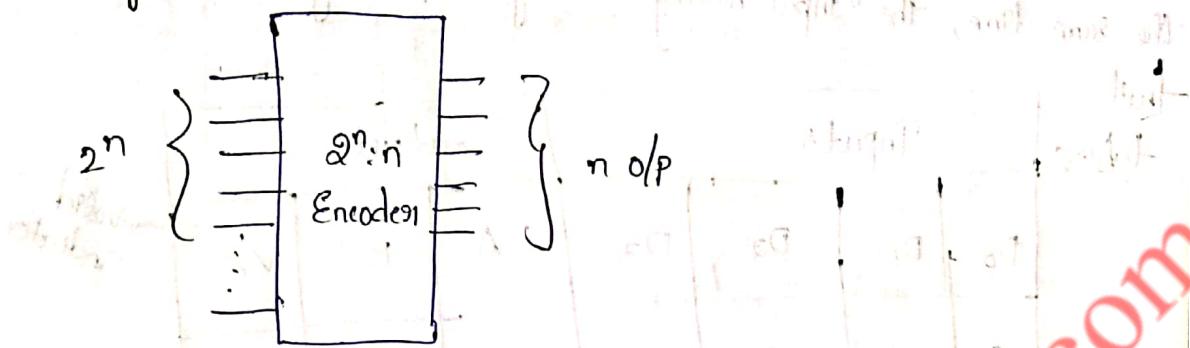

Ex 4

Octal - Binary Encoder

truth-table


→ The truth table of octal to binary converter

| Inputs | | | | | | | | Outputs | | |
|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|---------|---|---|
| D ₀ | D ₁ | D ₂ | D ₃ | D ₄ | D ₅ | D ₆ | D ₇ | A | B | C |
| 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 0 |
| 0 | 0 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 |
| 0 | 0 | 0 | 1 | 0 | 0 | 0 | 0 | 1 | 0 | 0 |
| 0 | 0 | 0 | 0 | 1 | 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 0 | 0 | 1 |
| 0 | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 1 | 0 |
| 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 1 | 0 |
| 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 1 |
| 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 1 |

$$A = D_4 + D_5 + D_6 + D_7$$

$$B = D_2 + D_3 + D_6 + D_7$$

$$C = D_1 + D_3 + D_5 + D_7$$

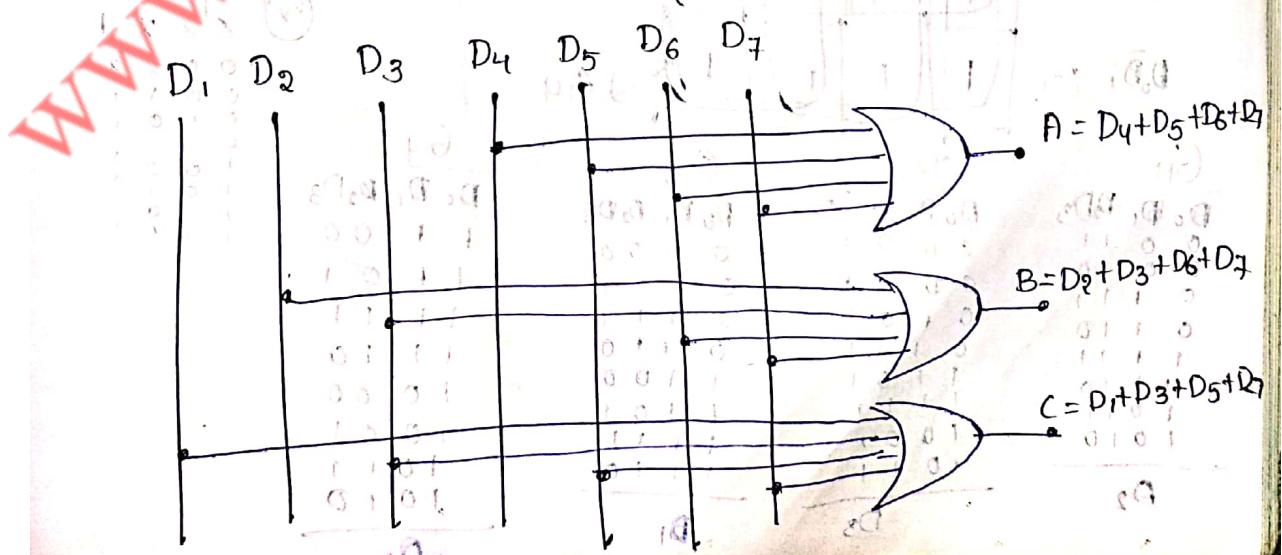

$$A = D_4 + D_5 + D_6 + D_7$$

$$B = D_2 + D_3 + D_6 + D_7$$

$$C = D_1 + D_3 + D_5 + D_7$$

Priority Encoders

t.me/jntukonlinebits


A priority encoder is an encoder circuit that includes the priority function. In priority encoder, if two or more inputs are equal to 1 at the same time, the input having the highest priority will take precedence.

truth

table:

| Inputs | | | | outputs | | | Valid indicator |
|----------------|----------------|----------------|----------------|---------|---|---|-----------------|
| D ₀ | D ₁ | D ₂ | D ₃ | A | B | | |
| 0 | 0 | 0 | 0 | x | x | 0 | |
| 1 | 0 | 0 | 0 | 0 | 0 | 1 | |
| x | 1 | 0 | 0 | 0 | 1 | 1 | |
| x | x | 1 | 0 | 1 | 0 | 1 | |
| x | x | x | 1 | 1 | 1 | 1 | |

four variable k-map - V

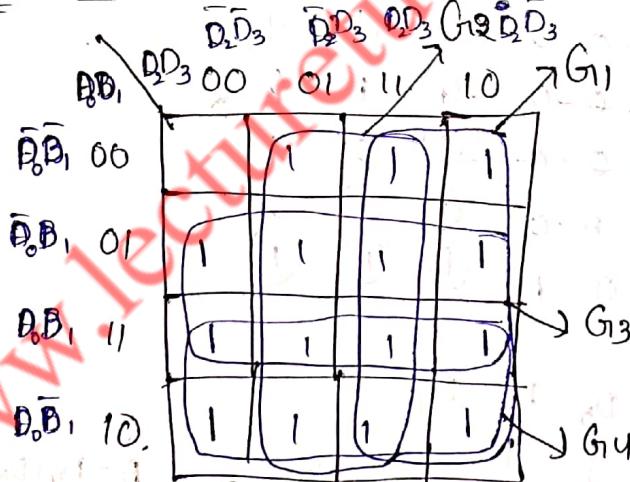

$$\begin{array}{l} G_1 \\ \hline D_0 D_1 D_2 D_3 \\ \hline 0 0 1 1 \\ 0 0 1 0 \\ 0 1 1 1 \\ 0 1 1 0 \\ 1 1 1 1 \\ 1 1 1 0 \\ 1 0 1 1 \\ 1 0 1 0 \end{array}$$

$$\begin{array}{l} G_2 \\ \hline D_0 D_1 D_2 D_3 \\ \hline 0 0 0 1 \\ 0 0 1 1 \\ 0 1 0 1 \\ 0 1 1 1 \\ 1 1 0 1 \\ 1 1 1 1 \\ 1 0 1 1 \\ 1 0 1 0 \end{array}$$

$$\begin{array}{l} G_3 \\ \hline D_0 D_1 D_2 D_3 \\ \hline 0 1 0 0 \\ 0 1 0 1 \\ 0 1 1 1 \\ 0 1 1 0 \\ 1 1 0 0 \\ 1 1 0 1 \\ 1 1 1 1 \\ 1 1 1 0 \end{array}$$

$$\begin{array}{l} G_4 \\ \hline D_0 D_1 D_2 D_3 \\ \hline 1 1 0 0 \\ 1 1 0 1 \\ 1 1 1 1 \\ 1 1 1 0 \\ 1 0 0 0 \\ 1 0 0 1 \\ 1 0 1 1 \\ 1 0 1 0 \end{array}$$

$$\begin{array}{l} D_2 \\ \hline D_3 \\ \hline 0 \\ 1 \\ 1 \\ 0 \\ 1 \\ 0 \\ 0 \\ 1 \end{array}$$


$$\begin{array}{l} D_3 \\ \hline D_2 \\ \hline 0 \\ 1 \\ 1 \\ 0 \\ 1 \\ 0 \\ 0 \\ 1 \end{array}$$

$$\begin{array}{l} D_2 \\ \hline D_1 \\ \hline 0 \\ 1 \\ 1 \\ 0 \\ 1 \\ 0 \\ 0 \\ 1 \end{array}$$

$$\begin{array}{l} D_1 \\ \hline D_0 \\ \hline 0 \\ 1 \\ 1 \\ 0 \\ 1 \\ 0 \\ 0 \\ 1 \end{array}$$

$$V = D_0 + D_1 + D_2 + D_3$$


K-map for "A"

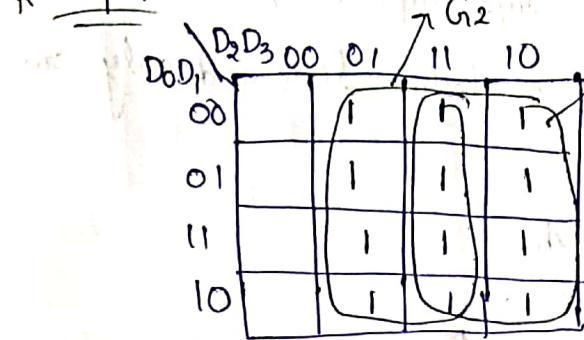

| | | G ₁ | G ₂ | G ₃ | G ₄ |
|--|--|----------------|----------------|----------------|----------------|
| | | D ₀ | D ₁ | D ₂ | D ₃ |
| | | 0 | 0 | 0 | 0 |
| | | 0 | 0 | 0 | 0 |
| | | 0 | 1 | 0 | 0 |
| | | 0 | 1 | 1 | 0 |
| | | 0 | 1 | 1 | 1 |
| | | 0 | 1 | 0 | 1 |
| | | 0 | 1 | 0 | 0 |
| | | 1 | 1 | 1 | 0 |
| | | 1 | 1 | 1 | 1 |
| | | 1 | 1 | 0 | 1 |
| | | 1 | 1 | 0 | 0 |
| | | 1 | 0 | 1 | 1 |
| | | 1 | 0 | 1 | 0 |
| | | 1 | 0 | 0 | 1 |
| | | 1 | 0 | 0 | 0 |
| | | 1 | 1 | 0 | 0 |
| | | 1 | 1 | 0 | 0 |
| | | 1 | 1 | 1 | 0 |
| | | 1 | 1 | 1 | 1 |
| | | 1 | 0 | 0 | 1 |
| | | 1 | 0 | 0 | 0 |
| | | 1 | 1 | 0 | 0 |
| | | 1 | 1 | 1 | 0 |
| | | 1 | 1 | 1 | 1 |
| | | 1 | 0 | 1 | 0 |
| | | 1 | 0 | 1 | 1 |
| | | 1 | 1 | 0 | 0 |
| | | 1 | 1 | 1 | 0 |
| | | 1 | 1 | 1 | 1 |

$$A = D_2 + D_3$$


K-map for "B"

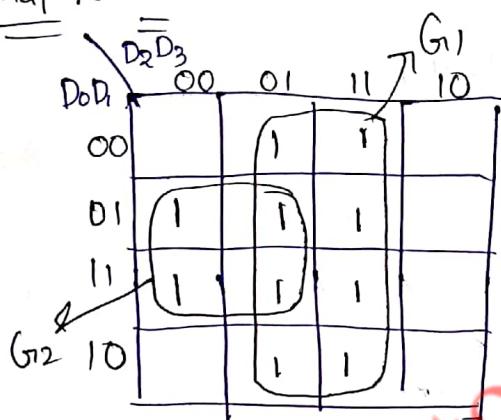

$$B = D_3 + \overline{D_1} \overline{D_2}$$


| | | G ₁ | G ₂ | G ₃ | G ₄ |
|--|--|----------------|----------------|----------------|----------------|
| | | D ₀ | D ₁ | D ₂ | D ₃ |
| | | 0 | 0 | 0 | 0 |
| | | 0 | 0 | 0 | 0 |
| | | 0 | 1 | 0 | 0 |
| | | 0 | 1 | 1 | 0 |
| | | 0 | 1 | 1 | 1 |
| | | 0 | 1 | 0 | 1 |
| | | 0 | 1 | 0 | 0 |
| | | 1 | 1 | 1 | 0 |
| | | 1 | 1 | 1 | 1 |
| | | 1 | 1 | 0 | 1 |
| | | 1 | 1 | 0 | 0 |
| | | 1 | 0 | 1 | 1 |
| | | 1 | 0 | 1 | 0 |
| | | 1 | 1 | 0 | 1 |
| | | 1 | 1 | 1 | 0 |
| | | 1 | 1 | 1 | 1 |
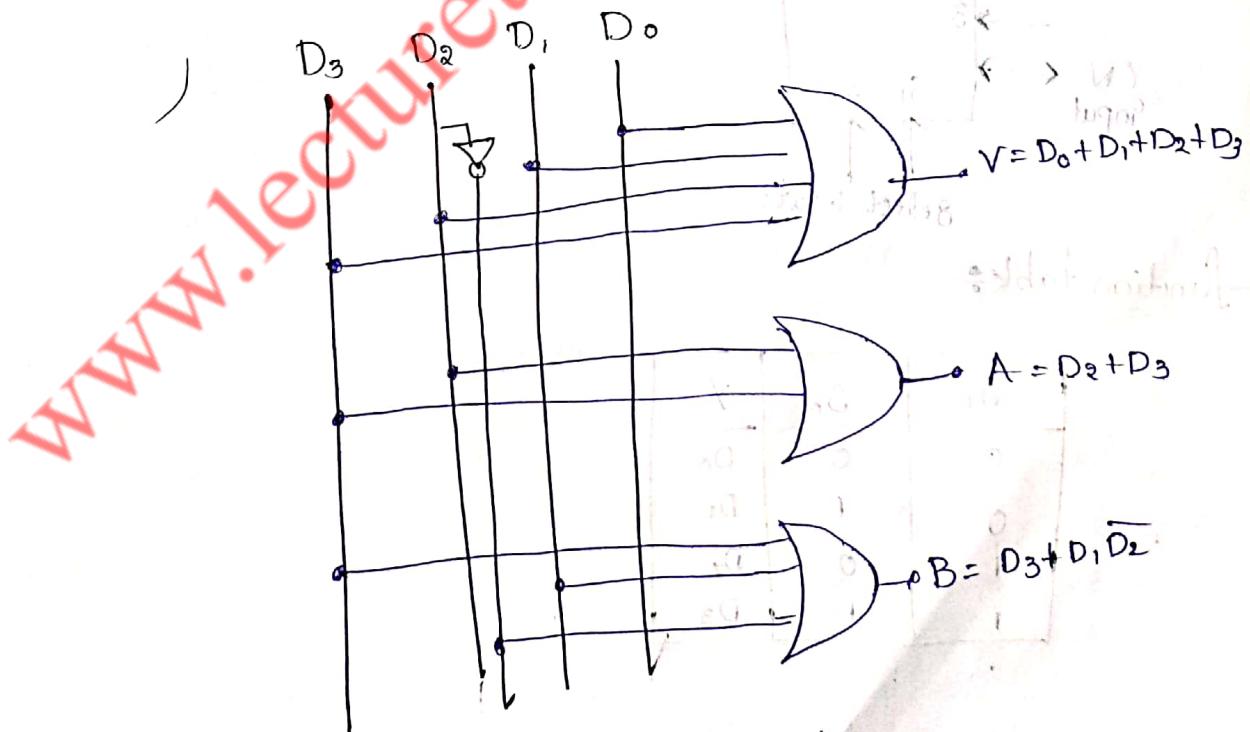
$$B = D_3 + \overline{D_1} \overline{D_2}$$



Multiplexers (2^n inputs - n selection lines \rightarrow 1 output) t.me/jntukonlinebits

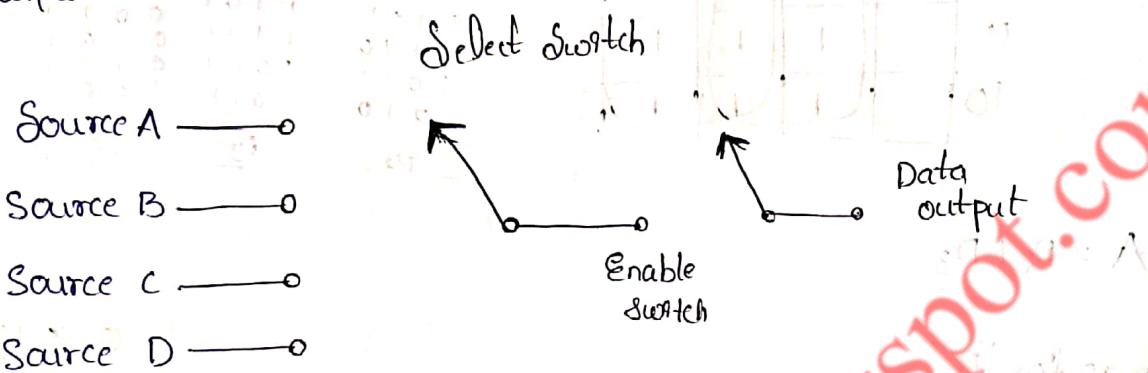
Multiplexer is a digital switch. It allows digital information from several sources to be routed onto a single output line. It consists of 2^n input lines and n selection lines and only one output.



Analog selector switch


4 to 1 line multiplexer

Logic symbol:

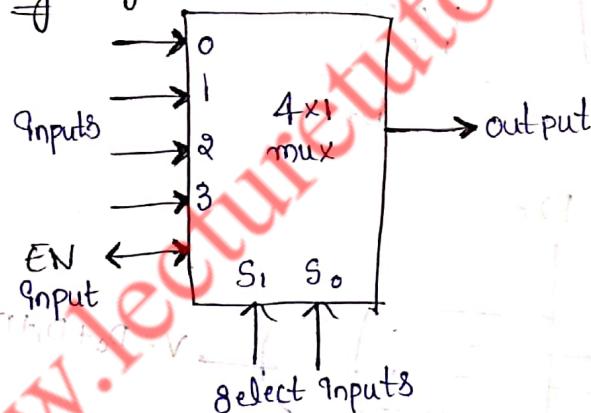

function table:


| S_1 | S_0 | y |
|-------|-------|-------|
| 0 | 0 | D_0 |
| 0 | 1 | D_1 |
| 1 | 0 | D_2 |
| 1 | 1 | D_3 |

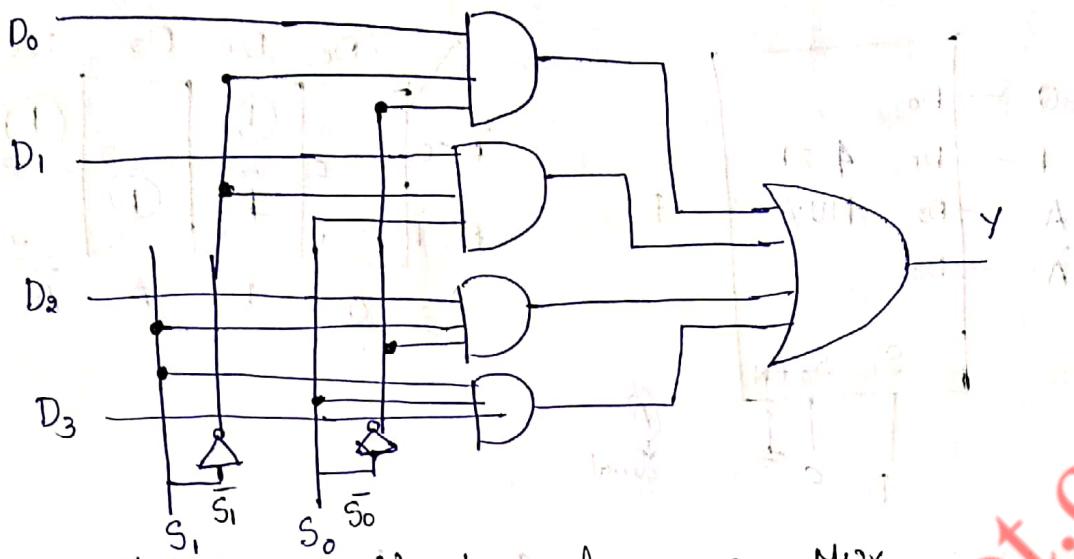

Implementation of combinational logic using MUX

Ex: Implement the following Boolean function using 8:1 multiplexer

$$F(A, B, C) = \sum m(1, 3, 5, 6)$$

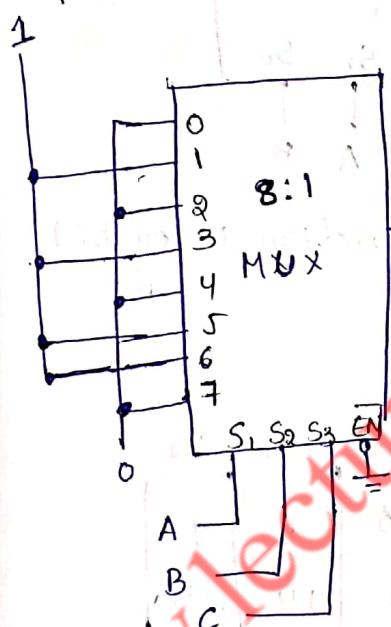

Boolean function implementation using MUX


Ex: Implement the following Boolean function 4:1 multiplexer

$$F(A, B, C) = \sum m(1, 3, 5, 6)$$

truth table

| minterm | A | B | C | F |
|---------|---|---|---|---|
| 0 | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 1 | 1 |
| 2 | 0 | 1 | 0 | 0 |
| 3 | 0 | 1 | 1 | 1 |
| 4 | 1 | 0 | 0 | 0 |
| 5 | 1 | 0 | 1 | 1 |
| 6 | 1 | 1 | 0 | 1 |
| 7 | 1 | 1 | 1 | 0 |

Multiplexer Implementation

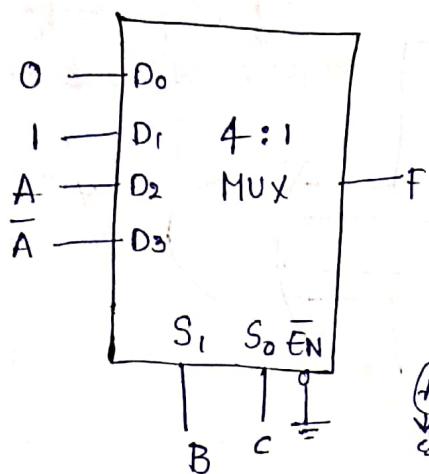


Implementation table
 $F = \sum m(1, 3, 5, 6)$

| | D_0 | D_1 | D_2 | D_3 |
|-------|-------|-------|-------|-----------|
| $A=0$ | 1 | 0 | 1 | 0 |
| $A=1$ | 0 | 1 | 1 | 1 |
| | 4 | 5 | 6 | 7 |
| | 0 | 1 | A | \bar{A} |


Case 2

| \bar{C} | C | D_0 |
|-----------|-----|-------|
| C | 0 | 1 |
| C | 2 | 3 |
| C | 4 | 5 |
| \bar{C} | 6 | 7 |

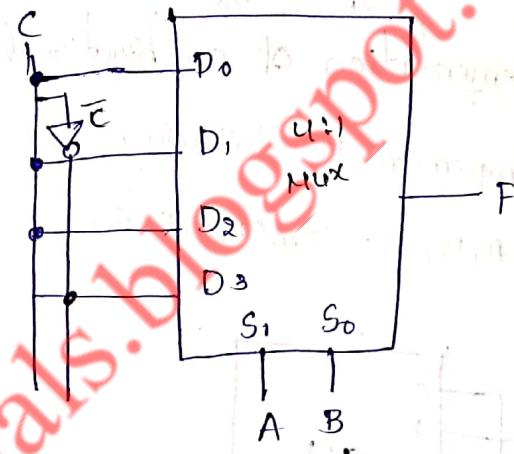


Ex: Implement the following Boolean function using 8:1 Mux. $F(P, Q, R, S) = \sum m(0, 1, 3, 4, 8, 9, 15)$

| | D_0 | D_1 | D_2 | D_3 | D_4 | D_5 | D_6 | D_7 |
|-----------|-------|-------|-------|-------|-------|-------|-------|-------|
| \bar{P} | 0 | 1 | 0 | 1 | 0 | 1 | 0 | 1 |
| P | 1 | 0 | 1 | 0 | 1 | 0 | 1 | 0 |

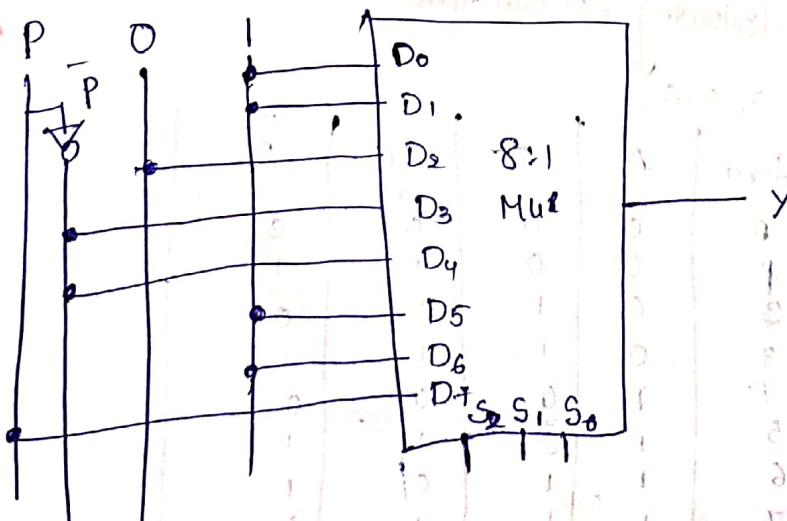


| D ₀ | D ₁ | D ₂ | D ₃ | D ₄ | D ₅ | D ₆ | D ₇ |
|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|
| 0 | 1 | 2 | 3 | 4 | 5 | 6 | 7 |
| 8 | 9 | 10 | 11 | 12 | 13 | 14 | 15 |
| 0 | A | 0 | 1 | A | A | A | A |

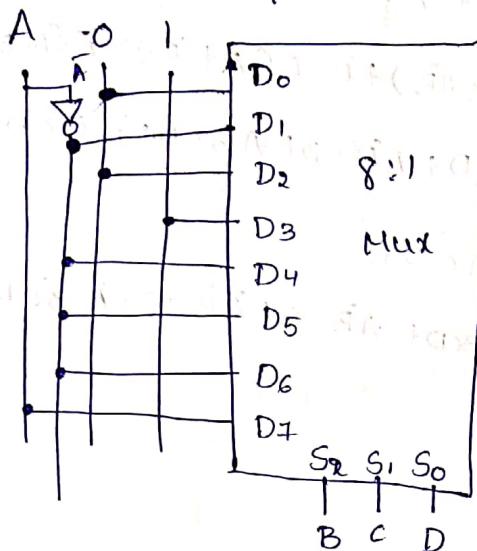Implementation tableMultiplexer Implementation

* Implement the following Boolean function using 8:1 multiplexer
 $F(A, B, C, D) = \overline{\text{M}}(0, 3, 8, 5, 9, 10, 12, 14)$

Here, instead of minterms, maxterms are specified
 Thus, we have to circle maxterms which are not included
 In the Boolean function shown below

| D ₀ | D ₁ | D ₂ | D ₃ | D ₄ | D ₅ | D ₆ | D ₇ | |
|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----|
| A | 0 | 1 | 2 | 3 | 4 | 5 | 6 | 7 |
| A | 8 | 9 | 10 | 11 | 12 | 13 | 14 | 15 |
| 0 | A | A | A | A | A | A | A | A |

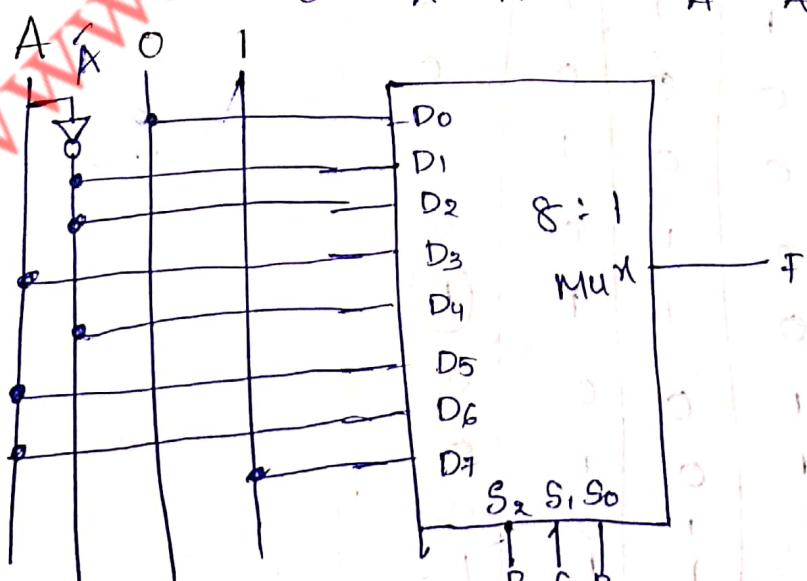


Implement the following Boolean function with 8:1 Multiplexer
t.me/jntukonlinebits

$$F(A, B, C, D) = \sum m(0, 2, 6, 10, 11, 12, 13) + d(3, 8, 14)$$

Sol:

| | D ₀ | D ₁ | D ₂ | D ₃ | D ₄ | D ₅ | D ₆ | D ₇ |
|---|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|
| A | 0 | 1 | 2 | 3 | 4 | 5 | 6 | 7 |
| A | 8 | 9 | 10 | 11 | 12 | 13 | 14 | 15 |


Here don't care's are treated as 1's

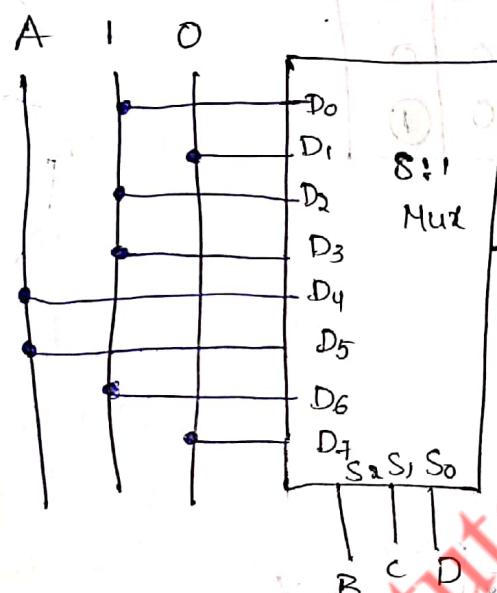

Demultiplexer (1 input - n selection lines - 2ⁿ outputs)

1 : 4 Demux

= logic symbol:

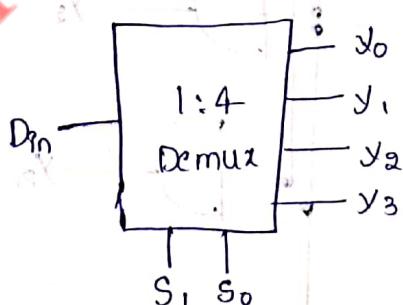

Enable (0) - Inputs are Don't care
outputs are zero


truth table:

t.me/jntukonlinebits

| Enable | S_1 | S_0 | D_{in} | y_0 | y_1 | y_2 | y_3 |
|--------|-------|-------|----------|-------|-------|-------|-------|
| 0 | x | x | x | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 1 | 1 | 0 | 0 | 0 |
| 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 1 | 0 | 1 | 1 | 0 | 1 | 0 | 0 |
| 1 | 1 | 0 | 0 | 0 | 0 | 0 | 0 |
| 1 | 1 | 0 | 1 | 0 | 0 | 1 | 0 |
| 1 | 1 | 1 | 0 | 0 | 0 | 0 | 0 |
| 1 | 1 | 1 | 1 | 0 | 0 | 0 | 1 |

1:4 demultiplexer

Logic diagram

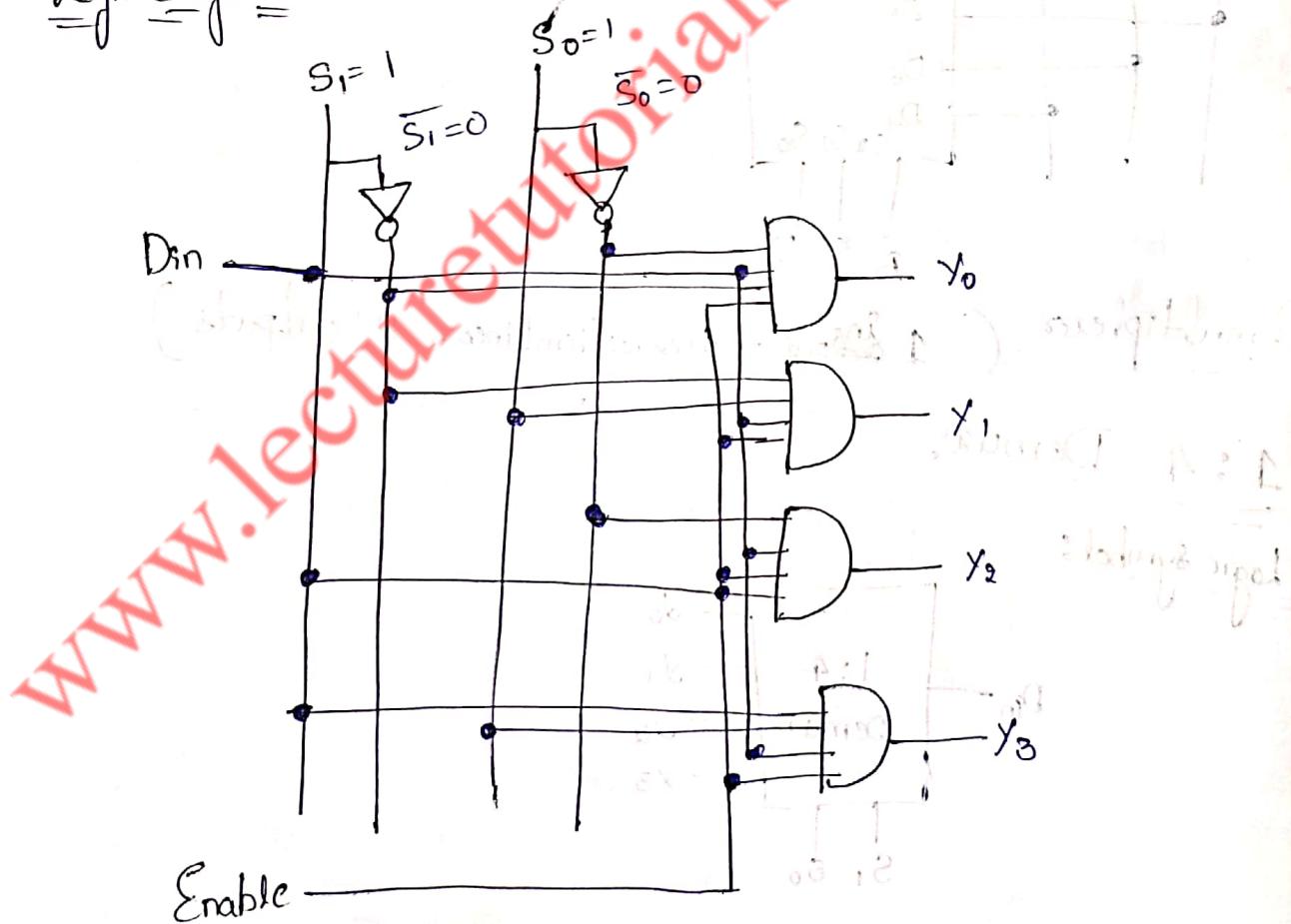

Enable

Ex: Implement the full subtractor by using demultiplexor

t.me/intukononlinebits

Sol:


| A | B | C | D Difference | B Borrow |
|---|---|---|-----------------|-------------|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 | 1 |
| 0 | 1 | 0 | 1 | 1 |
| 0 | 1 | 0 | 0 | 0 |
| 1 | 0 | 0 | 1 | 0 |
| 1 | 0 | 1 | 0 | 0 |
| 1 | 1 | 0 | 0 | 0 |
| 1 | 1 | 1 | 1 | 1 |

truth table of full subtractor

$$D = \sum m(1, 2, 4, 7)$$

$$B = \sum m(1, 2, 3, 7)$$

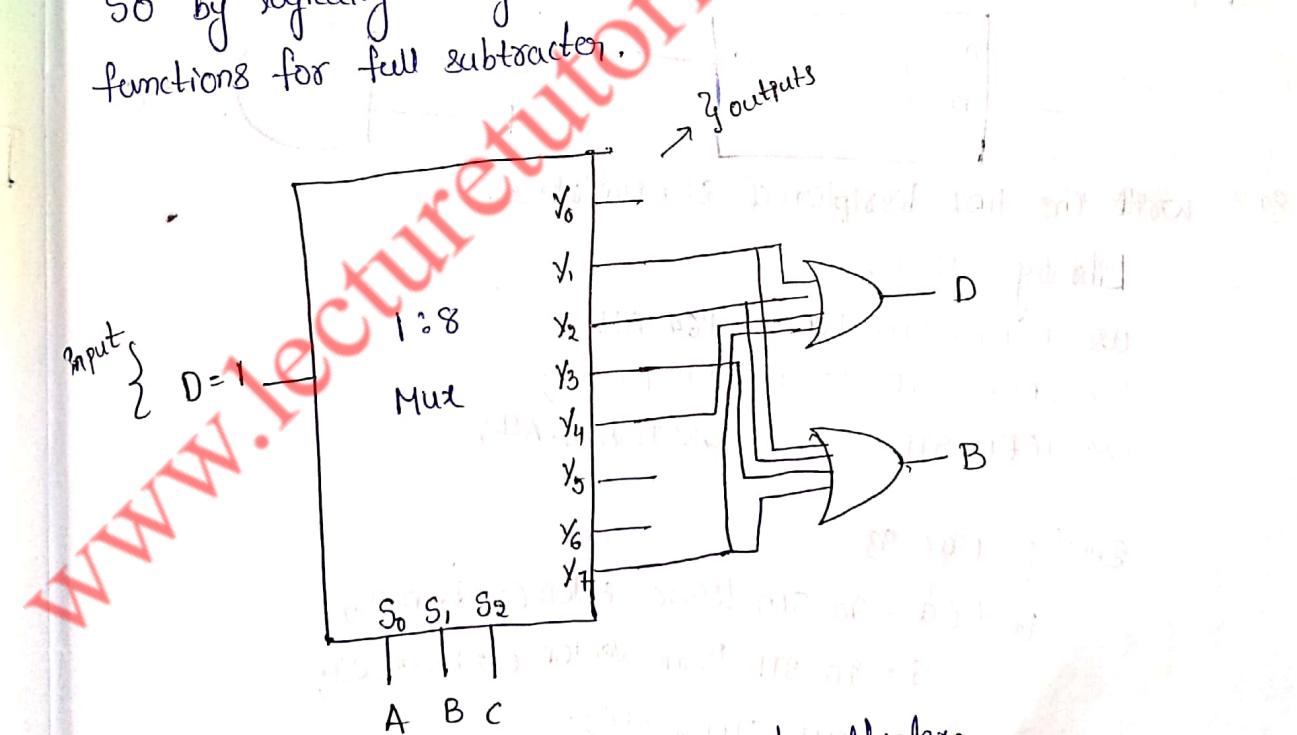With D as input 1, demultiplexer gives minterms at the output. So by logically ORing required minterms we can implement Boolean functions for full subtractor.



Full subtractor using 1:8 demultiplexer

Ex: write the HDL description of AND gate

```
Library IEEE;  
use IEEE.STD_LOGIC_1164.ALL;  
use IEEE.STD_LOGIC_UNSIGNED.ALL;
```

```
entity andgate is
```

```
port (a,b : in STD_LOGIC;
```

```
c : out STD_LOGIC);
```

```
end andgate;
```


```
architecture Behavioral of andgate is
```

```
begin
```

```
c<=a and b;
```

```
end Behavioral;
```

Output:

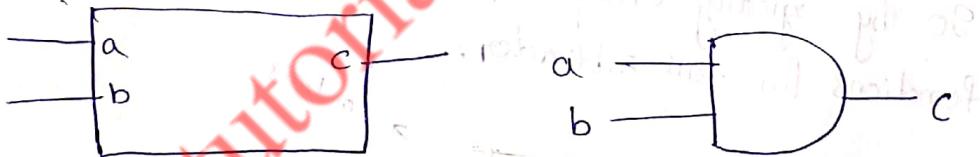

Ex: write the HDL description of 8:1 Multiplexer

```
Library IEEE;  
use IEEE.STD_LOGIC_1164.ALL;  
use IEEE.STD_LOGIC_UNSIGNED.ALL;
```

```
entity MUX is
```

```
port (a : in STD_LOGIC_VECTOR(7 downto 0);  
s : in STD_LOGIC_VECTOR(2 downto 0);  
v : out STD_LOGIC);
```

```
end MUX;
```

```
architecture Behavioral of MUX is
```

```
begin  
y <= a(0) when s = "000" else  
a(1) when s = "001" else
```

```
a(2) when s = "010" else
```

```
a(3) when s = "011" else
```

```
a(4) when s = "100" else
```

```
a(5) when s = "101" else
```



```
a(6) when s = "110" else
```

```
a(7) when s = "111" else
```

- a(2) when $s = "010"$ else
- a(3) when $s = "011"$ else
- a(4) when $s = "100"$ else
- a(5) when $s = "101"$ else
- a(6) when $s = "110"$ else
- a(7) when $s = "111"$;

end Behavioral;

Output:

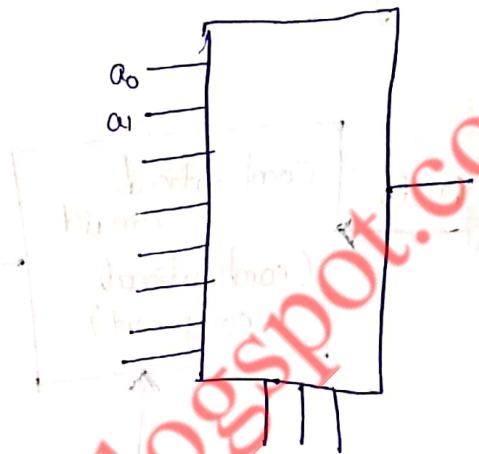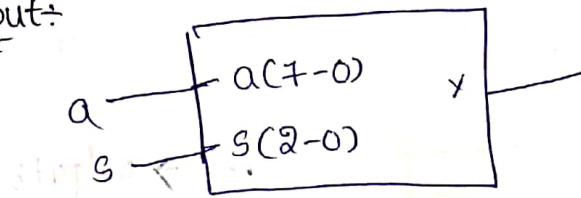

Ques. (19)

Design a state transition logic to implement a 4-bit adder with 2-bit carry.

Ans. State transition logic for 4-bit adder with 2-bit carry.

Date
5/8/19

Unit - V


t.me/jntukonlinebits

Synchronous Sequential Logic


Logic Circuit (ckt)

Combinational logical ckt Sequential logic ckt

Ex:

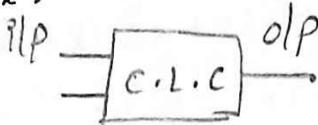



Ex: previous

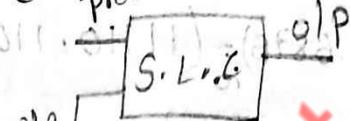


present

(NAND)


Basic Construction of S-R Flip Flop

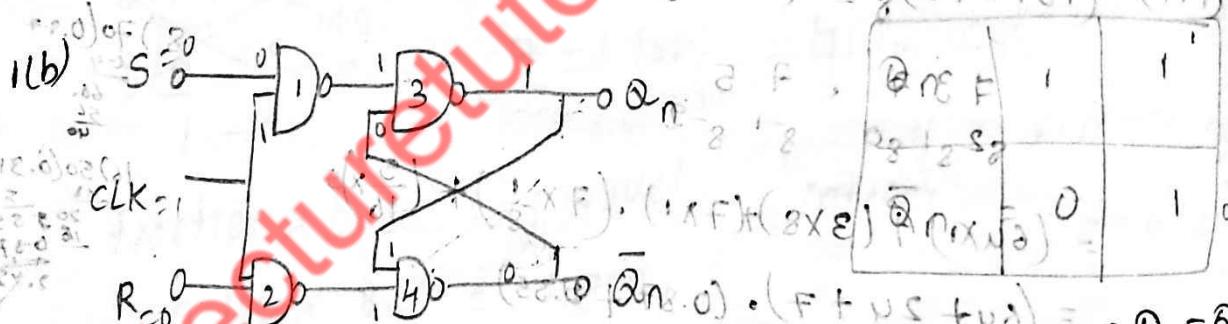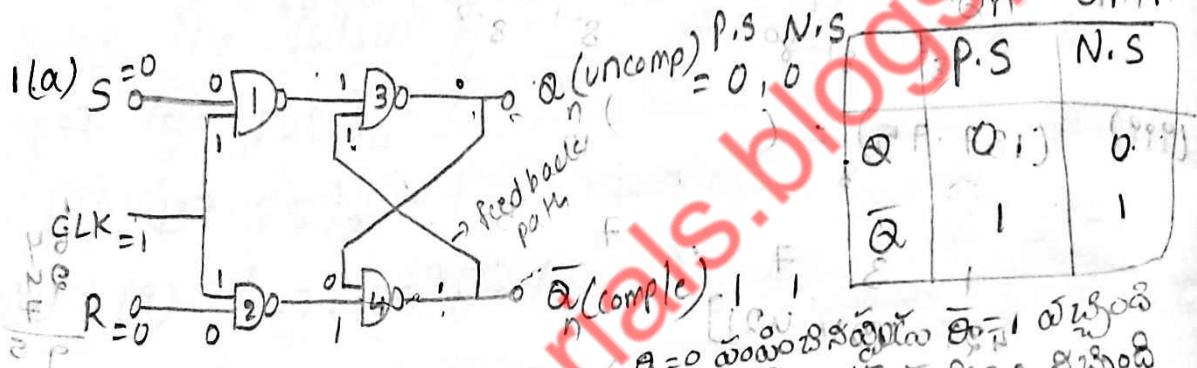


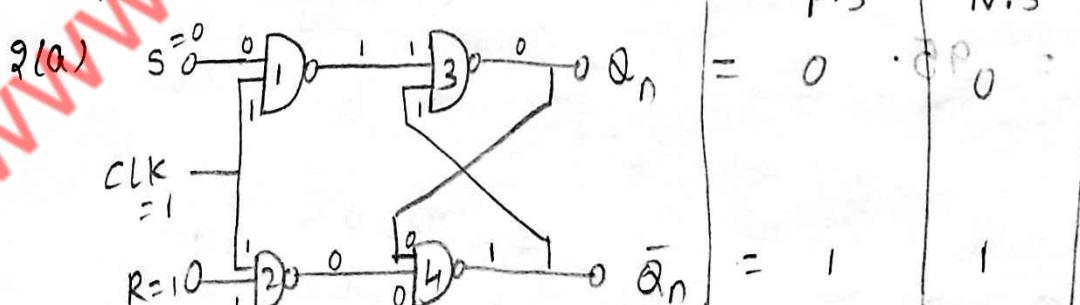1(a) & 1(b) are no change condition $P.S = N.S \Rightarrow Q_n = Q_{n+1}$




Reset condition (output=0)

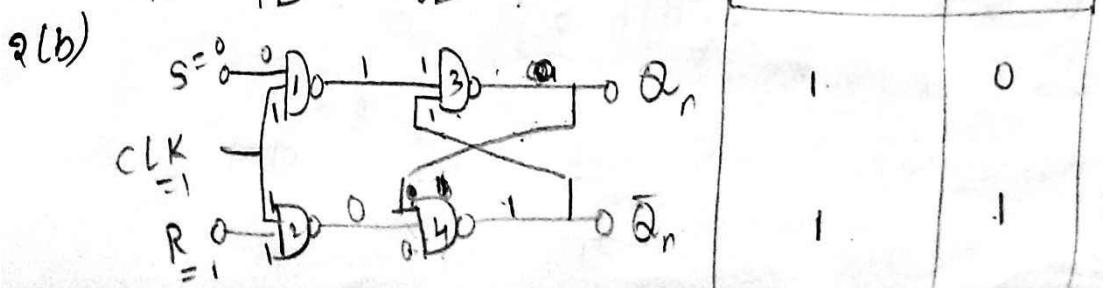

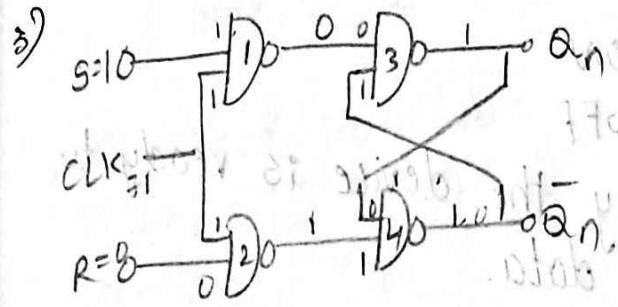

| P.S | N.S |
|-----|-----|
| 0 | 1 |
| 1 | 0 |
| 0 | 0 |


Set state
(output=1)

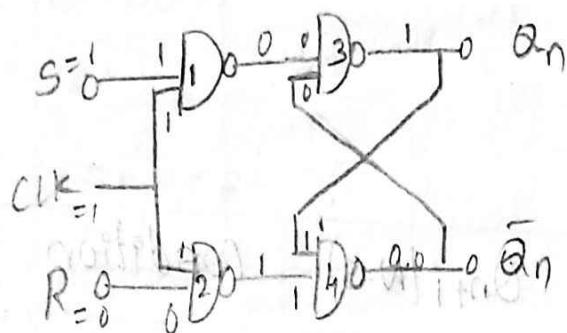


| state info | |
|------------|-----|
| P.S | N.S |
| 1 | 0 |
| 0 | 1 |

| P.S | N.S |
|-----|-----|
| 0 | 0 |
| 1 | 0 |
| 0 | 1 |

In determinate condition

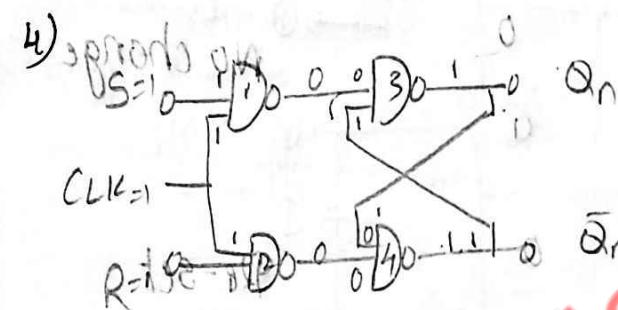

| P.S | N.S |
|-----|-----|
| 1 | 0 |
| 0 | 1 |
| 1 | 1 |
| 0 | 0 |

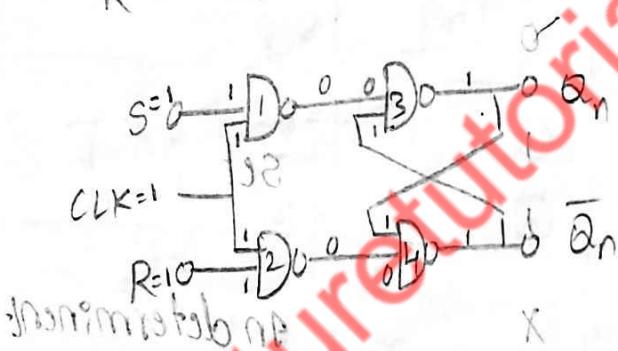

| X | 0 | 1 | 1 | 0 |
|---|---|---|---|---|
| X | 1 | 1 | 1 | 1 |

Flip flop:

- flip flop is a single bit storage device
- flip flop (SR, JK, T, D) are four
- Types of flip flop [Set, Reset]

* S-R flip flop [Set, Reset]

* J-K flip flop

| A | B | AB | $\bar{A} \cdot B$ |
|---|---|----|-------------------|
| 0 | 0 | 0 | 1 |

* T flip flop

| A | B | AB | $\bar{A} \cdot B$ |
|---|---|----|-------------------|
| 0 | 1 | 0 | 1 |

* D flip flop


| A | B | AB | $\bar{A} \cdot B$ |
|---|---|----|-------------------|
| 1 | 0 | 1 | 0 |

1. when $CLK = 1$ it is ON
2. when $CLK = 0$ it is OFF
3. CLK is used to say the device is ready to accept the input or data.
4. $P.S \rightarrow$ present state
5. $N.S \rightarrow$ Next state

Date Truth Table

8/8/19

| SNO | S | R | $Q_n(P.S)$ | $Q_{n+1}(N.S)$ | Condition |
|-----|---|---|------------|----------------|----------------|
| 0 | 1 | 0 | 0 | 0 | → ① No change |
| 1 | 0 | 0 | 1 | 1 | → ② |
| 2 | 0 | 1 | 0 | 0 | → ① Re-set |
| 3 | 0 | 1 | 1 | 0 | → ③ |
| 4 | 1 | 0 | 0 | 1 | → ② Set |
| 5 | 1 | 0 | 1 | 1 | → ④ |
| 6 | 1 | 1 | 0 | X | In determinent |
| 7 | 1 | 1 | 1 | X | |

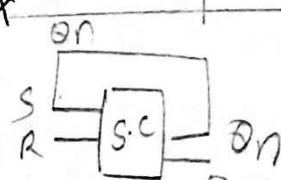Characteristic Eqⁿ

SR Qn goes to Qn+1

Guard (6, 4, 7, 5)

$$(S\bar{R} + \bar{S}R) \cdot (\bar{Q}_n + Q_n)S^{\bar{n}}$$

Row. col

$$\bar{S}R + S\bar{R}$$

pair (1, 5)

$$(\bar{S}R + S\bar{R}) \cdot \bar{Q}_n$$

$$\bar{R}(\bar{S} + S)\bar{Q}_n$$

$$\bar{R}\bar{Q}_n$$

$$\bar{Q}_n \bar{Q}_{n+1}$$

$$\bar{Q}_n \bar{Q}_{n+1}$$

$$\bar{Q}_n \bar{Q}_{n+1}$$

$$\bar{Q}_n \bar{Q}_{n+1}$$

$$\bar{Q}_n \bar{Q}_{n+1}$$

$$Q_{n+1} = S + \bar{R} Q_n$$


Minimized Truth Table

| S | R | $Q_{n+1} =$ |
|-----|-----|-------------|
| 0 | 0 | Q_n |
| 0 | 1 | 0 |
| 1 | 0 | 1 |
| 1 | 1 | X |

Excitation Table


| Q_n | Q_{n+1} | S | R |
|-------|-----------|-----|-----|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 0 | 1 |
| | | | X |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 1 |
| 1 | 1 | 0 | 0 |
| | | 1 | 0 |
| | | X | 0 |

Date 18/11/19 Symbol

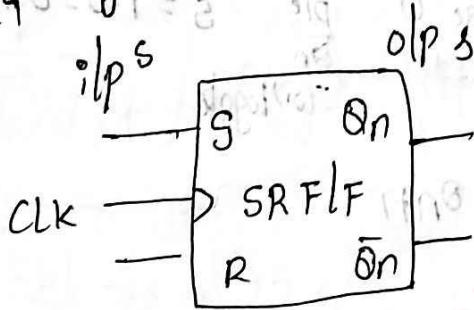


J-K- flip flop

AND Gate

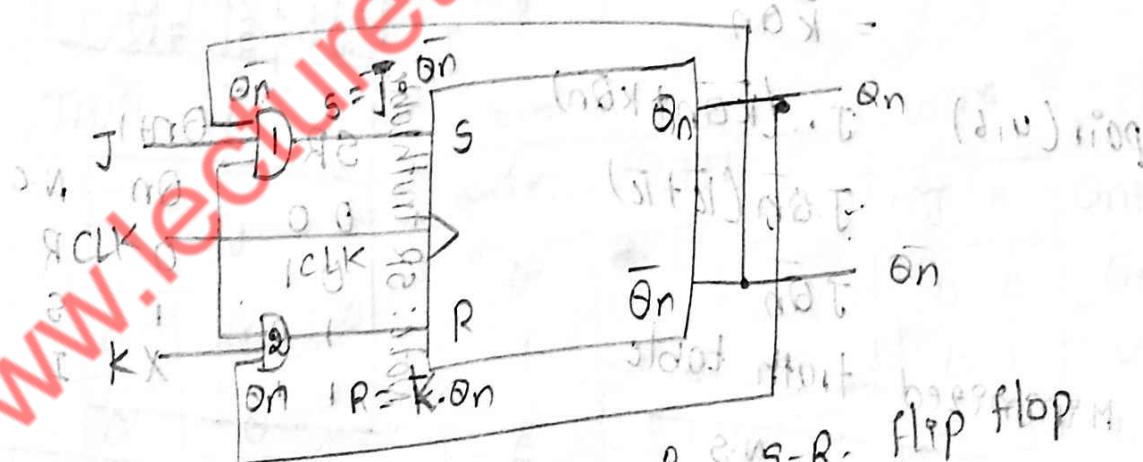

Circuit diagram for S-R flip flop

Symbol

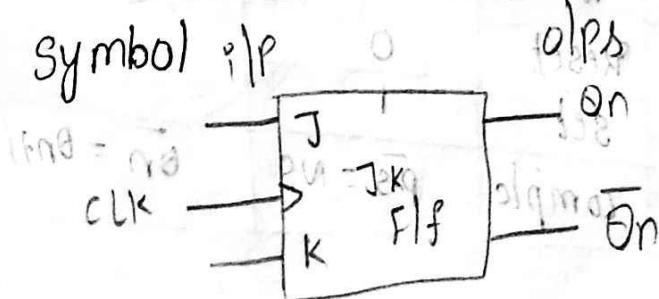

Truth Table

Exploded table

and function
border
conditions

t.me/jntukonlinebits

| J | K | S | R | P.S $Q_n = \bar{Q}_n$ | N.S \bar{Q}_{n+1} | C | $S = J\bar{Q}_n$ | $R = K\bar{Q}_n$ |
|---|---|---|---|--------------------------|------------------------|-------------------------|---------------------|---------------------|
| 0 | 0 | 0 | 0 | 0 | 1 | 0 | $S = 0 \cdot 1 = 0$ | $R = 0 \cdot 0 = 0$ |
| 1 | 0 | 0 | 0 | 1 | 0 | <u>1</u> ^{map} | $S = 0 \cdot 0 = 0$ | $R = 0 \cdot 1 = 0$ |
| 0 | 1 | 0 | 0 | 0 | 1 ^{NC} | 0 ^{map} | $S = 0 \cdot 1 = 0$ | $R = 1 \cdot 0 = 0$ |
| 0 | 1 | 0 | 1 | 1 | 0 ^{RS} | 0 ^{map} | $S = 0 \cdot 0 = 0$ | $R = 1 \cdot 1 = 1$ |
| 1 | 0 | 0 | 1 | 0 | 1 ^{set} | 1 ^{map} | $S = 1 \cdot 1 = 1$ | $R = 0 \cdot 0 = 0$ |
| 1 | 0 | 0 | 0 | 1 | 0 ^{NC} | 1 ^{map} | $S = 1 \cdot 0 = 0$ | $R = 0 \cdot 1 = 0$ |
| 1 | 1 | 1 | 0 | 0 | 1 ^{set} | 1 ^{map} | $S = 1 \cdot 1 = 1$ | $R = 1 \cdot 0 = 0$ |
| 1 | 1 | 0 | 1 | 1 | 0 ^{RC} | 0 ^{map} | $S = 1 \cdot 0 = 0$ | $R = 1 \cdot 1 = 1$ |

characteristic equation

$$J_K \bar{Q}_n \text{ if } ps \rightarrow \bar{Q}_{n+1}$$

pair(1, 5) rows. cols

$$(\bar{J} + J) \cdot \bar{K} \bar{Q}_n$$

$$= \bar{K} \bar{Q}_n$$

pair(4, 6) $J \cdot (\bar{K} \bar{Q}_n + K \bar{Q}_n)$

$$J \bar{Q}_n (\bar{K} + K)$$

$$J \bar{Q}_n$$

Minimized truth table

| J | K | \bar{Q}_n | \bar{Q}_{n+1} |
|---|---|-------------|-----------------|
| 0 | 0 | 1 | 1 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 1 |
| 1 | 1 | 0 | 0 |

| SR | | \bar{Q}_{n+1} | |
|----|---|-----------------|---|
| 0 | 0 | \bar{Q}_n | |
| 0 | 1 | 0 | R |
| 1 | 0 | 1 | S |
| 1 | 1 | X | I |

| J | K | $\bar{Q}_{n+1} =$ |
|---|---|-------------------|
| 0 | 0 | \bar{Q}_n |
| 0 | 1 | 0 |
| 1 | 0 | 1 |
| 1 | 1 | \bar{Q}_n |

| | $\bar{Q}_n = \bar{Q}_{n+1}$ | $\bar{Q}_n = Q_n$ | $\bar{Q}_n = \bar{Q}_n$ |
|-------|-----------------------------|-------------------|-------------------------|
| Reset | 0 | 0 | 0 |
| Set | 1 | 0 | 1 |
| Compl | \bar{Q}_n | \bar{Q}_n | \bar{Q}_n |
| | $\bar{Q}_n = NS$ | $\bar{Q}_n = NS$ | $\bar{Q}_n = \bar{Q}_n$ |

Exposition Table

t.me/jntukonlinebits

| K | 0 | - | X | 0 | - | X | - | - | - | 0 | 0 | 0 |
|------|---|---|---|---|---|---|---|---|---|---|---|---|
| J | 0 | 0 | | 0 | - | - | - | 0 | - | X | 0 | - |
| Qn | 0 | | | 1 | | | | 0 | | | 1 | |
| Qnti | 0 | | | | 1 | | | | 0 | | | 1 |
| On | 0 | . | . | 0 | | | | - | . | | - | |


T F/f / Toggle flip flop

T flip flop

ilp olp

1 2
T Qn, $\bar{Q}n$

outputs

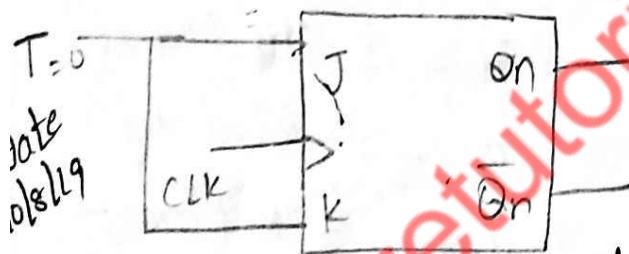

It has single input and we get two outputs

Truth table

Assumption

using J-K F/f

| T | J | K | Qn | Qnti |
|---|---|---|----|---------------------|
| 0 | 0 | 0 | 0 | 0 } $\rightarrow 0$ |
| 0 | 0 | 0 | 1 | 1 } N.C |
| 0 | 1 | 1 | 0 | 1 } $\rightarrow 0$ |
| 1 | 1 | 1 | 1 | 0 } comp |

| J | K | Qn | Qnti |
|---|---|-----------------|------|
| 0 | 0 | Qn NC | |
| 0 | 1 | 0 R | |
| 1 | 0 | 1 S | |
| 1 | 1 | $\bar{Q}n$ comp | |

Minimized truth table

D/I/P N.S
T Q_{n+1}

| D/I/P | N.S | | |
|-------|-----|-----|---------------------|
| 0 | 0 | i/p | N.S |
| 0 | 1 | T | Q _{n+1} |
| 1 | 0 | 0 | Q _n N.C |
| 1 | T | 1 | Q _n comp |

Excitation table

JNTU/jntukonlinebits


| D/I/P | Q _{n+1} | T |
|-------|------------------|---|
| 0 | 0 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 0 |

Characteristic equation

$$Q_{n+1} = \bar{T}Q_n + T\bar{Q}_n$$

| Q | 0 | 0 | 0 | Q _{n+1} |
|---|---|---|---|------------------|
| T | 0 | 0 | 1 | 0 |
| T | 1 | 0 | 1 | 1 |

D flip flop (or) delay flip flop

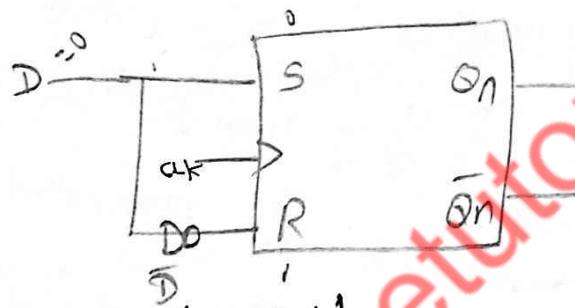

Truth Table

| D/I/P | S=D | R=̄D | (P.S) Q _n | (N.S) Q _{n+1} |
|-------|-----|------|----------------------|------------------------|
| 0 | 0 | 1 | 0 | 0] Reset |
| 0 | 0 | 1 | 1 | 0] |
| 1 | 1 | 0 | 0 | 1] Set |
| 1 | 1 | 0 | 1 | 1] |

This D flip flop can be constructed by using S-R flip flop

S.R. f/p Truth table

Minimized truth table

<http://infukonlinebits.com>

| S | R | Qn+1 | Condition |
|---|---|------|-----------|
| 0 | 0 | Qn | N.C |
| 0 | 1 | 0 | R |
| 1 | 0 | 1 | S |
| 1 | 1 | X | inde |

Excitation table

characteristic equation:

| Qn | Qn+1 | D |
|----|------|---|
| 0 | 0 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | 0 |
| 1 | 1 | 1 |

$$Qn+1 = D$$

| D | Qn | Qn+1 |
|---|----|------|
| 0 | 0 | 0 |
| 1 | 0 | 1 |
| 2 | 1 | 0 |
| 3 | 1 | 1 |

| D | Qn | Qn+1 |
|---|----|------|
| 0 | 0 | 1 |
| 1 | 1 | D3 |

Date
13/8/19

Conversion of flip flops

1. Convert S-R flip flop to D-flip flop (or)

1. convert S-R flip flop to D-flip flop using S-R flip flop.

construct D flip flop is going to construct take the

solu 1. which flip flop is going to use for the construction

truth table of that flip flop

2. which flip flop is going to use for the flip flop

take excitation table of the flip flop

| D | Qn | Qn+1 cond | SR | X |
|---|----|-----------|-------|-----|
| 0 | 0 | 0 | Reset | X0 |
| 1 | 0 | 0 | | 01 |
| 1 | 0 | 1 | Set | 10 |
| 1 | 1 | 1 | | X0X |

Truth table of D flip flop

| Qn | Qn+1 | SR |
|----|------|------|
| 0 | 0 | 0 X0 |
| 0 | 1 | 1 0 |
| 1 | 0 | 0 1 |
| 1 | 1 | X 0 |

excitation table
of SR flip flop

S-R flip flop \rightarrow D flip flop

S K-map

| | | | |
|----|---|---|-----|
| D | 0 | 0 | 0 |
| Qn | 0 | 1 | |
| QD | 1 | 2 | X 3 |


$$S = \bar{D} (\bar{Q}_n + Q_n)$$

$$S = \bar{D}$$

R - K-map

| | | | |
|----|---|---|---|
| D | 0 | 0 | 0 |
| Qn | 0 | 1 | |
| QD | 1 | 2 | 3 |
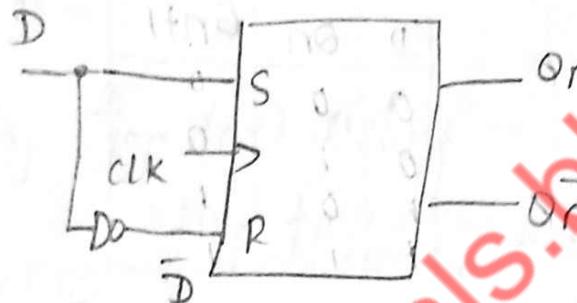
$$\begin{aligned} R &= \bar{D} (\bar{Q}_n + Q_n) \\ &= \bar{D} \end{aligned}$$



2. Convert S-R flip flop to J-K flip flop
present (S R) flip flop \rightarrow JK flip flop (construct)
Excitation table Truth table
Truth table of J-K flip flop Excitation table of S-R flip flop

| J | K | present Qn | next Qn | condi on | S R |
|---|---|------------|---------|----------|-------|
| 0 | 0 | 0 | 0 | N.C | 0 X |
| 1 | 0 | 1 | 1 | | X 0 |
| 2 | 1 | 0 | 0 | | 0 X |
| 3 | 1 | 1 | 0 | Reset | 0 1 |
| 4 | 1 | 0 | 1 | Set | 1 0 |
| 5 | 1 | 1 | 1 | | X 0 X |
| 6 | 1 | 0 | 1 | Comp | 1 0 |
| 7 | 1 | 1 | 0 | | 0 1 X |

| Qn | On | S R |
|----|----|-----|
| 0 | 0 | 0 X |
| 0 | 1 | 1 0 |
| 1 | 0 | 0 1 |
| 1 | 1 | X 0 |

$$S = \sum_m (U, 6) + d(1, 5)$$

$$R = \sum_m (3, 7) \quad \text{tutkuonlinebits}$$

* S K-map

| | | K-Qn | | | |
|----|---|------|----|------|----|
| | | K̄Qn | Qn | K̄Qn | Qn |
| | | 00 | 01 | 11 | 10 |
| J | 0 | X | | | |
| | 1 | 1 | 1 | 3 | 2 |
| J̄ | 0 | 0 | 1 | 3 | 2 |
| | 1 | 1 | X | 7 | 6 |

R K-map

| | | K-Qn | | | |
|----|---|------|----|------|----|
| | | K̄Qn | Qn | K̄Qn | Qn |
| | | 00 | 01 | 11 | 10 |
| J | 0 | X | | 1 | X |
| | 1 | 0 | 1 | 3 | 2 |
| J̄ | 0 | X | | 1 | X |
| | 1 | 0 | 1 | 3 | 2 |

pair(U, 6)

$$= J \cdot (\bar{K}Qn + K\bar{Q}n)$$


$$= J\bar{Q}n(\bar{K} + K)$$

$$S = J\bar{Q}n$$

pair(3, 7)

$$= (\bar{J} + J)\bar{Q}n$$


$$R = K\bar{Q}n$$

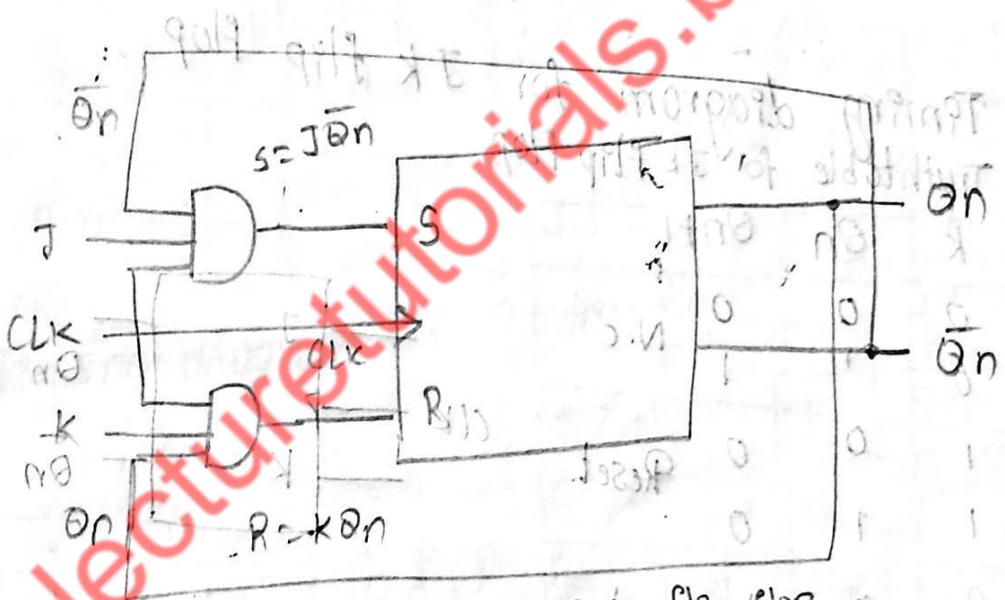

J-K flip flop

Timing Diagrams
⇒ S-R flip flop (or) edge trigger flop flop

start

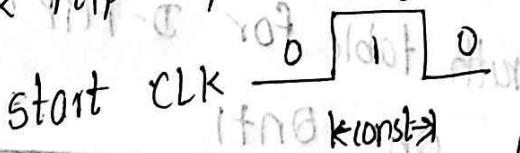

const

OFF

→ ON (triggering)

minimized
truth table

| S | R | Qn(t) |
|---|---|-------|
| 0 | 0 | Qn(t) |
| 0 | 1 | 0 |
| 1 | 0 | 1 |
| 1 | 1 | X |



R-S

S

Qn(t)


↑ +ve edge triggering

↑ +ve edge triggering

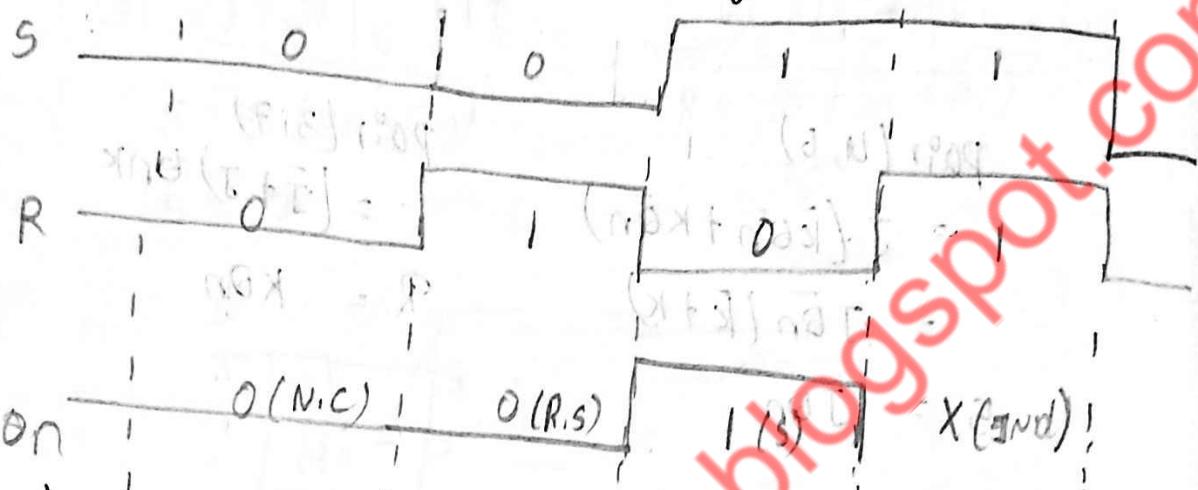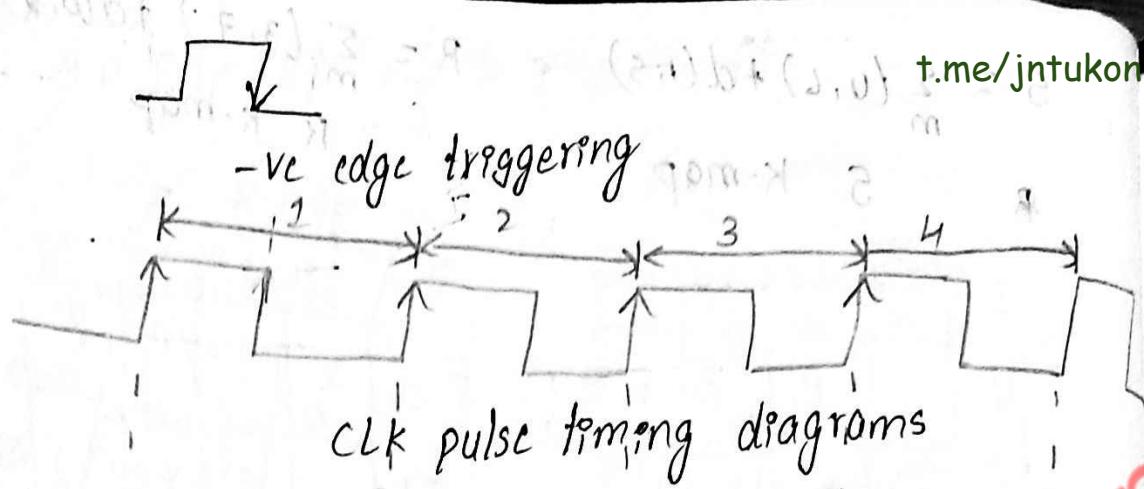

Date : 14/8/19 Timing diagram for JK flip flop
Truth table for JK flip flop


| J | K | Qn | Qn+1 | |
|---|---|----|------|--------|
| 0 | 0 | 0 | 0 | |
| 0 | 0 | 1 | 1 | |
| 0 | 1 | 0 | 0 | |
| 0 | 1 | 1 | 0 | Reset. |
| 1 | 0 | 0 | 1 | Set |
| 1 | 0 | 1 | 1 | |
| 1 | 1 | 0 | 1 | comple |
| 1 | 1 | 1 | 0 | |

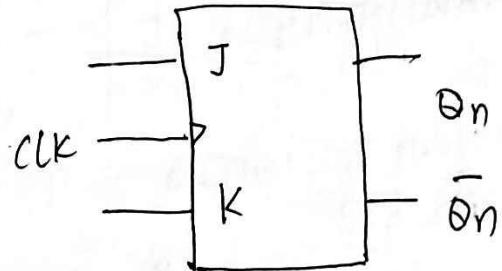


minimized truth table for D-Flop Flop

| D | Qn | Qn+1 |
|---|----|------|
| 0 | 0 | 0 |
| 0 | 1 | 0 |
| 1 | 0 | 1 |
| 1 | 1 | 1 |

Reset is $Qn+1 = 0$
Set

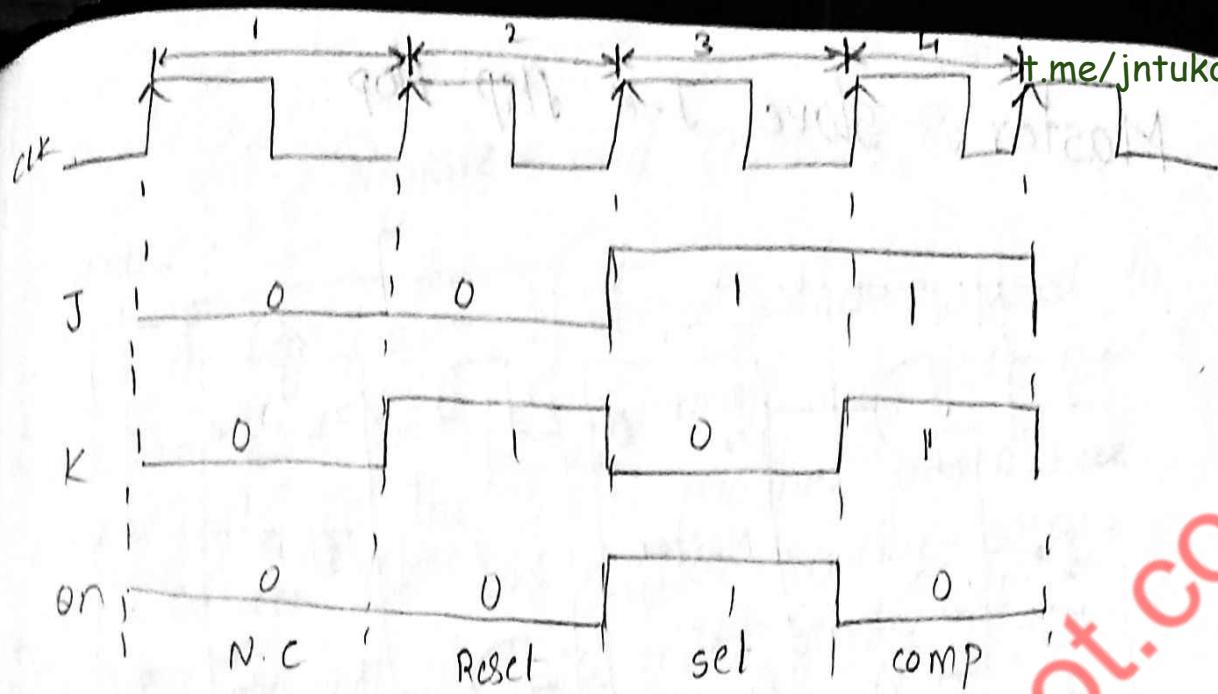

Timing diagram for D flip flop

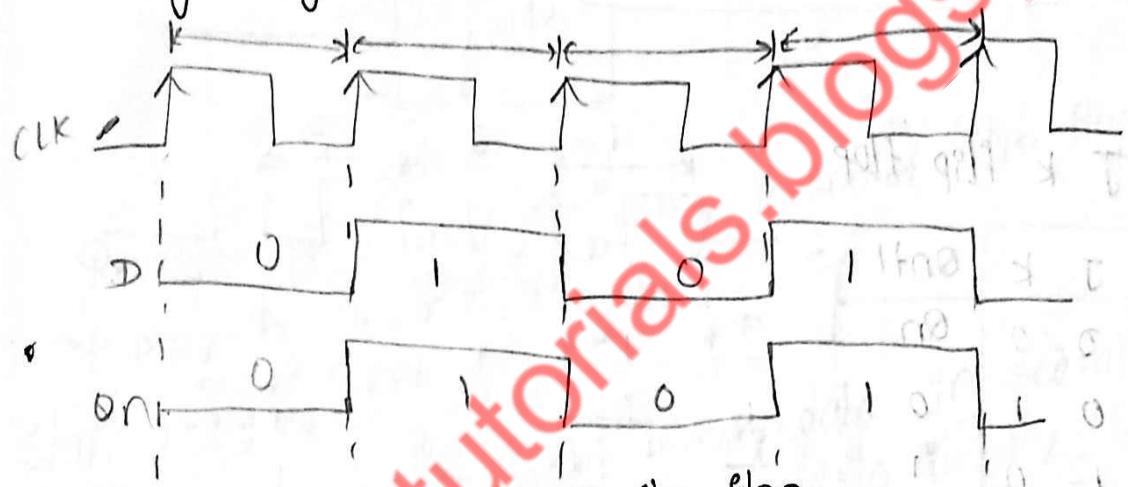


Timing diagram for T flip flop

| T | Qn | anti |
|-----|----|------|
| P-S | Qn | N-S |
| 0 | 0 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 0 |

minimized truth table


Master's slave J-K flip flop

t.me/jntukonlinebits

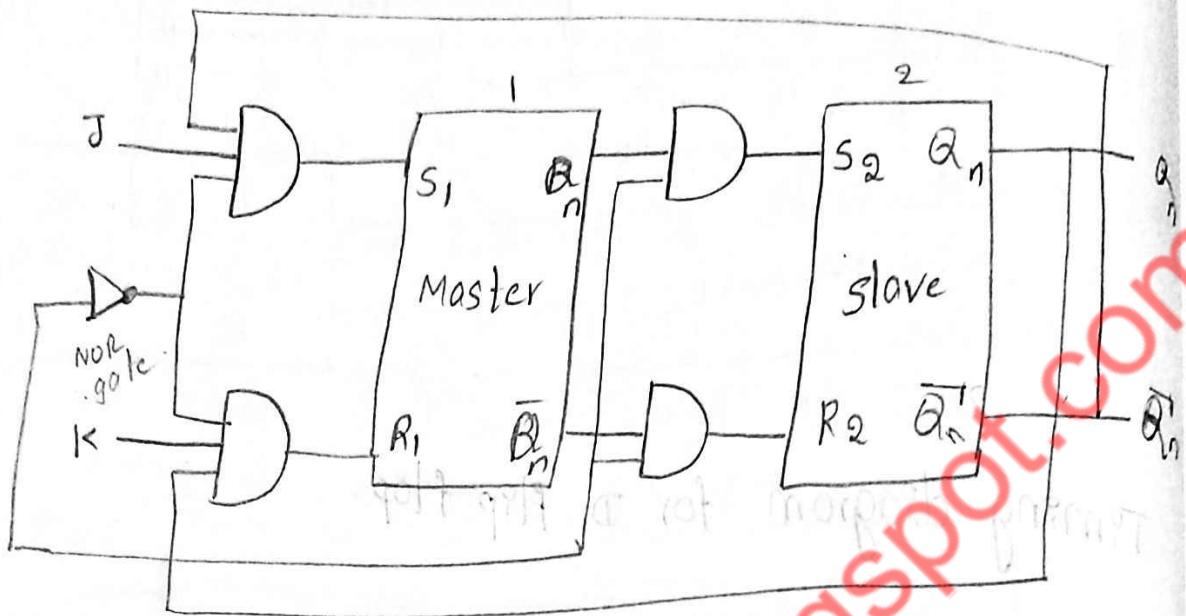

J K flip flop

| J | K | Qn |
|---|---|-------------|
| 0 | 0 | Qn |
| 0 | 1 | 0 |
| 1 | 0 | 1 |
| 1 | 1 | \bar{Q}_n |

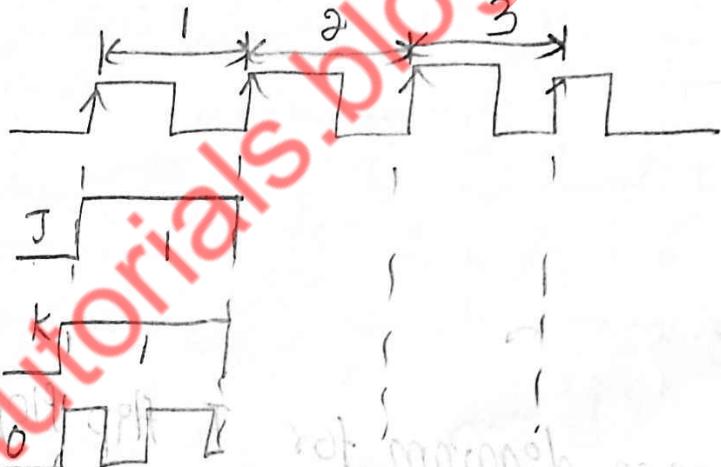


Race around problem

Here when the values of J K are both "1" we get the toggle or complement as output

while occurring this output an error race around problem occurred to avoid this "Master slave JK flip flop is used".

Finite State Machine


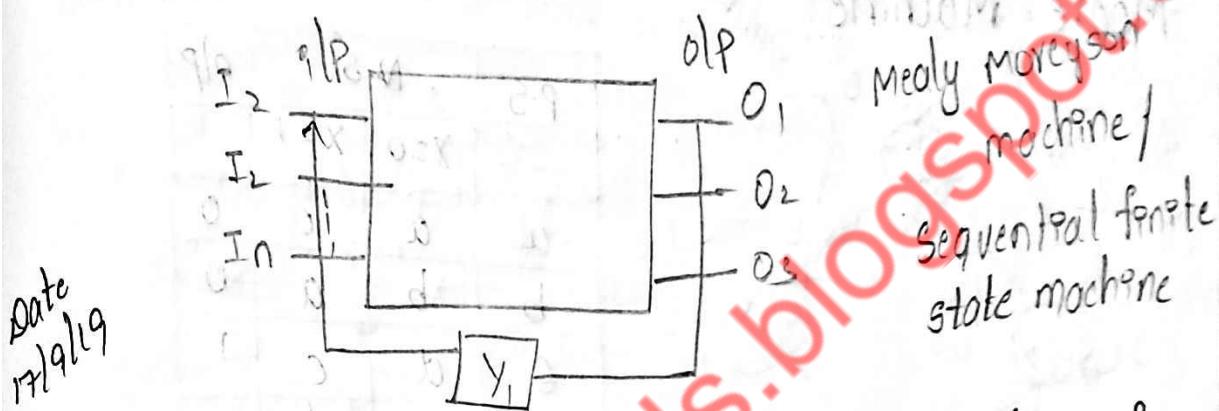
Finite state machine is a model which is used to describe the synchronous sequential machine. It is a machine with fixed no. of states i_1, i_2, \dots, i_n input variables; $o_1, o_2, o_3, \dots, o_n$ = output variables $y_1, y_2, y_3, \dots, y_n$ are state variables



State Diagrams

State diagram is the pictorial representation of states, present state \Rightarrow next state

Mealy Machine

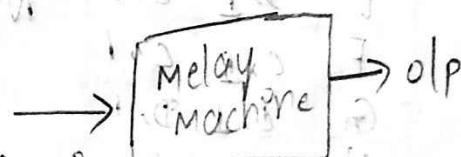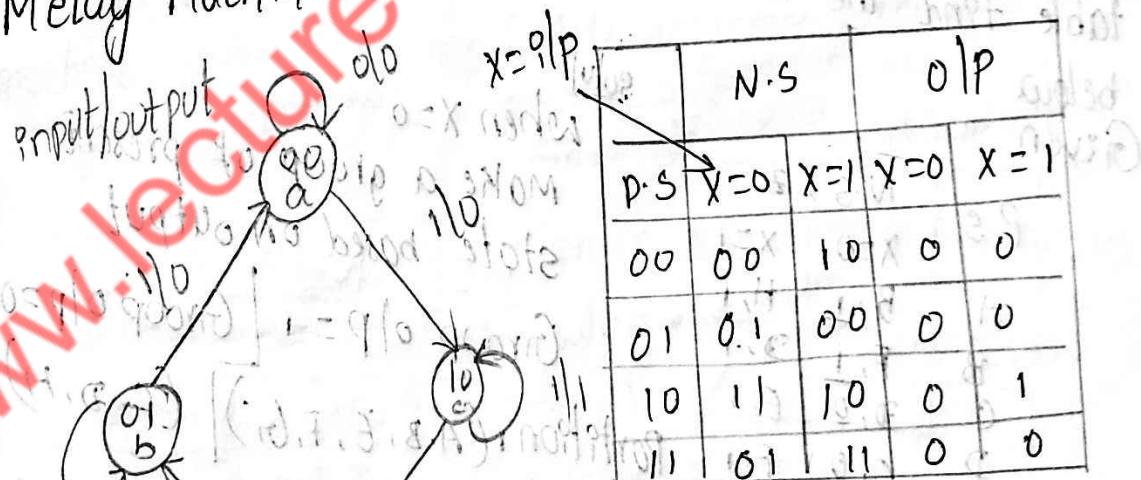

P.S \rightarrow N.S

Excitation table


| N.S | | output | | Q.O.P |
|-----|-----|--------|----|-------|
| P.S | X=0 | X=1 | | |
| 00 | 00 | 0 | 10 | 00P |
| 01 | 01 | 0 | 00 | 0 |
| 10 | 11 | 0 | 10 | 1 |
| 11 | 01 | 0 | 11 | 0 |

Note

t.me/jntukonlinebits

If they didn't mention any model it is melay otherwise moore

Moore Machine

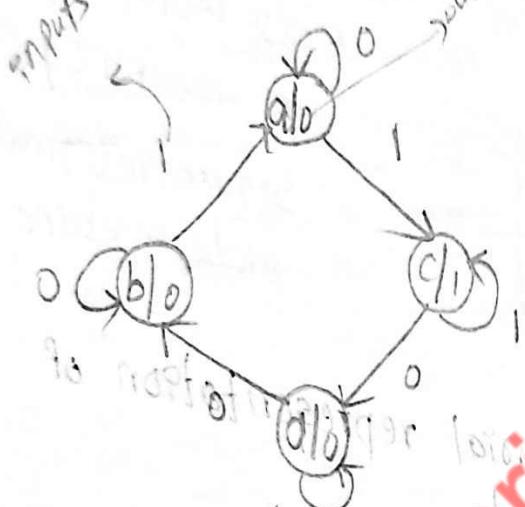

State table

| P.S | N.S | | Q.O.P |
|-----|-----|-----|-------|
| | X=0 | X=1 | |
| a | a | c | 0 |
| b | b | a | 0 |
| c | d | c | 1 |
| d | b | d | 0 |

what are the conditions to minimize the state table find the minimized state table for the given below.

Given

| P.S | N.S, Z | |
|-----|--------|------|
| | X=0 | X=1 |
| A | B, 1 | H, 1 |
| B | F, 1 | D, 1 |
| C | D, 0 | E, 1 |
| D | C, 0 | F, 1 |
| E | D, 1 | C, 1 |
| F | C, 1 | C, 1 |
| G | C, 1 | D, 1 |
| H | C, 0 | A, 1 |

when X=0

make a group of present state based on output

Group Q.O.P = 1 Group Q.O.P = 0

Partition : (A, B, E, F, G) (C, D, H)

N.S when X=0

(B, F, D, C, C) . | (D, C, C)

we have to make the successor values as a group

partition 2

$$(A+B)(E+F+G)(C)(DH) \quad [\because B \text{ is } \text{sum} \text{ of } \text{bits}]$$

F is a successor of B

N.S when $X=1$

$$(HD) \underbrace{(CCD)}_{\text{successor}} (E) \underbrace{(FA)}_{\text{other successors}}$$

HD are successor of AB
 E is not successor of C

partition 3

$$(AB)(EFG)(X)(DH)(CD)(H)$$

minimized state table

| P.S | N.S, Z | |
|-----|--------|------|
| | X=0 | X=1 |
| A | B, 1 | H, 1 |
| B | F, 1 | D, 1 |
| C | D, 0 | E, 1 |
| E | D, 1 | C, 1 |
| H | C, 0 | A, 1 |

Date
19/9/2019

Derive a circuit that realizes the finite state machine defined by the state assignment table below using J-K flip flop.

when $X=0$

Group 0/p = 1

Group 0/p = 0

| P.S | N.S, Z | |
|-----|--------|------|
| | X=0 | X=1 |
| A | B, 0 | E, 0 |
| B | E, 0 | D, 0 |
| C | D, 1 | A, 0 |
| D | C, 1 | E, 0 |
| E | B, 0 | D, 0 |

partition 1 (C, D)

N.S when $X=0$

(D, C)

(A, B, E)

(B, E, B)

partition 2

(E) (D) (C)

N.S when $X=1$

(A, E)

(AB) E

(E, D, D)

partition 3

D, C

(AB) E

Minimized truth table

t.me/jntukonlinebits

| P.S | N.S, Z | |
|-----|--------|------|
| | X=0 | X=1 |
| A | B, 0 | C, 0 |
| C | D, 1 | A, 0 |
| D | C, 1 | E, 0 |
| E | B, 0 | D, 0 |

Implement the finite state machine using J-K flip flops [the given state table is reduced state table for the above reduced table]

| Q ₁ P ₀ | X | P.S | N.S | | Q ₁ P ₀ | J _P | K _P | J _Q | K _Q |
|-------------------------------|---|-------|----------------|----------------|-------------------------------|----------------|----------------|----------------|----------------|
| | | | Q ₁ | P ₀ | | | | | |
| 0 | 0 | A, 00 | B, 01 | 0 | 0 | 0 | X | 1 | X |
| 1 | 0 | B, 01 | B, 01 | 0 | 0 | X | X | 0 | |
| 2 | 0 | C, 10 | D, 11 | 1 | X | 0 | 1 | | X |
| 3 | 0 | D, 11 | C, 10 | 1 | X | 0 | X | 1 | X |
| 4 | 1 | A, 00 | B, 01 | 0 | 0 | 0 | X | 1 | |
| 5 | 1 | B, 01 | D, 11 | 0 | 1 | X | X | 0 | |
| 6 | 1 | C, 10 | A, 00 | 0 | X | 1 | 0 | | X |
| 7 | 1 | D, 11 | B, 01 | 0 | X | 1 | X | 0 | |

Given minimized table

| Q _n | Q _{n+1} | J K | | P.S | N.S, Z | |
|----------------|------------------|-----|---|-----|--------|------|
| | | X | X | | X=0 | X=1 |
| 0 | 0 | 0 | X | A | B, 0 | B, 0 |
| 0 | 1 | 1 | X | B | B, 0 | D, 0 |
| 1 | 0 | X | 1 | C | D, 1 | A, 0 |
| 1 | 1 | X | 0 | D | C, 1 | B, 0 |

Excitation table of JK flip flop

| | 00 | 01 | 11 | 10 |
|---|-----|-----|----|----|
| 0 | 1 X | X 1 | 1 | |
| 1 | 1 X | X 1 | 1 | |

$$Jq = \bar{x} + \bar{p}$$

| | 00 | 01 | 11 | 10 |
|---|----|----|-----|----|
| 0 | X | 1 | 1 X | |
| 1 | X | 1 | 1 | X |

$$Kq = \bar{x} \cdot p$$

| | 00 | 01 | 11 | 10 |
|---|-----|-----|-----|----|
| 0 | | | X X | |
| 1 | 0 1 | 3 2 | | |

$$Jp = xq$$

| | 00 | 01 | 11 | 10 |
|---|-----|-----|----|----|
| 0 | X X | 1 3 | 2 | |
| 1 | X X | 1 1 | 1 | |

$$Kp = x$$


olp: z

Here x, p, q are inputs.


| | 00 | 01 | 11 | 10 |
|---|-----|-----|-----|----|
| 0 | 0 1 | 1 1 | 1 1 | 2 |
| 1 | 0 5 | 1 7 | 6 | |

$$z = \bar{x}p$$

logic circuit

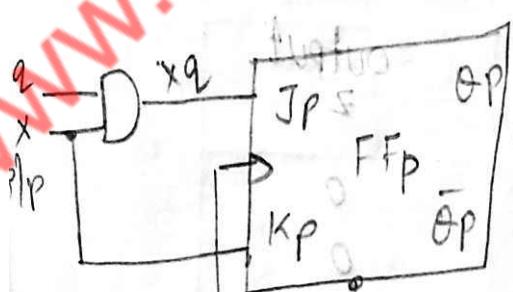

CLK
clear pulse

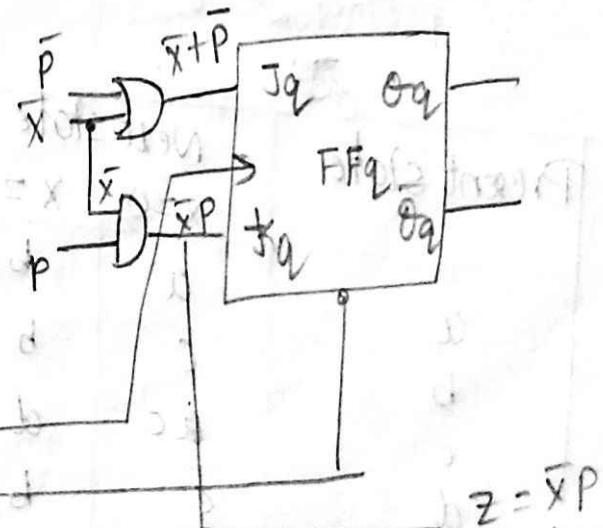

$$z = \bar{x}p$$


olp

- Assignment*
1. If the simple example explain the difference between Mealy and Moore type machine (unit-II)
 2. Draw the diagram of Moore type FSM (finite state machine) for serial adder (unit-II).
 3. Draw the diagram of Mealy type state machine for serial adder and explain its operation (unit-II).
 4. what are the capabilities and limitations of finite state machine explain (unit-II).

Date 20/01/19 Sequence Detector

Design a Moore type sequence detector to detect a serial input sequence of 101

o/p sequence 101

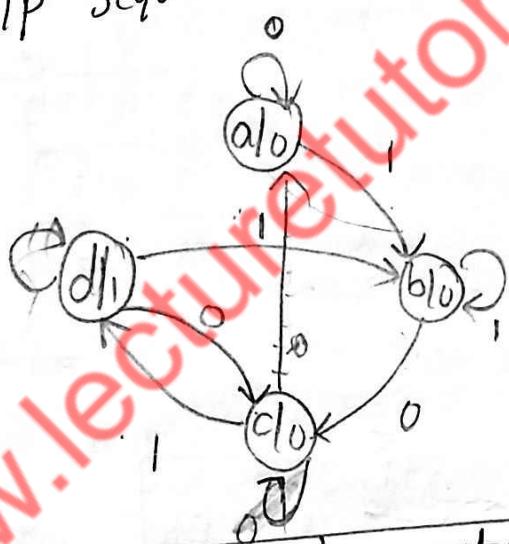

Excitation table of Ff

| on | on + 1 | D |
|----|--------|---|
| 0 | 0 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | 0 |
| 1 | 1 | 1 |

| Present state | Next state | | output z |
|---------------|------------|-----|-------------|
| | x=0 | x=1 | |
| a | a | b | 0 |
| b | c | b | 0 |
| c | ac | d | 0 |
| d | c | b | 1 |



| XQ/P | $P \cdot S$ | $N \cdot S$ | D_P | D_Q |
|--------|-------------|-----------------|-------|-------|
| | $P \cdot Q$ | $P+1 \cdot Q+1$ | | |
| 0 | 0 | a | 00 | a |
| 1 | 0 | b | 01 | c |
| 2 | 0 | c | 10 | c |
| 3 | 0 | d | 11 | c |
| 4 | 1 | a | 00 | b |
| 5 | 1 | b | 01 | b |
| 6 | 1 | c | 10 | d |
| 7 | 1 | d | 11 | b |

| $X \cdot P \cdot Q$ | 00 | 01 | 11 | 10 |
|---------------------|----|----|----|----|
| 0 | 1 | 1 | 1 | 1 |
| 1 | 0 | 1 | 1 | 1 |
| 2 | 1 | 1 | 1 | 1 |
| 3 | 1 | 1 | 1 | 1 |
| 4 | 1 | 1 | 1 | 1 |
| 5 | 1 | 1 | 1 | 1 |
| 6 | 1 | 1 | 1 | 1 |
| 7 | 1 | 1 | 1 | 1 |

| $X \cdot P \cdot Q$ | 00 | 01 | 11 | 10 |
|---------------------|----|----|----|----|
| 0 | 0 | 1 | 3 | 2 |
| 1 | 1 | 1 | 1 | 1 |
| 2 | 1 | 1 | 1 | 1 |
| 3 | 1 | 1 | 1 | 1 |
| 4 | 1 | 1 | 1 | 1 |
| 5 | 1 | 1 | 1 | 1 |
| 6 | 1 | 1 | 1 | 1 |
| 7 | 1 | 1 | 1 | 1 |

$$D_P = P \cdot \bar{Q} + \bar{P} \cdot Q$$

$$D_Q = X$$

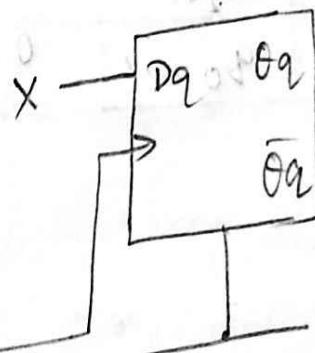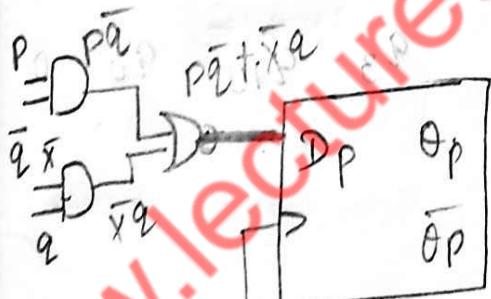

clear
pulse

Date
21/9/19 Melay to Moore Machine

t.me/jntukonlinebits

| P.S | N.S, z | |
|----------------|-------------------|-------------------|
| | X=0 | X=1 |
| q ₀ | q _{3,0} | q _{11,1} |
| q ₁ | q _{0,1} | q _{3,10} |
| q ₂ | q _{2,11} | q _{2,10} |
| q ₃ | q _{1,10} | q _{0,1} |

| | | |
|------------------|-------------------|-------------------|
| q _{0,1} | q _{1,1} | q _{11,1} |
| q _{0,1} | q _{1,0} | q _{10,0} |
| No change | | |
| q _{3,0} | q _{2,11} | q _{21,} |
| q _{3,0} | q _{2,10} | q _{20,1} |
| No change | | |

State table

| P.S | N.S, z | | O/P |
|-----------------|-------------------|-------------------|-----|
| | X=0 | X=1 | |
| q ₀ | q _{3,0} | q _{11,1} | 1 |
| q ₁₀ | q _{0,1} | q _{3,0} | 0 |
| q ₁₁ | q _{0,1} | q _{3,0} | 1 |
| q ₂₀ | q _{21,1} | q _{20,0} | 0 |
| q ₂₁ | q _{21,1} | q _{20,0} | 1 |
| q ₃ | q _{10,0} | q _{0,1} | 0 |

Moore Machine

| P.S | X=0 | X=1 | O/P |
|-----------------|-----------------|-----------------|-----|
| q ₀ | q ₃ | q ₁₁ | 1 |
| q ₁₀ | q ₀ | q ₃ | 0 |
| q ₁₁ | q ₀ | q ₃ | 1 |
| q ₂₀ | q ₂₁ | q ₂₀ | 0 |
| q ₂₁ | q ₂₁ | q ₂₀ | 1 |
| q ₃ | q ₁₀ | q ₀ | 0 |

Date
16/8/19

Registers and Counters

Registers

A register is a device which is used to store the data in binary format and shifts the binary bits in the serial manner and also we can collect the information in the same binary format. It is called bit by bit.




temporary

flip flops

Register is formed by using the no. of flip flop.
it may be D or T flip flop.


shift register
It shifts the given binary data in serial manner and we can collect the data in the same binary manner

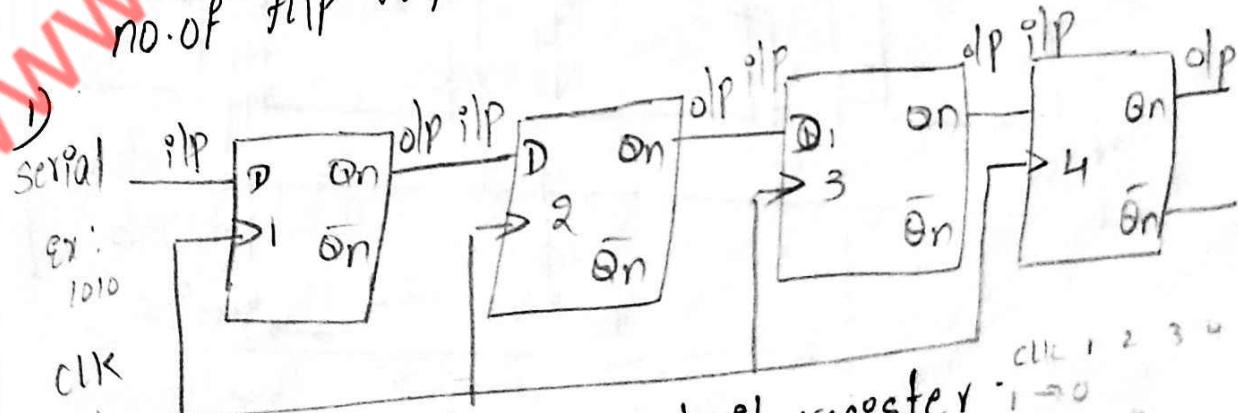4 bit register
no. of flip flops = 4 ; we may use "D" flip flop



Serial in - serial out shift register
 \because in means = entry of data


1 → 0
 2 → 1
 3 → 0
 4 → 1

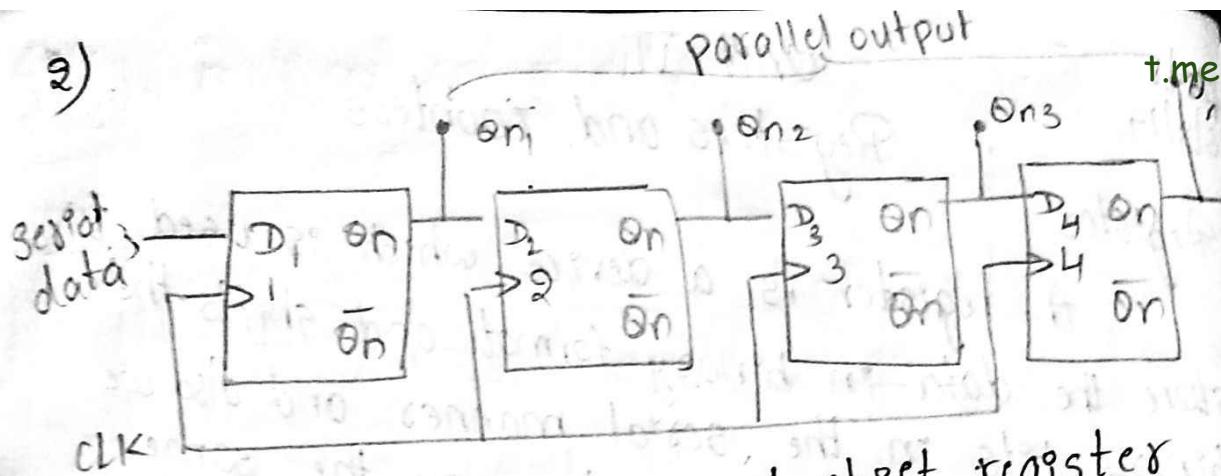

Serial - in - parallel - out shift register


| CLK | ops across f/f | | | |
|-----|----------------|----------------|----------------|----------------|
| | D ₁ | D ₂ | D ₃ | D ₄ |
| 0 | - | - | - | - |
| 1 | 0 | - | - | - |
| 2 | 1 | 0 | - | - |
| 3 | 0 | 1 | 0 | - |
| 4 | 1 | 0 | 1 | 0 |

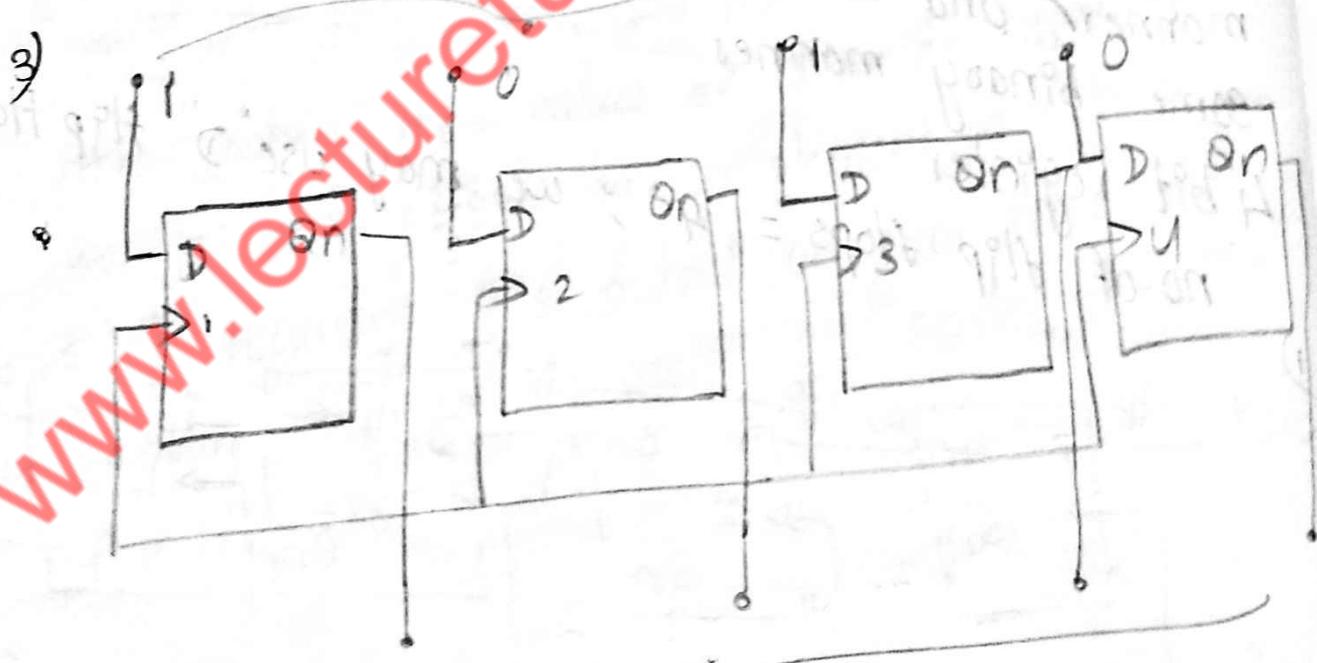In this register the data entered in serial
and collected in parallel out



Parallel - in - parallel - out shift register

2)

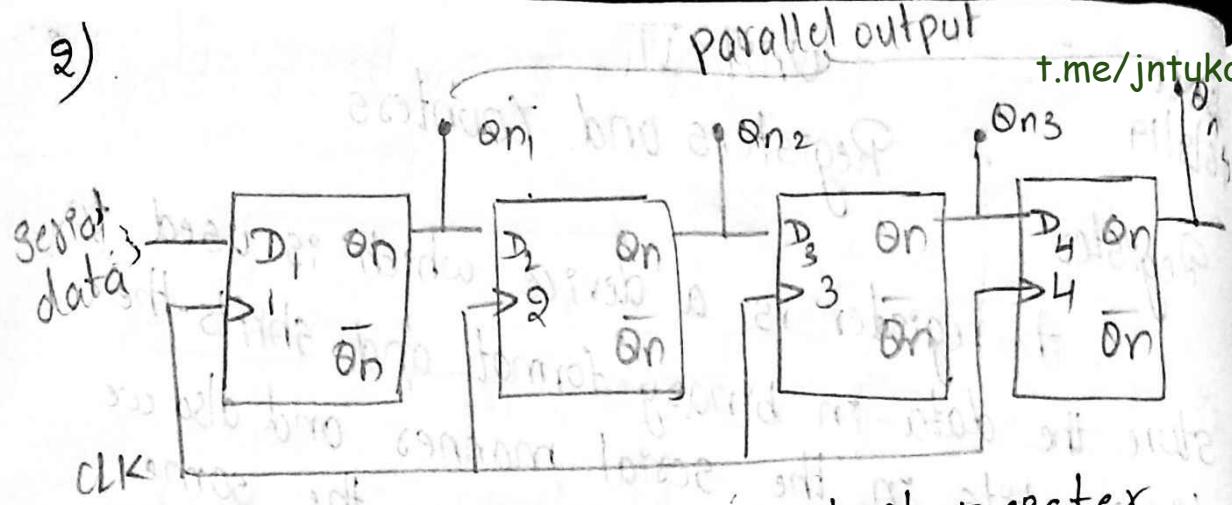


Serial - in - parallel - out shift register

| | | ops across f/f | | | | | |
|---|---|----------------|---|----------------|----------------|----------------|----------------|
| 4 | 3 | 2 | 1 | D ₁ | D ₂ | D ₃ | D ₄ |
| 1 | 0 | 1 | 0 | - | - | - | - |
| 2 | 0 | 1 | 0 | - | - | - | - |
| 3 | 1 | 0 | 1 | 0 | - | - | - |
| 4 | 0 | 1 | 0 | 1 | 0 | - | - |

In this register the data entered in serial
and collected in parallel out

parallel in

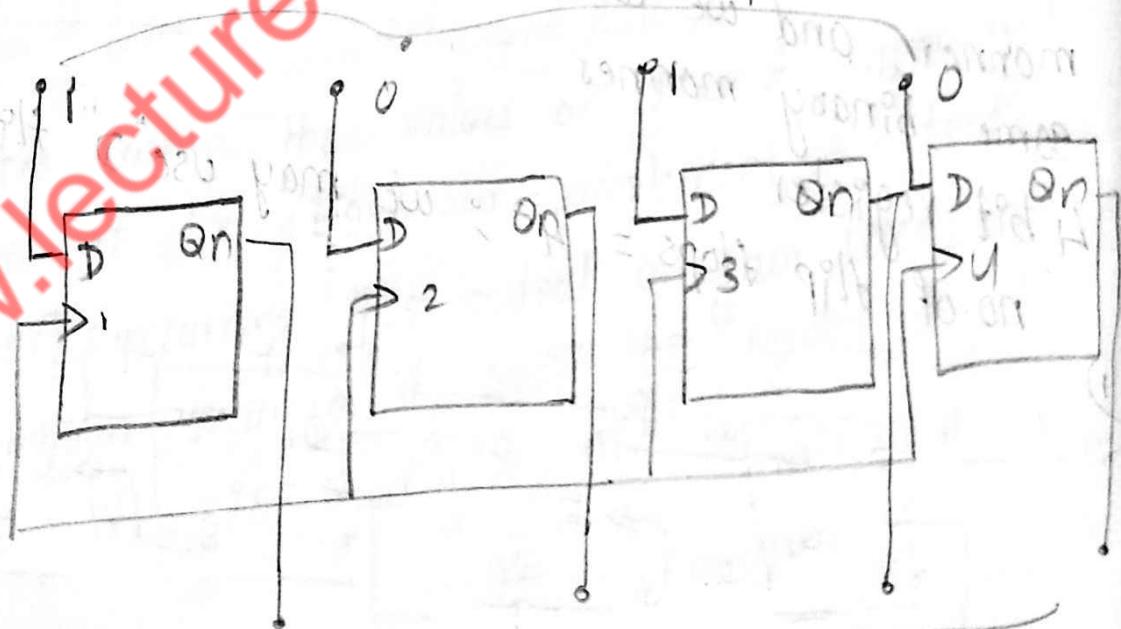


Parallel - in - parallel - out shift register

| CLK | D_1 | D_2 | D_3 | D_4 |
|-------|-------|-------|-------|-------|
| 0 | - | - | - | - |
| 1 | 1 | 0 | 1 | 0 |
| 2 | Q_1 | Q_2 | Q_3 | Q_4 |
| | 1 | 0 | 1 | 0 |

Note: The input is parallel and collected
the output is parallel

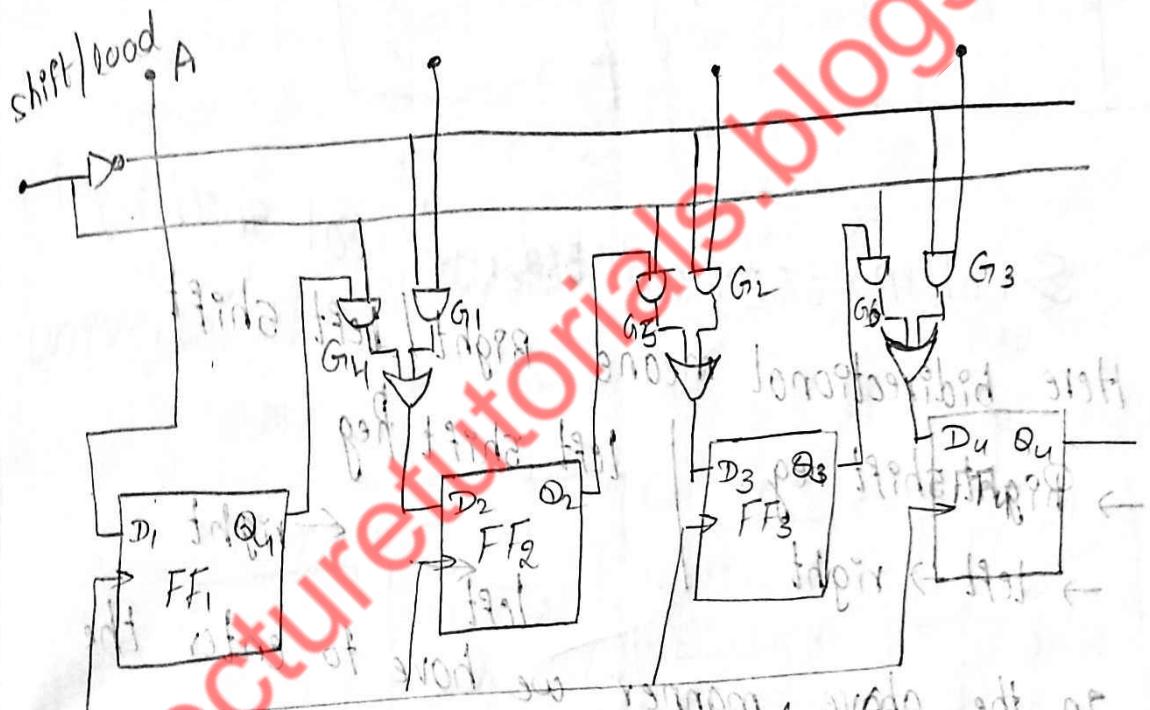4) Parallel-in. Serial out shift register



~~shift flood~~ = 30


~~shift flood~~ = ~~en~~ 0 0 0
0 0 0 0 ~~Disable~~ ~~en~~ ~~enable~~
~~load~~ ~~fault~~

$$\text{stofa} \cdot \overline{\text{baldeib}} \\ \text{shift} / \overline{\text{lood}} = 0$$

signature

```

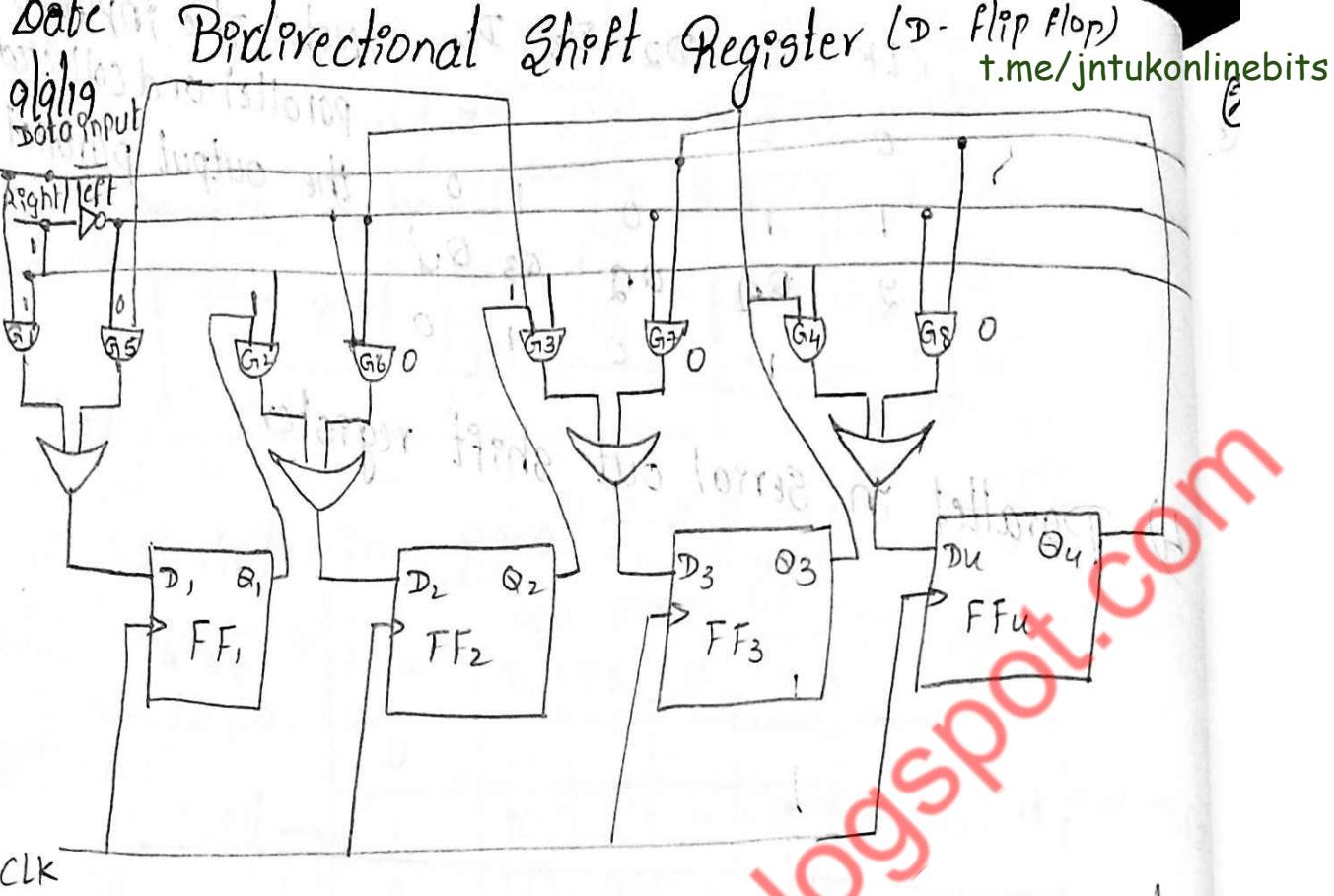graph LR
    G1((G1)) -- A --> G2((G2))
    G2 -- B --> G3((G3))
    G3 -- C --> D((D))
    D -- D --> G1
    D -- D --> E((E))
    E -- E --> G1
    
```



Serial-in - Serial out Bidirectional shift register

Here bidirectional means Right / left shift

→ Right shift reg | left shift Reg

→ left → right | ← right

In the above manner we have to enter the data according to arrow marks


| | G ₁ | G ₂ | G ₃ | G ₄ | G ₅ | G ₆ | G ₇ | G ₈ |
|------------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|
| Right / Left = , | 1 | 1 | 1 | 1 | 0 | 0 | 0 | 0 |
| enabled state | | | | | | | disabled state | |

example


initial state
 $\begin{matrix} CLK \\ 0 \\ \downarrow \end{matrix} \rightarrow \begin{matrix} D_1 \\ 0 \\ \downarrow \end{matrix} \rightarrow \begin{matrix} D_2 \\ 0 \\ \downarrow \end{matrix} \rightarrow \begin{matrix} D_3 \\ 0 \\ \downarrow \end{matrix} \rightarrow \begin{matrix} D_4 \\ 0 \\ \downarrow \end{matrix} \rightarrow \text{initial state}$

Data input 1111 left

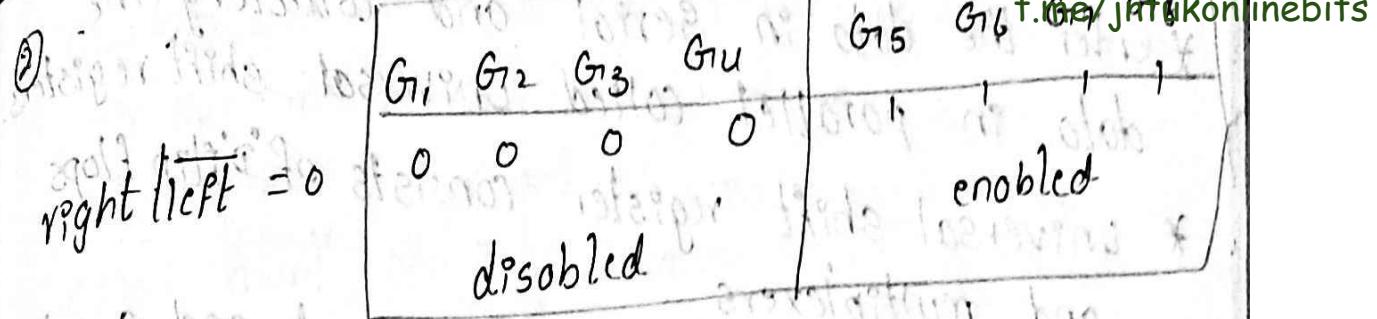
$2 \rightarrow 1 \rightarrow 1 \rightarrow 0 \rightarrow 0$
 $3 \rightarrow 1 \rightarrow 1 \rightarrow 1 \rightarrow 0$
 $4 \rightarrow 1 \rightarrow 1 \rightarrow 1 \rightarrow 1$




example

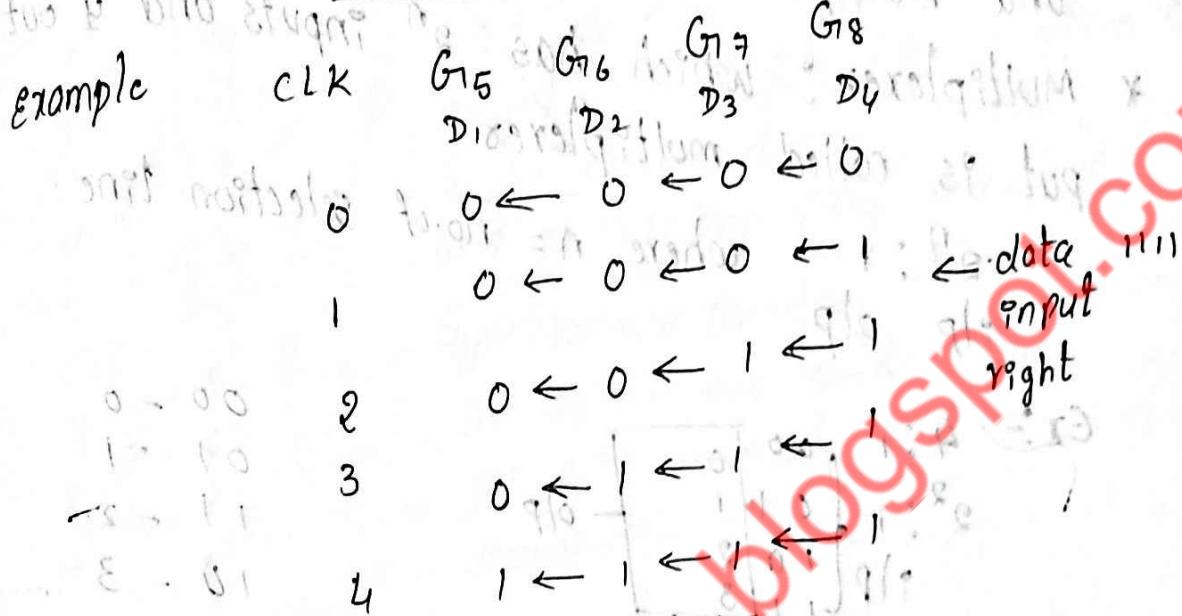

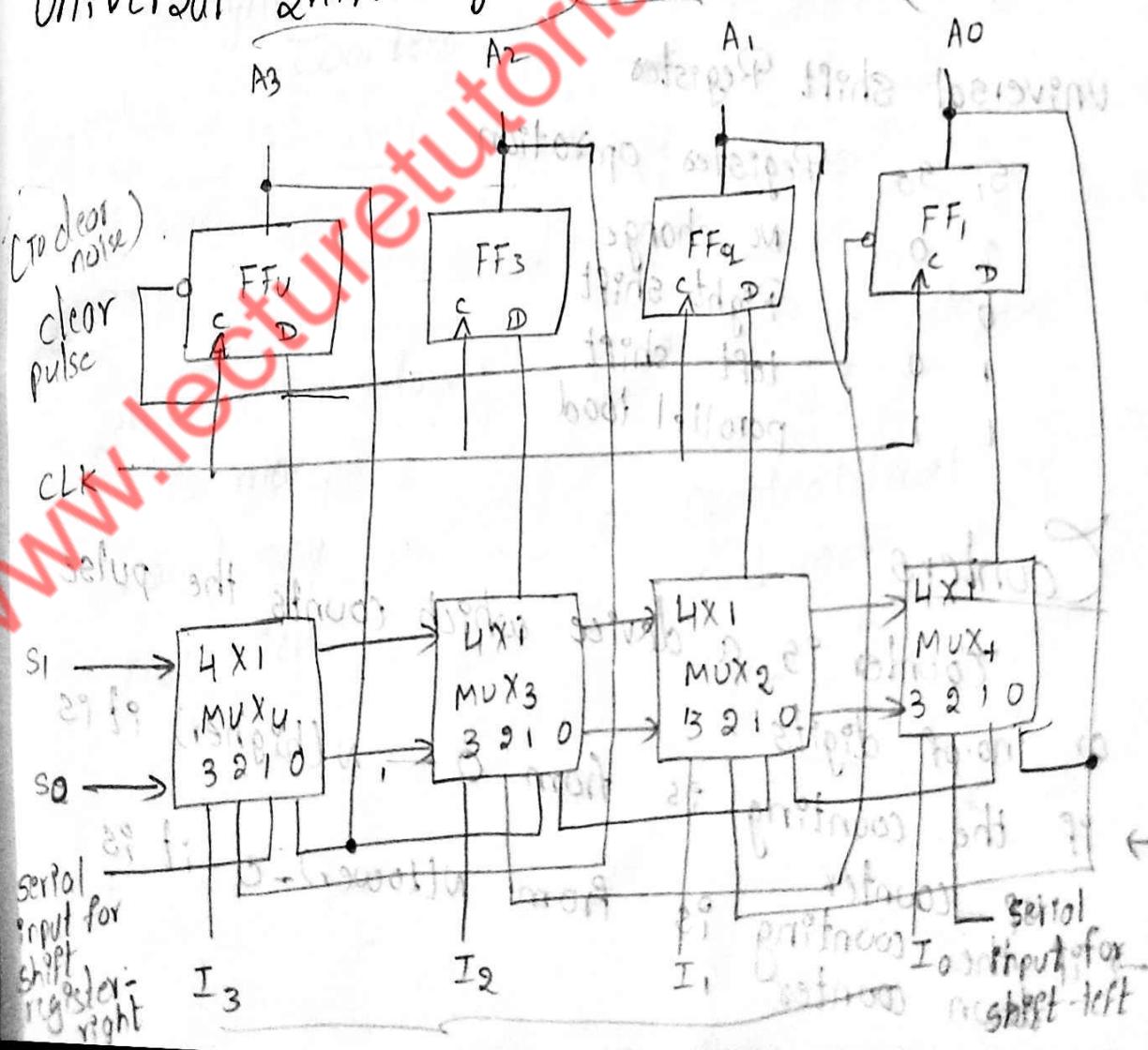universal Shift Registers parallel outputs



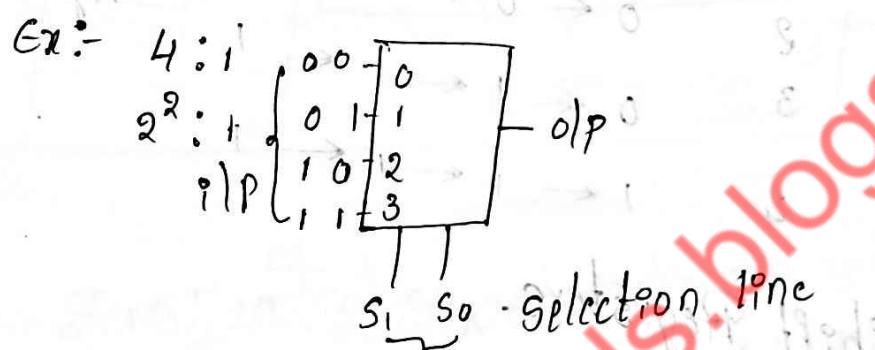- * Enter the data in serial and collecting the data in parallel called universal shift registers.
- * universal shift register consists of D flip flops and multiplexers
- * Multiplexer: which has 2^n inputs and 1 output is called multiplexer
- $2^n : i$ where $n = \text{no. of selection line}$



| | |
|----|----|
| 00 | -0 |
| 01 | -1 |
| 11 | -2 |
| 10 | -3 |

Universal Shift Register

S_1, S_0 Register Operation

| | |
|-----|---------------|
| 0 0 | No change |
| 0 1 | Right shift |
| 1 0 | Left shift |
| 1 1 | parallel load |

Counters

Counter is a device which counts the pulse

or no. of digits

- if the counting is from 0 - N (higher) it is up counter
- if the counting is from N (lower) - 0 it is down counter

Counters are of two types.

t.me/jntukonlinebits

→ Synchronous counters

→ Asynchronous counters

CLK decimal count

1 0
2 1
3 2
4 3
5 4
6 5
7 6
8 7
9 8
10 9


Asynchronous counters

In asynchronous counters, the output of first flip flop is given to the CLK as second flip flop and propagation delay is occurred

Synchronous Counters

In synchronous counters, the CLK pulse is same and no propagation delay

Asynchronous Counters

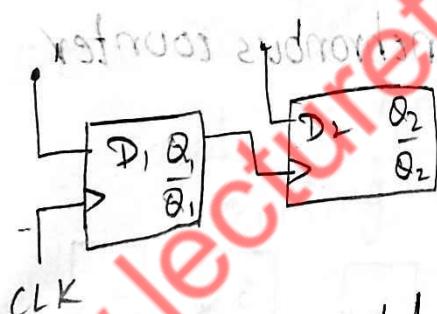


propagation delay

is more

count easy

cost less

Synchronous Counters

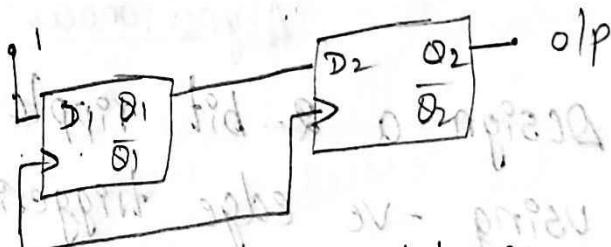

propagation delay is less

count difficult
cost more

$$S = \frac{1}{2} \cdot 1 = 0.5 \text{ ms}$$


$$S = \frac{1}{2} \cdot 1 = 0.5 \text{ ms}$$

$$(1/2 \times t)$$

1. Design a two bit ripple up-counter
 J-K flip flop by negative edge triggering


no. of bits $n = 2$

no. of flip flops $= 2$


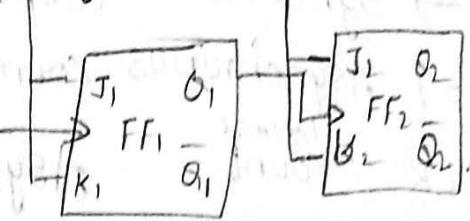


(J K F/F)

By using 're' edge triggering

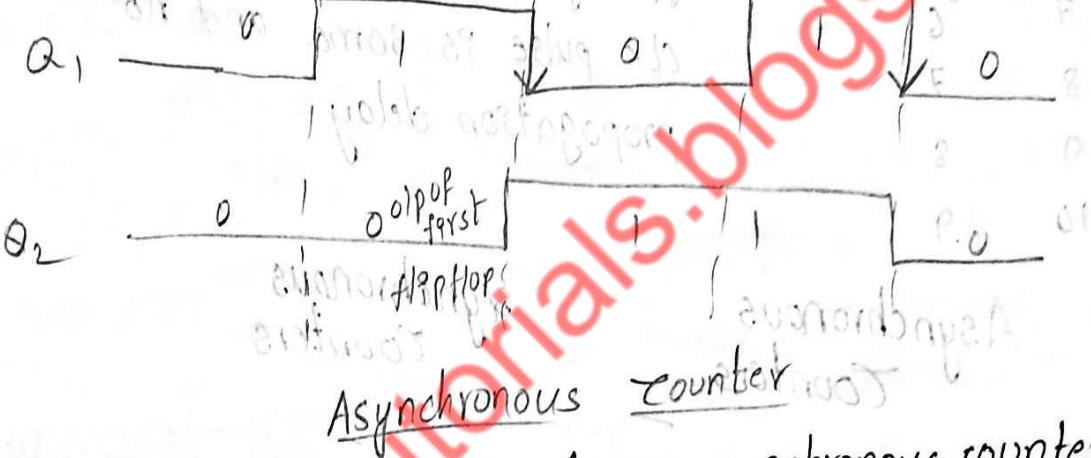

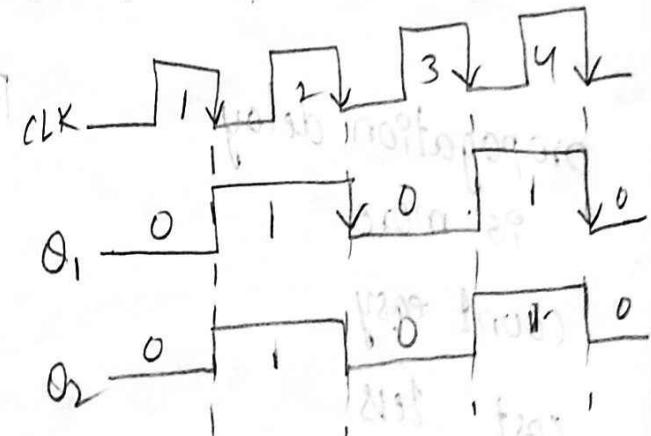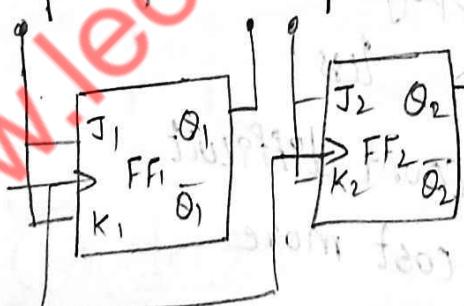2. Design a 2-bit ripple up-synchronous counter
 using -ve edge triggering



$n = \text{no. of bits} = 2$

no. of F/F = 2

(J K F/F)

synchronous counter by -ve edge triggering

Design of Synchronous Counters

It is represented as bit counter or divide by 2^n or n counter or modulo n counter or mod n counter.

Design a decade counter or mod 10 counter using T flip flop.

Counters.

n bit counter

modulo - N counter

MOD - N counter

Divide by N counter

$N = \text{no. of counter}$.

$N = 0 \text{ to } N-1$

Ex: $N = 10$

Decade Counter

Count the numbers $= N = 10$

Counting sequence $(0-(N-1))$
 $(0-9)$

No. of f/f required to construct the counter

$n = \text{no. of f/f}$

$n = 4$



$$2^n \geq N$$

$$n=0 \quad 2^0 \not\geq 10$$

$$n=1 \quad 2^1 \not\geq 10$$

$$n=2 \quad 2^2 \not\geq 10$$

$$n=3 \quad 2^3 \not\geq 10$$

$$n=4 \quad 2^4 \geq 10$$

| CLK | Dc no | present state | | | | Next state | | | |
|-----|-------|----------------|----------------|----------------|----------------|------------------|------------------|------------------|------------------|
| | | Q _D | Q _C | Q _B | Q _A | Q _{D+1} | Q _{C+1} | Q _{B+1} | Q _{A+1} |
| 1 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 0 | 1 |
| 2 | 1 | 0 | 0 | 1 | 0 | 0 | 0 | 1 | 0 |
| 3 | 2 | 0 | 1 | 1 | 3 | 0 | 0 | 1 | 0 |
| 4 | 3 | 0 | 1 | 0 | 4 | 0 | 1 | 0 | 1 |
| 5 | 4 | 0 | 1 | 0 | 5 | 0 | 0 | 1 | 0 |
| 6 | 5 | 0 | 1 | 0 | 6 | 0 | 0 | 0 | 1 |
| 7 | 6 | 0 | 1 | 1 | 7 | 0 | 0 | 0 | 0 |
| 8 | 7 | 0 | 1 | 0 | 8 | 0 | 0 | 1 | 1 |
| 9 | 8 | 1 | 0 | 0 | 9 | 1 | 0 | 0 | 1 |
| 10 | 9 | 1 | 0 | 0 | 10 | 0 | 0 | 1 | 0 |

 T_A

| Q _D Q _C Q _B Q _A | | Dc no | |
|---|----|-------|----|
| 00 00 01 11 10 | | 00 | |
| 1 | 0 | 1 | 1 |
| 2 | 1 | 1 | 2 |
| 3 | 2 | 1 | 3 |
| 4 | 3 | 1 | 4 |
| 5 | 4 | 1 | 5 |
| 6 | 5 | 1 | 6 |
| 7 | 6 | 1 | 7 |
| 8 | 7 | 1 | 8 |
| 9 | 8 | X | 10 |
| 10 | 9 | X | 11 |
| 11 | 10 | X | 12 |

 T_B

| Q _D Q _C Q _B Q _A | | Dc no | |
|---|---|-------|----|
| 00 00 00 01 10 | | 00 | |
| 1 | 0 | 1 | 1 |
| 2 | 1 | 1 | 2 |
| 3 | 1 | 2 | 3 |
| 4 | 2 | 1 | 4 |
| 5 | 3 | 1 | 5 |
| 6 | 4 | 1 | 6 |
| 7 | 5 | 1 | 7 |
| 8 | 6 | 1 | 8 |
| 9 | 7 | X | 10 |
| 10 | 8 | X | 11 |

 T_D guard

double octent

 T_C

| Q _D Q _C Q _B Q _A | | Dc no | |
|---|---|-------|----|
| 00 00 00 01 10 | | 00 | |
| 1 | 0 | 1 | 1 |
| 2 | 1 | 1 | 2 |
| 3 | 1 | 2 | 3 |
| 4 | 2 | 1 | 4 |
| 5 | 3 | 1 | 5 |
| 6 | 4 | 1 | 6 |
| 7 | 5 | 1 | 7 |
| 8 | 6 | X | 10 |
| 9 | 7 | X | 11 |

guard

$$= Q_D \cdot Q_C \cdot Q_B \cdot Q_A$$

$$= Q_D \cdot Q_B \cdot Q_A$$

$$= Q_C \cdot Q_B \cdot Q_A$$

$$= Q_B \cdot Q_A$$

$$= Q_D \cdot Q_A$$

| Q _D Q _C Q _B Q _A | | Dc no | |
|---|---|-------|----|
| 00 00 00 01 10 | | 00 | |
| 1 | 0 | 1 | 1 |
| 2 | 1 | 1 | 2 |
| 3 | 1 | 2 | 3 |
| 4 | 2 | 1 | 4 |
| 5 | 3 | 1 | 5 |
| 6 | 4 | 1 | 6 |
| 7 | 5 | 1 | 7 |
| 8 | 6 | X | 10 |
| 9 | 7 | X | 11 |

$$T_D = (Q_B \cdot Q_C + Q_B \cdot Q_A) \text{ or } T_D = Q_D \cdot Q_A$$

$$T_B = Q_C \cdot Q_A$$

$$T_A = Q_D \cdot Q_A$$

$$T_D = Q_B \cdot Q_A + Q_C \cdot Q_B$$

$$T_B = Q_B \cdot Q_A$$

$$T_A = Q_D \cdot Q_A$$

excitation table of T flip-flop

| TD | TC | TB | TA | P.S | N.S | T |
|----|----|----|----|-----|-----|----|
| 0 | 0 | 0 | 1 | 1 | 1 | |
| 0 | 0 | 0 | 0 | 0 | 0 | |
| 0 | 1 | 0 | 1 | 1 | 1 | |
| 0 | 1 | 0 | 0 | 0 | 0 | |
| 1 | 0 | 0 | 0 | 0 | 1 | -1 |
| 1 | 0 | 0 | 1 | 0 | 0 | -1 |
| 1 | 1 | 0 | 0 | 1 | 0 | -1 |
| 1 | 1 | 0 | 1 | 0 | 1 | -1 |
| 1 | 1 | 1 | 0 | 1 | 1 | -1 |
| 1 | 1 | 1 | 1 | 0 | 1 | -1 |




$$T_C = Q_B \cdot Q_A$$

clk

Timing Diagram

t.me/jntukonlinebits

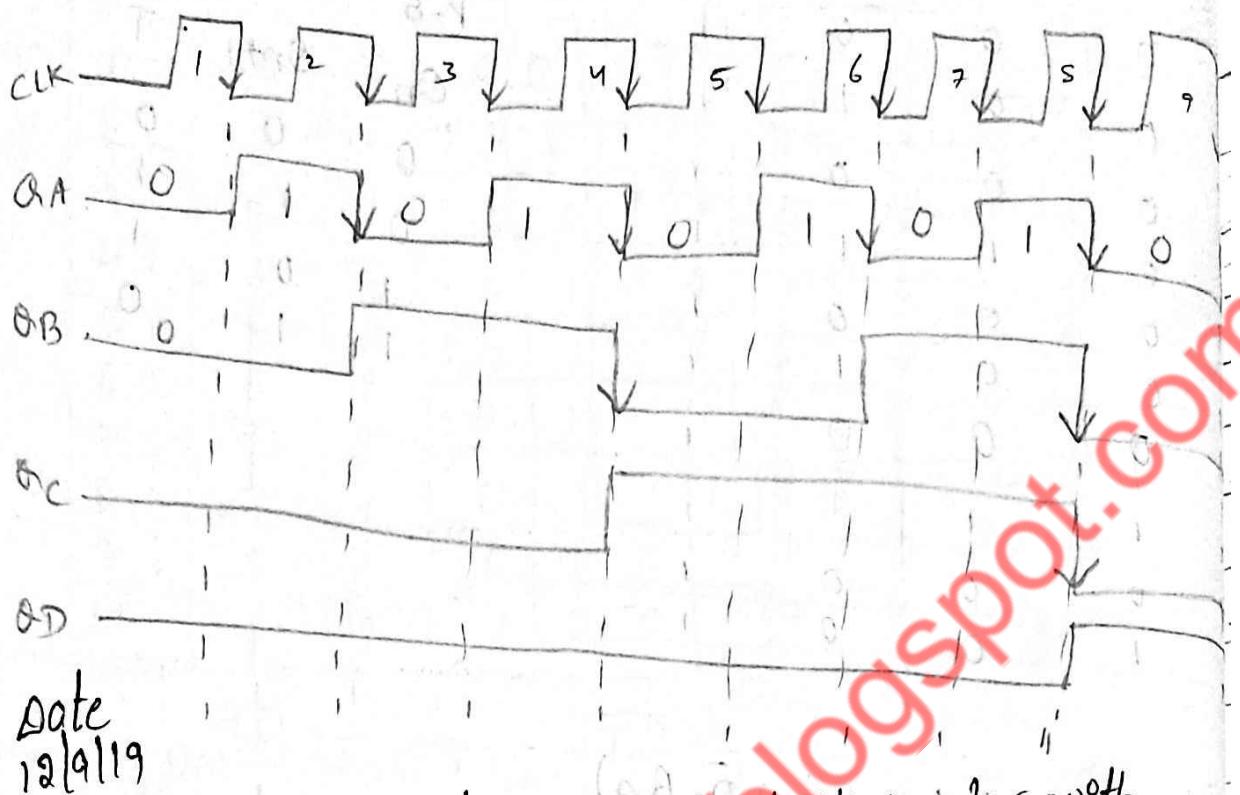

Date
12/01/19

Design a 10 bit ring and shift counter with
D flip flops

10 bit shift and ring counter

It is called shift counter because it shifts the

value from present to next

It is called ring counter when the cycle is
repeated after counting the maximum value

10 bit counter ; $N = 10$ (0 - 9)

Shift counter Ring counter



0 - 0

1

2

3

4

5

6


7

8

9

| CLK Decim Num ber | A | B | C | D | E | F | G | H | I | J |
|----------------------------|------------|------------|------------|------------|------------|------------|------------|------------|------------|------------|
| | Θ_A | Θ_B | Θ_C | Θ_D | Θ_E | Θ_F | Θ_G | Θ_H | Θ_I | Θ_J |
| 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 2 | 1 | 0 | 1 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 3 | 2 | 0 | 0 | 1 | 0 | 0 | 0 | 0 | 0 | 0 |
| 4 | 3 | 0 | 0 | 0 | 1 | 0 | 0 | 0 | 0 | 0 |
| 5 | 4 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 0 | 0 |
| 6 | 5 | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 0 |
| 7 | 6 | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 |
| 8 | 7 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 0 |
| 9 | 8 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 |
| 10 | 9 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 |

Timing Diagram

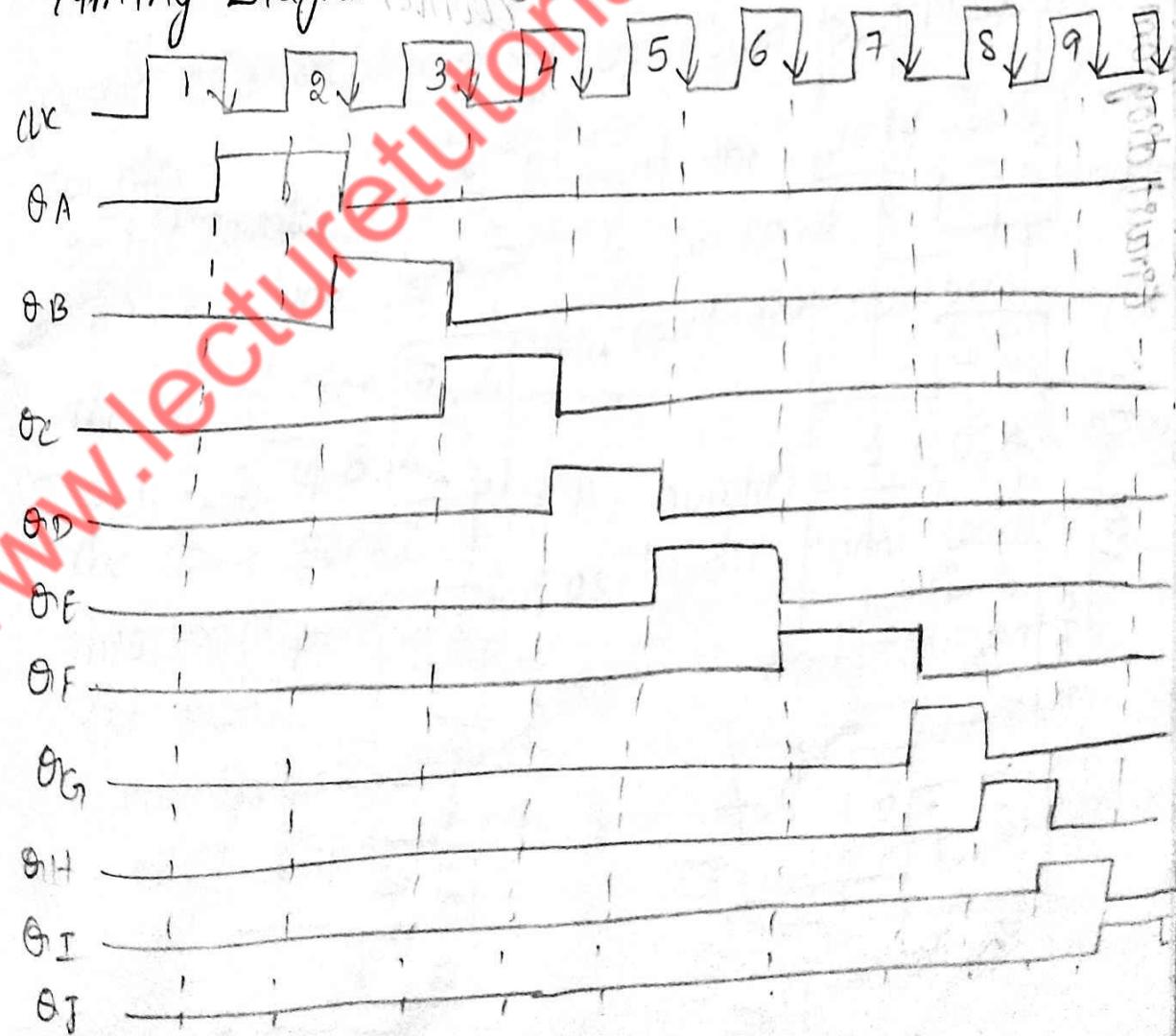


Ring counter Circuit diagram for shift and ring counter



clear pulse/preset

| CLK | Q_A | Q_B | Q_C | Q_D | \bar{Q}_D |
|-----------------------|-------|-------|-------|-------|-------------|
| 0 | 0 | 0 | 0 | 0 | 1 |
| 1 | 1 | 0 | 0 | 0 | 1 |
| 2 | 1 | 1 | 0 | 0 | 1 |
| 3 | 0 | 1 | 1 | 0 | 1 |
| 4 | 1 | 1 | 1 | 1 | 0 |
| 5 | 0 | 1 | 1 | 1 | 0 |
| again | 0 | 0 | 0 | 1 | 0 |
| CLK pulse is given | 0 | 0 | 0 | 1 | 0 |
| 8 | 0 | 0 | 0 | 1 | 0 |


Circuit diagram for Johnson counter

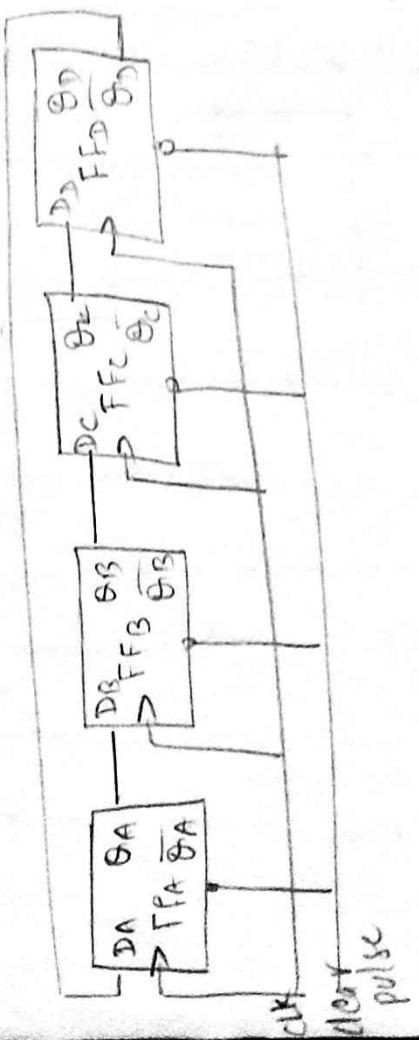

next pulse

Design a 4-bit Johnson Counter or a 4-bit shift and twisted ring counter with D flip flops
 4 bit Johnson counter / 4 bit and twisted ring counter

$$N = 4(0-3) \quad [4+4 = 8(0-7)]$$

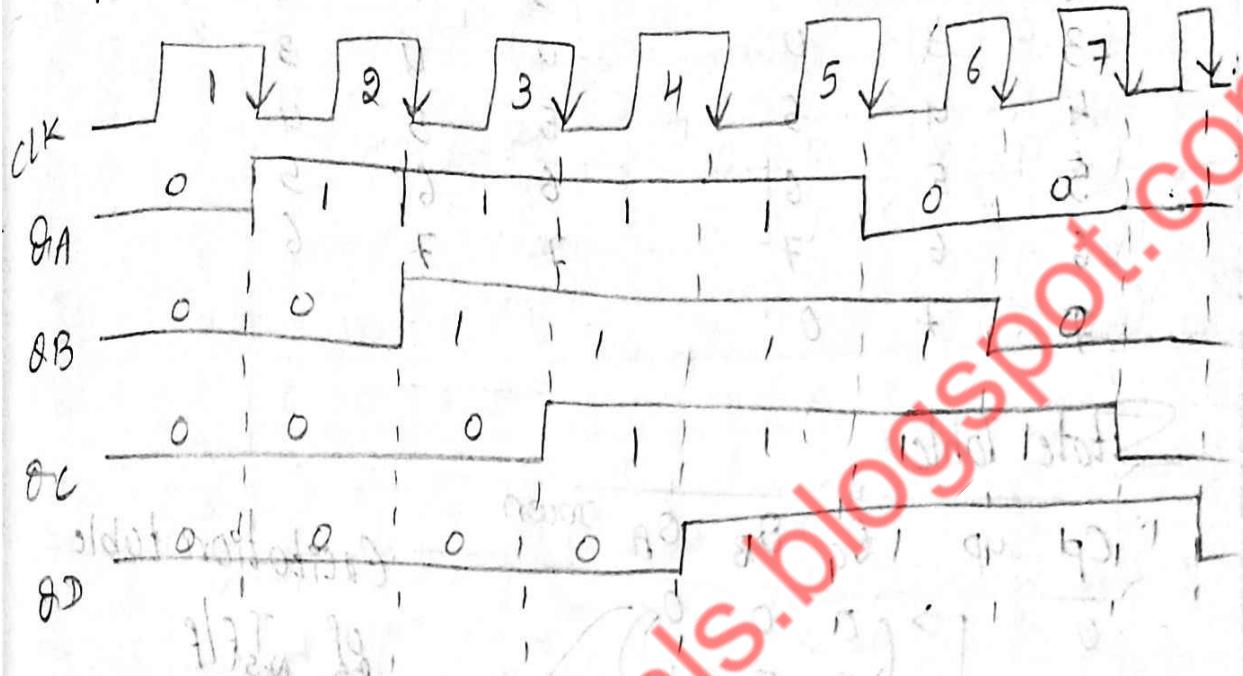

Timing Diagram
 Design a 3-bit [down-5] up-down synchronous

counter

3-bit counter enable to count the numbers as $2^3 = 8$

$2^3 = 8$: you can be able to count 8 i.e., (0-7)

The up-counter can able to count the numbers

0, 1, 2, 3, 4, 5, 6, 7, 0..

The down counter count the numbers 7, 6, 5, 4, 3, 2, 1, 0

This counter is known as bi-directional counter

(up-down)

Counting = N. sequence

No. of flip flops = $n = 3$

| Mode signal | |
|---------------|----------|
| up | down = 1 |
| → 1 | 0 |
| ON | OFF |
| UP counter | |
| up down = 0 | |
| → 0 | |
| OFF | ON |
| down counter | |

Date
13/9/19

T.me/jntukonlinebits

| | UP Counter | | Down Counter | |
|---|------------|-----|--------------|-----|
| | P.S | N.S | P.S | N.S |
| 0 | 0 | 1 | 0 | 7 |
| 1 | 1 | 2 | 1 | 0 |
| 2 | 2 | 3 | 2 | 1 |
| 3 | 3 | 4 | 3 | 2 |
| 4 | 4 | 5 | 4 | 3 |
| 5 | 5 | 6 | 5 | 4 |
| 6 | 6 | 7 | 6 | 5 |
| 7 | 7 | 0 | 7 | 6 |

State Table

| Cp | up | θ_C | θ_B | θ_A | down |
|----|----|------------|------------|------------|------|
| 0 | 0 | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 0 | 1 | 0 |
| 2 | 0 | 0 | 1 | 0 | 0 |
| 3 | 0 | 0 | 1 | 1 | 0 |
| 4 | 0 | 1 | 0 | 0 | 0 |
| 5 | 0 | 1 | 0 | 1 | 0 |
| 6 | 1 | 0 | 1 | 0 | 0 |
| 7 | 1 | 1 | 1 | 1 | 0 |

Excitation table

of N.S

| Qn | Qanti | T |
|----|-------|---|
| 0 | 0 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 0 |

For K-map

$$T_A = \sum_m (0, 1, 2, 3, 15)$$

$$T_B = \sum_m (0, 2, 4, 6, 9, 11, 13, 15)$$

$$T_C = \sum_m (0, 4, 11, 15)$$

Exco

Excitation table

present state

Next state

t.me/jntukonlinebits

| $\bar{U/D}$ | \bar{Q}_C | \bar{Q}_B | \bar{Q}_A | no need | Q_C+1 | $Q_B Q_A + 1$ | $Q_A + 1$ | T_C | T_B | T_A |
|-------------|-------------|-------------|-------------|---------|---------|---------------|-----------|-------|-------|-------|
| 0 | 0 | 0 | 0 | 0 | 0 | 1 | 1 | 1 | 1 | 1 |
| 1 | 0 | 1 | 0 | 1 | 1 | 0 | 0 | 0 | 0 | 1 |
| 2 | 0 | 2 | 0 | 1 | 0 | 2 | 0 | 1 | 10 | 1 |
| 3 | 0 | 3 | 0 | 1 | 1 | 3 | 0 | 1 | 20 | 0 |
| 4 | 0 | 4 | 1 | 0 | 0 | 4 | 0 | 1 | 39 | 1 |
| 5 | 0 | 5 | 1 | 0 | 1 | 5 | 1 | 0 | 40 | 0 |
| 6 | 0 | 6 | 1 | 1 | 0 | 6 | 1 | 0 | 150 | 1 |
| 7 | 0 | 7 | 1 | 1 | 1 | 7 | 1 | 1 | 060 | 0 |
| 8 | 1 | 0 | 0 | 0 | 0 | 8 | 0 | 0 | 110 | 0 |
| 9 | 1 | 1 | 0 | 0 | 1 | 9 | 0 | 1 | 020 | 1 |
| 10 | 1 | 2 | 0 | 1 | 0 | 10 | 0 | 1 | 130 | 0 |
| 11 | 1 | 3 | 0 | 1 | 1 | 11 | 1 | 0 | 41 | 1 |
| 12 | 1 | 4 | 1 | 0 | 0 | 12 | 1 | 0 | 150 | 0 |
| 13 | 1 | 5 | 1 | 0 | 1 | 13 | 1 | 1 | 060 | 1 |
| 14 | 1 | 6 | 1 | 1 | 0 | 14 | 1 | 1 | 170 | 0 |
| 15 | 1 | 7 | 1 | 1 | 1 | 15 | 0 | 0 | 01 | 1 |

| $\bar{U/D} \bar{Q}_C$ | \bar{Q}_A | T_A | $\bar{U/D} \bar{Q}_B \bar{Q}_A$ | T_B | $\bar{U/D} \bar{Q}_C \bar{Q}_B \bar{Q}_A$ | T_C |
|-----------------------|-------------|-------|---------------------------------|-------|---|-------|
| 00 | 00 | 01 | 11 | 10 | 00 | 01 |
| 01 | 10 | 15 | 17 | 11 | 01 | 13 |
| 11 | 11 | 13 | 15 | 14 | 11 | 12 |
| 10 | 18 | 19 | 11 | 16 | 10 | 14 |

$$q_1 \rightarrow \bar{U/D} \bar{Q}_A$$

$$q_2 \rightarrow \bar{U/D} \bar{Q}_B$$


$$p_1 \rightarrow \bar{U/D} \bar{Q}_B \bar{Q}_A$$

$$p_2 \rightarrow \bar{U/D} \bar{Q}_B \bar{Q}_A$$

$$T_B = \bar{U/D} \bar{Q}_A + \bar{U/D} \bar{Q}_A$$

$$T_C = \bar{U/D} \bar{Q}_B \bar{Q}_A + \bar{U/D} \bar{Q}_B \bar{Q}_A$$

Date 14/9/19
up/down = 1

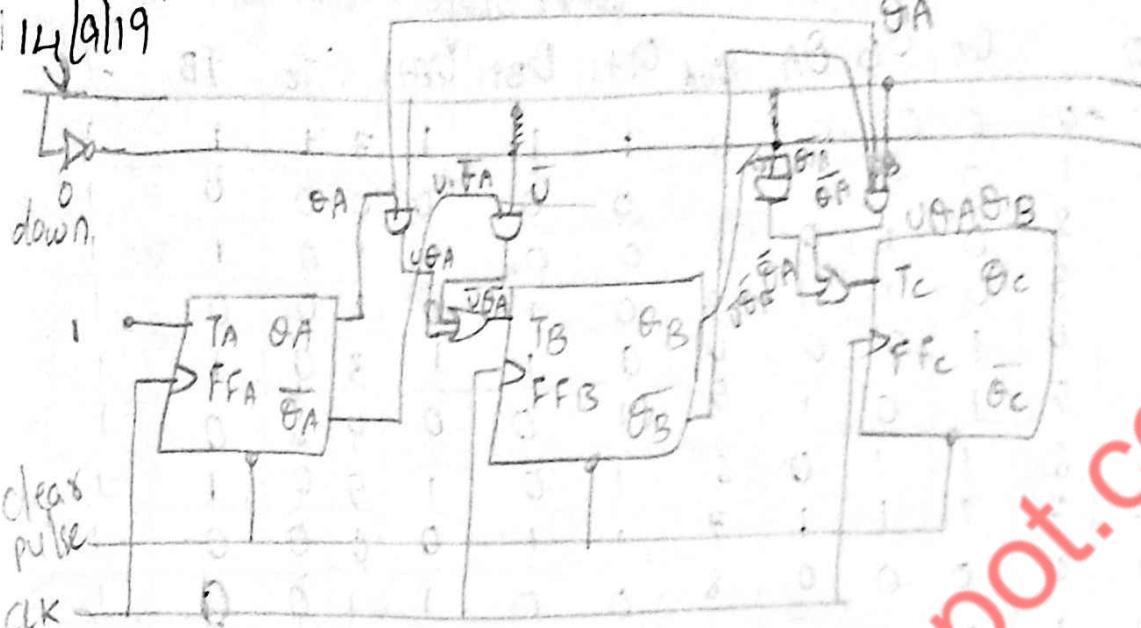

logic diagram of divide by 6 counter using T flip flop

Design divide by "6" counter

Mod 6 Counter

divide by 6 counter (01) MOD 6 - Counter
no. of counts = 6 ; counting range 0 - (N-1)
(0-5)

$$n = \text{no. of flip flops} \quad 2^n \geq N$$

$$n=1 \quad 2^1 \not\geq 6 \quad \text{No. of flip flops} = 3$$

$$n=2 \quad 2^2 \not\geq 6$$

$$n=3 \quad 2^3 \geq 6$$

$$\text{no. of bits} = \text{no. of flip flops} = 3$$

Note

$$\text{MOD } -6(0-5); n=3 \left(\frac{0-7}{6,7,0}\right)$$

don't care

$$-5(0-4); n=3 \left(\frac{0-7}{5,6,7}\right)$$

don't care

| P.S | N.S |
|-----|-----|
| 0 | 1 |
| 1 | 2 |
| 2 | 3 |
| 3 | 4 |
| 4 | 5 |
| 5 | 0 |

| CLK | $P_i S$ | | | | N's | | | | T_C | T_B | T_A |
|-----|------------|---------------------|------------|----------------|----------------|----------------|---|---|-------|-------|-------|
| | θ_C | $\theta_B \theta_A$ | θ_A | θ_{C+1} | θ_{B+1} | θ_{A+1} | | | | | |
| 0 | 0 | 0 0 | 0 | 1 | 0 | 0 | 1 | 0 | 0 | 0 | 1 |
| 1 | 1 | 0 0 | 1 | 2 | 0 | 1 | 0 | 0 | 1 | 1 | |
| 2 | 2 | 0 1 | 0 | 3 | 0 | 1 | 1 | 0 | 0 | 0 | 1 |
| 3 | 3 | 0 1 1 | 1 | 4 | 1 | 0 | 0 | 1 | 1 | 1 | |
| 4 | 4 | 1 0 0 | 5 | 1 | 0 | 1 | 0 | 0 | 0 | 0 | 1 |
| 5 | 5 | 1 0 1 | 0 | 0 | 0 | 0 | 0 | 1 | 0 | 1 | |
| 6 | 6 | X X X | | | | | | | | | |
| 7 | 7 | X X X | | | | | | | | | |

Excitation table of T flipflop

$$\text{On } \theta_{n+1} \quad T = \sum_m (0, 1, 2, 3, 4, 5)$$

$$T_B = \sum_m (1, 3)$$

$$T_C = \sum_m (3, 5)$$

| θ_C | $\theta_B \theta_A$ | | θ_C | $\theta_B \theta_A$ | | θ_C | $\theta_B \theta_A$ | |
|------------|---------------------|----|------------|---------------------|----|------------|---------------------|----|
| | 00 | 01 | 11 | 10 | 00 | 01 | 11 | 10 |
| 0 | 1 | 0 | 3 | 2 | 0 | 1 | 3 | 2 |
| 1 | 1 | X | X | X | 1 | 1 | 5 | 6 |

$$T_B = \bar{\theta}_C \cdot \theta_A$$

$$T_A = 1$$

$$T_C = P_2 + P_1 \rightarrow (\bar{\theta}_C \theta_A + \theta_B \theta_A)$$


| θ_C | $\theta_B \theta_A$ | | | | P_2 |
|------------|---------------------|----|----|----|-------|
| | 00 | 01 | 11 | 10 | |
| 0 | 0 | 1 | 3 | 2 | 0 |
| 1 | 1 | X | X | X | 1 |

$$T_C = \bar{\theta}_C \theta_A + \bar{\theta}_C \theta_B \theta_A$$

$$P_1 (\bar{\theta}_C \theta_A) + P_2 \bar{\theta}_C$$

$$(\bar{\theta}_C + \theta_C) (\theta_B \theta_A)$$
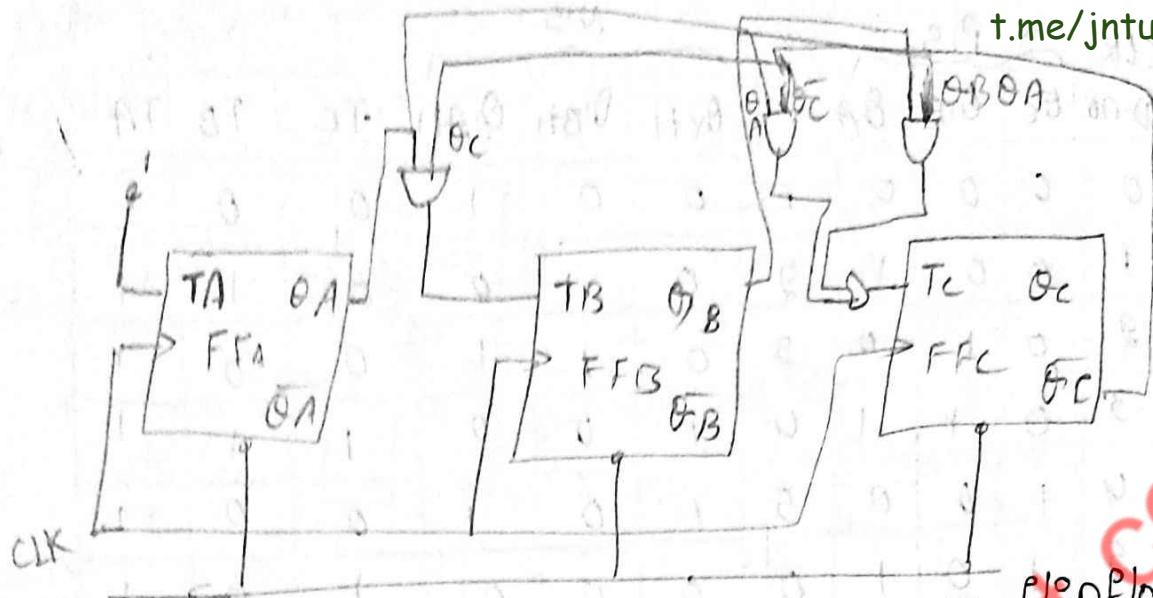
$$\bar{\theta}_C \theta_A + \theta_B \theta_A$$



Date Design Mod-12 Counter using T- flipflops

16/9/19 The total no of counts $N = 12$

Counting sequence - 0 to $N-1$

0 to $(12-1)$

0 to 11 (12, 13, 14, 15)

don't cares

No. of flip flops - $n - 2^n \geq N$

| | $2^1 \geq 12$ |
|---|---------------|
| 1 | $2^1 \geq 12$ |
| 2 | $2^2 \geq 12$ |
| 3 | $2^3 \geq 12$ |
| 4 | $2^4 \geq 12$ |


T flip flop

P.S N.S

| | P.S | N.S |
|---|-----|-----|
| 0 | 0 | 0 |
| 1 | 0 | 1 |
| 2 | 1 | 1 |
| 3 | 1 | 1 |
| 4 | 1 | 0 |

No. of flip flops = No. of binary bits
 $n = 4$; $0 - (2^n - 1)$

counter

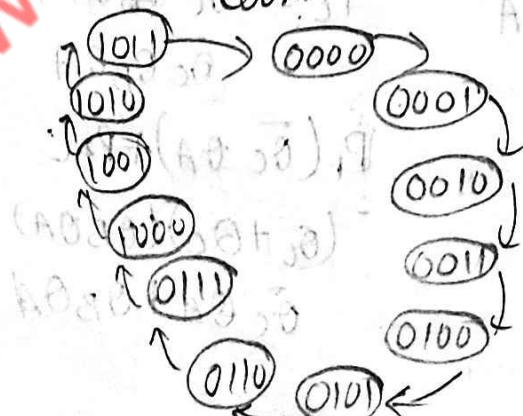

| | P.S | N.S |
|----|-----|-----|
| 0 | 0 | 1 |
| 1 | 1 | 2 |
| 2 | 2 | 3 |
| 3 | 3 | 4 |
| 4 | 4 | 5 |
| 5 | 5 | 6 |
| 6 | 6 | 7 |
| 7 | 7 | 8 |
| 8 | 8 | 9 |
| 9 | 9 | 10 |
| 10 | 10 | 11 |
| 11 | 11 | 0 |

| D.NO | θ_D | θ_C | θ_B | θ_A | θ_{D+1} | θ_{C+1} | θ_{B+1} | θ_{A+1} | T_D | Time/jntukonlinebits |
|------|------------|------------|------------|------------|----------------|----------------|----------------|----------------|-------|----------------------|
| | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 0 | TA |
| 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 0 | 0 | 2 | 0 | 0 | 1 | 0 | 0 |
| 2 | 0 | 0 | 1 | 0 | 3 | 0 | 0 | 1 | 1 | 0 |
| 3 | 0 | 0 | 0 | 0 | 4 | 0 | 1 | 0 | 0 | 1 |
| 4 | 0 | 1 | 0 | 0 | 5 | 0 | 1 | 0 | 1 | 0 |
| 5 | 0 | 1 | 0 | 1 | 6 | 0 | 1 | 1 | 0 | 1 |
| 6 | 0 | 1 | 1 | 0 | 7 | 0 | 1 | 1 | 0 | 0 |
| 7 | 0 | 1 | 1 | 1 | 8 | 1 | 0 | 0 | 1 | 1 |
| 8 | 1 | 0 | 0 | 0 | 9 | 1 | 0 | 0 | 0 | 0 |
| 9 | 1 | 0 | 0 | 1 | 10 | 1 | 0 | 1 | 0 | 1 |
| 10 | 1 | 0 | 1 | 0 | 11 | 1 | 0 | 1 | 0 | 0 |
| 11 | 1 | 0 | 1 | 1 | 0 | 0 | 0 | 0 | 1 | 1 |

$$TA = \sum_m (0, 1, 2, \dots, 11)$$

$$TB = \sum_m (1, 3, 5, 7, 9, 11)$$

$$TC = \sum_m (3, 7) ; TD = \sum_m (7, 11)$$

| | | TA | | | |
|------------|------------|-----|-----|-----|----|
| θ_D | θ_B | 00 | 01 | 11 | 10 |
| 00 | 10 | 11 | 13 | 12 | |
| 01 | 14 | 15 | 17 | 16 | |
| 11 | X12 | X13 | X15 | X14 | |
| 10 | 8 | 9 | 11 | 10 | |

| | | TB | | | |
|------------|------------|-----|-----|-----|----|
| θ_D | θ_B | 00 | 01 | 11 | 10 |
| 00 | 00 | 0 | 1 | 3 | 2 |
| 01 | 01 | 0 | 15 | 17 | 16 |
| 11 | X12 | X13 | X15 | X14 | |
| 10 | 8 | 19 | 11 | 1 | 10 |

Octent (1)

| | | TC | | | |
|------------|------------|-----|-----|-----|----|
| θ_D | θ_B | 00 | 01 | 11 | 10 |
| 00 | 0 | 1 | (1) | 2 | |
| 01 | u | 5 | (1) | 6 | |
| 11 | X12 | X13 | X15 | X14 | |
| 10 | 8 | 9 | 11 | 10 | |

$$\text{pair}(3, 7); TC = \overline{\theta_D} \theta_B \theta_A$$

$$\text{Octent } TB = \theta_A$$


| | | TD | | | |
|------------|------------|-----|-----|-----|----|
| θ_D | θ_B | 00 | 01 | 11 | 10 |
| 00 | 0 | 1 | 3 | 2 | |
| 01 | u | 5 | (1) | 6 | |
| 11 | X12 | X13 | X15 | X14 | |
| 10 | 8 | 9 | 11 | 10 | |

$$\text{pair}(7, 5); \text{pair}(15, 11)$$

$$TD = \theta_C \theta_B \theta_A + \overline{\theta_D} \theta_B \theta_A$$

$$T_A = 1^\circ, T_B = \theta_A, T_C = \bar{\theta}_D \theta_B \theta_A, T_D = \theta_D \theta_B \theta_A$$

onlinebits.in/

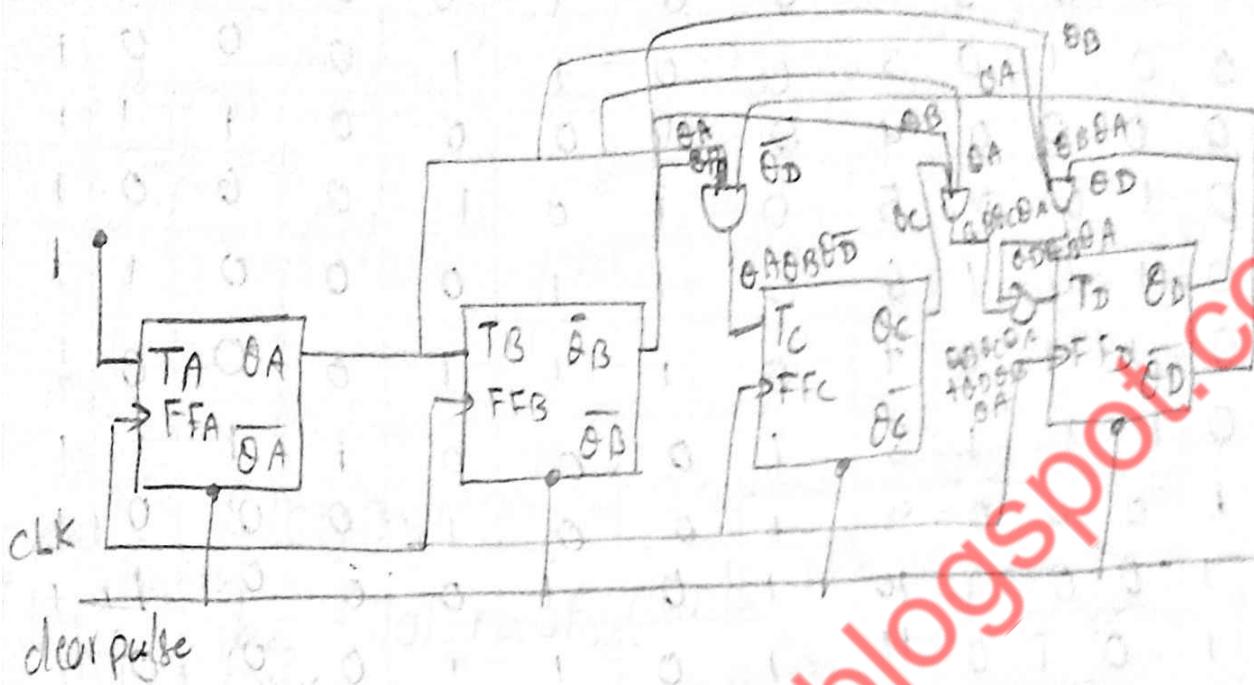

www.lecturetutorials.blogspot.com